

FREE SUPPLEMENT
TEST & MEASUREMENT


Take part in our
winter competition
See contents page for details

10
22
36
39
40
54
40 73
ELECTRONICS

**VIDEO
COPY PROCESSOR**

**STEREO
MICROPHONE
AMPLIFIER**

**MINI 80-METRE
RECEIVER**

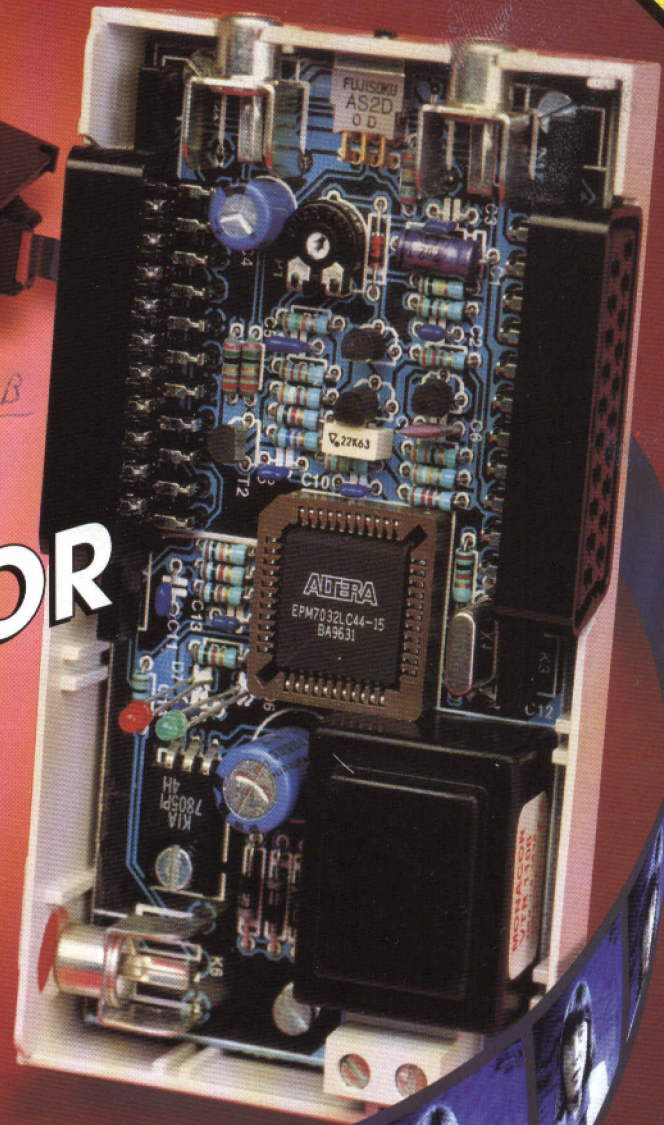


November 1997 Volume 23
Number 260 ISSN 0268/4519


**16-page SUPPLEMENT on
Test & Measurement**
Centrefold

**International Autumn/Winter
Prize Competition**
See pages 43 and 75

Video copy processor 28

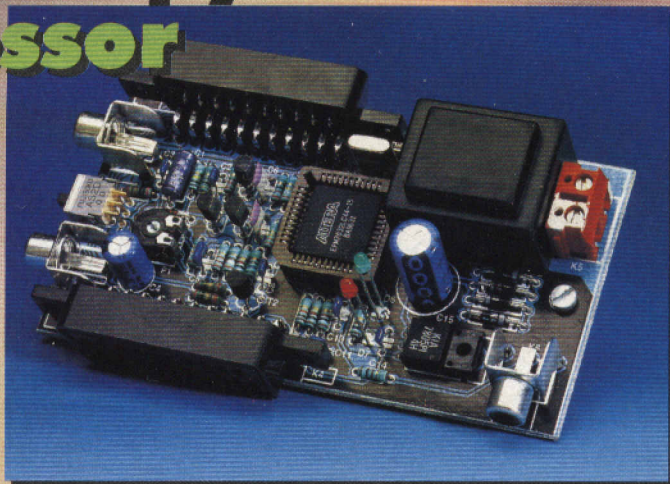

Stereo microphone amplifier

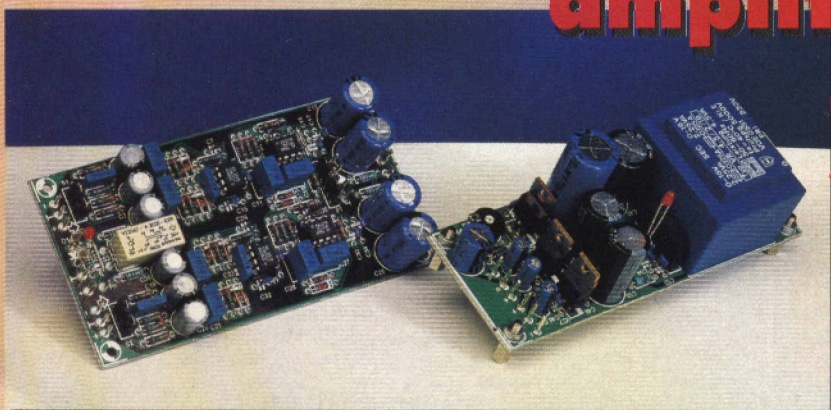

22

48 Digital signal processing



APPLICATION NOTE

- 40 Type TMP12
airflow and temperature sensor
An Analog Devices Application

AUDIO & HI-FI

- 22 PROJECT: Stereo microphone
☆☆ amplifier
Design by J Brangé
- 28 PROJECT: Video copy processor
☆☆ Design by W Foede
- 58 PROJECT: The wall box
☆ Design by H Baggen

GENERAL INTEREST

- 46 PROJECT: Radar-controlled door
☆☆ opener
Design by S Parizet
- 48 Digital Signal Processing
By our Editorial Staff
- 54 Make your own front panels
By our Design Staff

RADIO & TELEVISION

- 11 PROJECT: 80-metres receiver
☆☆ Design by Eric Edwards GW8LJJ

TEST & MEASUREMENT

- 16 PROJECT: Hygrometer
☆ Design by H Bonekamp


MISCELLANEOUS INFORMATION

- 73 Data sheets
* Electronics now
- 67 Electronics on line: DSPs on the Internet
- 82 Index of advertisers
- 19 In passing ...
* New Books
- 82 Next month in Elektor Electronics
- 36 Readers' letters: P O Box 1414
- 68 Product news
- 70 Readers' services


* It is regretted that, owing to lack of space, the columns 'Electronics Now' and 'New Books' have had to be held over to next month.

Copyright © 1997 Segment BV

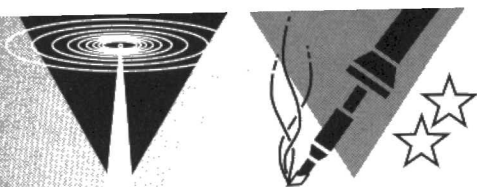A B C
AUDIT BUREAU OF CIRCULATIONS
CONSUMER PRESS



80-metres receiver

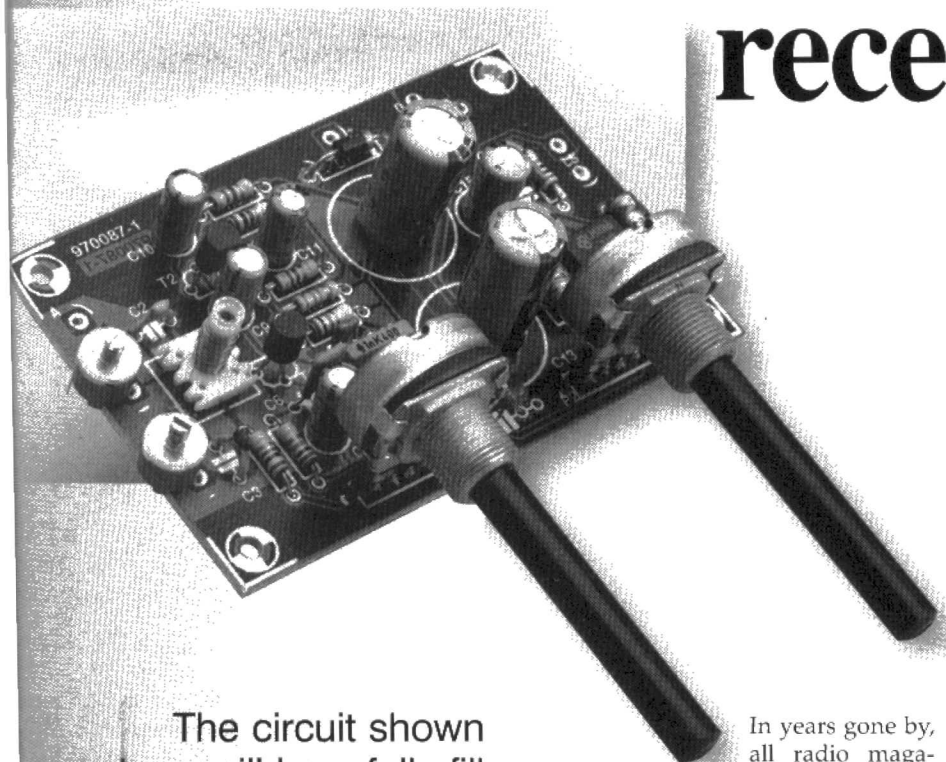

The circuit shown here will hopefully fill an important gap, so missing, in current DIY electronics. So, leave the computer alone for one night and let's build a short-wave radio. The 80-m band CW/SSB receiver to be described is simple to construct, yet is capable of high performance with a good aerial and, equally important, a good earth.

In years gone by, all radio magazines produced 'blueprints'. These were circuit diagrams on a separate pull-out sheet that was blue and contained instructions to make a radio (wireless) set. They were the *plans*. Although the blueprints have long gone, and there is still a lot of interest in home constructing of radios, there does seem to be little information on building from the junk box. By contrast, there have been many articles where specialised components are required or coils have to be sourced commercially.

The radio we will build is of the regenerative type. The circuit is adjusted to the point of just oscillating when it is at its most sensitive. With a few minutes practice this control will become second nature in using whilst tuning the band.

The band I have chosen is eighty metres (3.5 MHz). This is a good frequency band to listen to local and DX (long-distance) radio amateurs. I have decided to use radio amateurs as our listening choice because on this band, and indeed all other short-wave bands, radio amateurs use single-side-band and CW (Morse code). This receiver is best suited for receiving these modes of transmissions.

To start with, you will need a box of some sort to house the receiver. This can be any size and type to suit your own personal taste. I used two boxes, one for the radio circuit and the other one for the loudspeaker. You can, of course, build the complete radio and loudspeaker into one box. This can be

die-cast or any other type as long as it is strong. With any radio equipment, stability is most important. The radio is not to be built into a shoe box!

DESIGN PRINCIPLE

As stated earlier, the radio is of the regenerative type. This principle was used in early radios employing a *reaction control*. The principle is, part of the output signal is sent back to the input and is amplified, this again is sent back and amplified even more. The amount of positive feedback is controlled by a regenerative potentiometer to the point of *just oscillating*. Since received signals present variable signal levels at the input of the receiver (albeit of the order of micro-volts), they actually control the oscillator activity. In this way we can receive SSB and CW signals at good sensitivity.

The *selectivity* can be controlled by either a very slow motion tuning drive or another variable tuning capacitor wired in parallel with the main tuning to provide what was called *bandspread* (or fine tuning). The tuning arrangement I used on one of my designs was from an old frequency wavemeter. This had a suitable tuning capacitor and a very slow tuning dial. Another of my designs used a 150-pF main tuning capacitor and a smaller tuning capacitor of about 30 pF as the bandspread control. A 150-pF or so can be made from a standard tuning capacitor by removing some of the plates. These are usually crimped onto the main shaft and can be extracted with pliers and brute force. Just imagine you are a dentist while tugging away at the capacitor vanes! Leaving about five or six vanes will be a useful main tuning control. Of course, you can buy one of these but they will be expensive as commercial radio manufactures do not use many of these nowadays. Look around on radio rallies or in junk stores for suitable tuning capacitors, or even old radios if they are not too expensive. A tuning type capacitor is also used in series with the aerial (it must be insulated from the front panel). This control is used to introduce a mismatch at the input and so attenuate strong signals to prevent overloading. You will soon realise the

By Eric Edwards, GW8LJJ

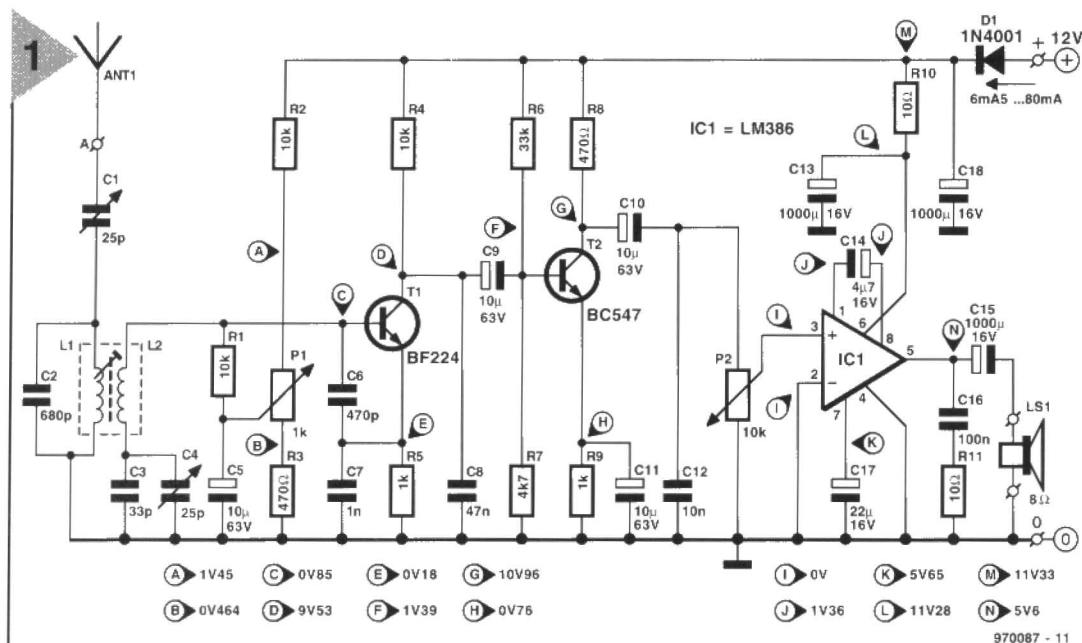


Figure 1. Circuit diagram of the CW/SSB regenerative receiver for the 80-m amateur radio band.

sensitivity of this little receiver, and you will be keeping the aerial at some attenuation.

CIRCUIT DESCRIPTION

The circuit as shown in **Figure 1** uses a Clapp oscillator in which the base bias of the oscillator transistor is adjusted by the 'reaction' potentiometer, P1. The tuning is by means of a variable capacitor or a trimmer in series with the bottom end of L2, the secondary winding on the coil former. As most of you will eventually be using some form of ex-radio tuning capacitor (with or without bandspread, see above), a single 25-pF trimmer, C4, and a parallel capacitor, C3, are designed into the circuit for the sake of convenience, and for quick testing.

Because of the very large gain variations produced by received signals, the collector voltage of the tuned oscillator in fact represents the demodulated signal. It is tapped via a capacitor, C9, and fed to T2, which acts as an audio pre-amplifier. Next comes a volume control, P2. An LM386, IC1, is used as the audio output stage. Although any output device will do here, I chose this IC because of its low cost, and I already

had four of them in my junk box! The LM386 has the usual Boucherot network at its output (here, C16-R11) to prevent oscillation. Test voltages measured on our prototype of the receiver are shown at various important junctions in the circuit diagram.

IN PRACTICE

The complete circuit is built on the custom designed printed circuit board shown in **Figure 2**. Construction of the receiver on this board is self explanatory as you only have to follow the parts list and the component overlay. Unfortunately the PCB is not available ready-made through our Readers Services.

The only component you have to make yourself is the combined inductor L1-L2. The components that make up the 10F1 inductor assembly (from Neosid) are illustrated in **Figure 3**. L1 consists of 15 close-wound turns of 0.1-mm dia. (SWG40) enamelled copper wire on the lower part of the former. Although the other winding, L2, is made with the same wire type, it differs from L1 in that it consists of two layers: the lower one has 40 turns, the upper one, 20. L2 is wound on the

upper part of the 10F1 former. As the copper wire is quite thin, it is also brittle, so work carefully. Don't forget to remove the enamel layer from the wire ends, this is best done by carefully sandpapering or scratching (with a sharp hobby knife) the last 5 mm or so, and then pretinning with your solder iron. Check the continuity of the inductors at the base pins of the former, using the PCB component mounting plan and the circuit diagrams as guidance. Also make sure none of the base pins comes into contact with the metal cap which is pushed over the former once this is in place on the circuit board. Before mounting the finished inductor onto the board, check its looks against those of our prototype, shown in **Figure 4**.

If you are unable to produce the PCB shown in **Figure 2**, there is an alternative: veroboard construction. The method I have used is a little different in the sense that I use the veroboard up-side-down! I lay the components on the tracks and cut away the unwanted copper. The component leads do not go through the board as is the norm, but actually sit on the tracks. This keeps all component leads to an absolute minimum length. The un-coppered side is then stuck (with super-glue) to a copper ground plane. In RF circuits it is important to keep stray capacitance to an absolute minimum. One way of achieving this is by placing the complete circuit on an earthed plane such as copper clad board. The leads of components must be as short as possible, if not non-existent, as these can act as part of a tuned circuit especially at high frequencies. Although not as critical in the frequencies we are using here, it is still good practice to cut component leads very short.

The 12 Volts is applied, and the aerial with the all important earth is also attached. If you are using a bandset



Back to Earth

Do not be tempted to use the mains earth, although good for what it is intended for in the household, it may not be the best for radio reception. Make an earth spike out of preferably copper, but almost any metal will do. Mine is made from an old copper pipe that I made into a point at one end for entering the garden, and a flat at the other end to which I drilled a small hole to fit a nut and bolt with a solder tag. The pipe is about ten inches long but this is not important¹, as any length will do depending how deep your garden goes. I soldered a length of good thick earth wire

and fed it through a hole in my shack wall (Shack is a radio amateur's shed), which was then attached to a box with a couple of 4-mm sockets. The total length of the wire is about two meters. The shorter the wire and the heavier the gauge, the better the earth will be. Always keep it damp, no problem on wet days but you will need to throw a bucket of water over it on drier spells... when the water board is not looking.

¹ Note that the author lives practically at sea level. A much longer earthing rod may be required depending on your location and the soil condition. Tech. Editor.

Figure 2. Copper track layout and component mounting plan of the PCB designed for the receiver (board not available ready-made). The large copper plane provides very good decoupling of RF signals where necessary, and so helps to keep the receiver stable.

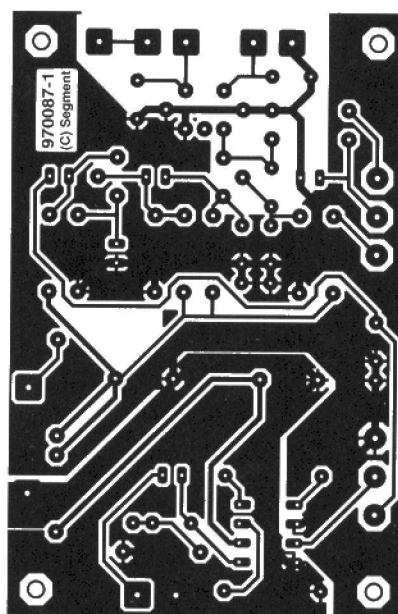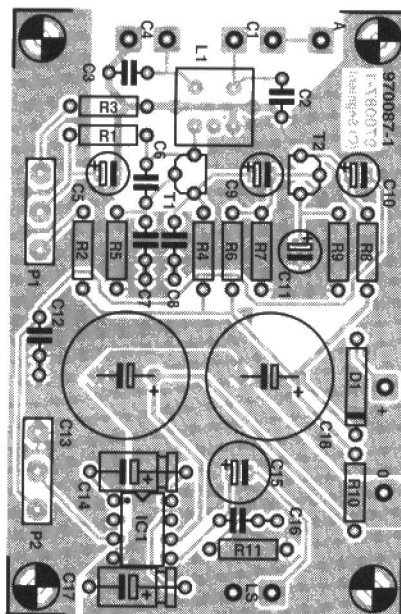

control as the main (coarse) tuning, then set this to about halfway (half mesh). The bandspread control is also set the same. If you have a good slow motion drive on the main tuning capacitor, then you will probably not need the bandspread capacitor (the bandspread capacitor is wired directly across the main tuning capacitor). Set the aerial tuning capacitor (here, trimmer C1) to half-mesh also.

If you have a signal generator or a grid dipper you can then align the coil to the middle of the band around 3.65 MHz, critical alignment being made with the coil and capacitor/s. Do not switch the receiver on. Couple the generator signal to the receiver input by means of a few turns of wire around the coil former. Set C4 to almost minimum capacitance, and peak the core for best reception of the

test signal. The signal level may be measured by connecting a 10:1 (<15 pF load) oscilloscope probe to the hot side of C4. Carefully and alternately adjust the core and C4 until the signal level peaks. At this setting, L1 and C2 are tuned exactly to the centre of the band.

If you have a short-wave receiver already, you can find where you are by comparison. If you have neither of these, don't worry, you'll soon find what you want by experimenting. Remember, though, that due to radio-wave propagation the 80-m band does not come alive until after sunset, and that reception is generally better in winter time. Set the reaction pot also to about halfway. With all the necessary items attached slowly adjust the pot until a slight oscillation is heard. Turn the main tuning control whilst keeping the reaction in the state of just oscillating. When a signal is detected, adjust the bandspread (fine tuning, if fitted), aerial tuning and reaction until the signal is a pleasure to listen to. Obviously you will have adjusted the volume control accordingly. A little practice and you will soon realise how well this little circuit performs. I am listening to some continental amateurs as I am typing this text. I live quite low down by the coast and have a moderate wire aerial.

IN CONCLUSION

Enjoy building this little receiver and have hours of fun tuning around the band. The important factors are stability and short component leads. The rest is just patience to start with in getting to know this receiver. This really should not take more than a few min-

COMPONENTS LIST

Resistors:

R1, R2, R4 = 10kΩ
R3, R8 = 470Ω
R5, R9 = 1kΩ
R6 = 33kΩ
R7 = 4kΩ
R10, R11 = 10Ω
P1 = 1kΩ linear
P2 = 10kΩ logarithmic

Capacitors:

C1, C4 = 25pF trimmer or tuning capacitor
C2 = 680pF
C3 = 33pF
C5, C9, C10, C11 = 10μF 63V
C6 = 470pF
C7 = 1nF
C8 = 47nF
C12 = 10nF
C13, C18 = 1000μF 16V radial
C14 = 4μF 16V
C15 = 100μF 16V
C16 = 100nF
C17 = 22μF 16V

Inductors:

L1 = Neosid 10F1 (brown dot on core)

Semiconductors:

D1 = 1N4001
T1 = BF224 or BF494
T2 = BC547B
IC1 = LM386

Miscellaneous:

LSP1 = 8 ohm 1 watt

utes. You may experiment with the number of turns of the coils, but keep to the same ratio. Happy tuning!

(970087-1)

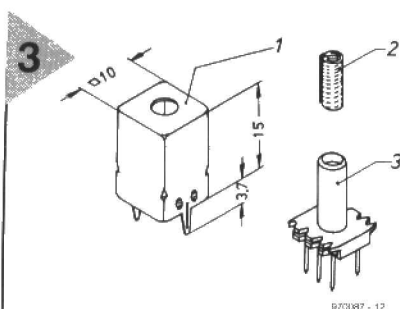


Figure 3. The components that make up the 10F1 assembly from Neosid. (1) screening can; (2) ferrite core; (3) coil former with base.

4


Figure 4. Close-up of the finished input band filter, L1-L2, fitted in the circuit. Do not apply too much heat while soldering the enamelled copper wire, as the 10F1 base is prone to soften a little and the pins will easily come loose. Also note that we've used a few drops of candle wax to secure the windings.





hygrometer

*with LED display and
switched output*

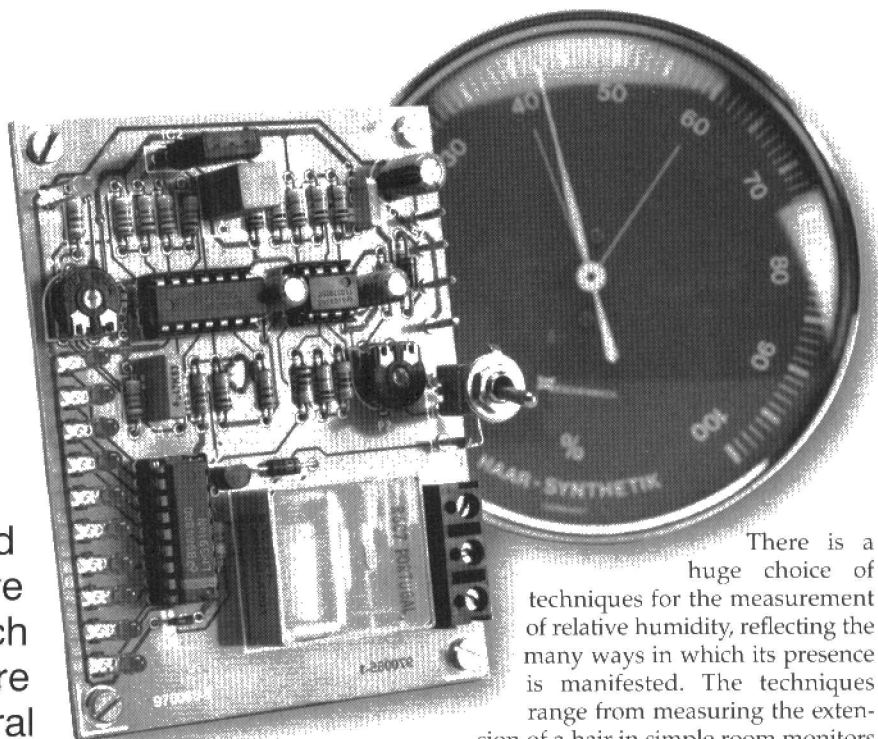

The measurement and control of the moisture content of gases, such as the atmosphere around us, is an integral part of many industries,

but is also of importance in the home and workshop. Although moisture, that is, water vapour, is not an ideal gas, for many hygrometry purposes it is sufficient to assume that it behaves ideally. In environmental applications the basic unit of moisture is relative humidity, which is the ratio in per cent of the actual vapour pressure in the atmosphere to the saturation vapour pressure of water at the same temperature. It is thus temperature dependent but independent of the atmospheric pressure.

There is a huge choice of techniques for the measurement of relative humidity, reflecting the many ways in which its presence is manifested. The techniques range from measuring the extension of a hair in simple room monitors to sophisticated electronic instruments.

The instrument proposed in this article is based on a special sensor of which a detailed description is given in the box further on in this article. It is especially intended for use indoors and has a range of 35–80 per cent RH (relative humidity). Its readout is made up of high efficiency light-emitting diodes (LEDs). Provision is made for driving an external fan or dehumidifier via an integral relay contact.

ELECTRICAL SENSORS

There are many substances whose electrical impedance changes with the surrounding moisture level. This change of impedance can be calibrated in terms of moisture concentration or relative humidity (RH).

Most of these electrical sensors consist of two electrodes separated by a material whose impedance changes in direct proportion to the relative humidity. The separating material may be a polymer, tantalum oxide, silicon oxide, lithium chloride mixed with plastic, or a host of others.

The sensor used in the present hygrometer is a Type NH-3 which may be considered a moisture-depen-

Design by H. Bonekamp

dent potential divider. When a stable alternating voltage is applied across the divider, a potential is produced at the junction of the two divider branches which is directly proportional to the ambient moisture concentration. This voltage is rectified and differentiated, after which it is used to drive a bar of LEDs via a suitable display driver. The associated electronics circuits are simple.

CIRCUIT DESCRIPTION

In the circuit diagram in Figure 1, the moisture-dependent sensor is IC₂, while the display LEDs are driven by IC₄. Rectification and differentiation of the sensor output is effected by IC_{3a-c}.

To ensure that the moisture-dependent potential divider in the sensor functions satisfactorily, it needs to be powered by an accurately defined, symmetrical alternating voltage. This is provided by rectangular-wave generator IC_{1a}. This is a comparator with a totem pole (single-ended) output, in which the conditions for oscillation are met by the positive feedback provided by R₃. The time-constant, τ , is equal to $R_4 \cdot C_2$. The rectangular wave output is symmetrical (square wave) and has a frequency of 1 kHz. Its level of 3 V_{p-p} is stable since the generator is powered by a reference voltage, U_{REF}, of 3 V.

Since there should be no direct current through the sensor, the output of the generator, IC_{1a}, is cou-

pled to the sensor, IC₂, via capacitor C₃.

The impedance of the sensor varies in direct proportion to the ambient relative humidity: from 2 k Ω at 90% RH to 10 M Ω at 30% RH. The consequent long time constants, and thus the sustained switching phenomena, are countered by resistor R₅ in parallel with the sensor.

A high dissipation in the sensor affects its linearity and the design therefore ensures that this remains below 1 mW over the entire measurement range.

The sensor output, taken from pin 2, is applied to op amp IC_{3b} via buffer IC_{3a}. The op amp not only raises the signal by $\times 2.7$, but, since it operates asymmetrically, also rectifies it (half-wave). Moreover, in this stage the reference level is shifted from U_{REF} to earth.

The pulsating direct voltage at the output of IC_{3b} is differentiated by network R₁₀-C₄, after which the signal is buffered by IC_{3c}, and then applied to the input of IC₄ via calibration control P₁.

Circuit IC₄ is an accurate potential divider containing ten comparators each of which can drive an LED directly. The IC is therefore able to display variations in the applied direct voltage on a bar of ten LEDs. Its pin 9 enables a choice to be made between dot and bar

Figure 1. The circuit of the hygrometer consists of a sensor, rectifier/differentiator, display driver, bar of LEDs, and power supply.



SENSOR

In the prototype, the moisture-dependent sensor is a Type NH3 from Figaro, but other suitable models may, of course, be used.

Basically, the sensor consists of a combination of a moisture absorbing material and a thermistor. The Type NH-3 is an ultra-linear model which uses two such combinations. The sensor proper is embedded in porous ceramic, which ensures stability as well as a long life. The electrodes are made from ruthenium oxide, RuO₂, which is also a porous material.

Both the sensor and thermistor are mounted on a ceramic substrate.

In the equivalent circuit shown, the resistors forming the potential divider are marked R_{H1} and R_{H2}, and the thermistors, TH₁ and TH₂. The applied alternating voltage is V₀, while the sensor output is V₁.

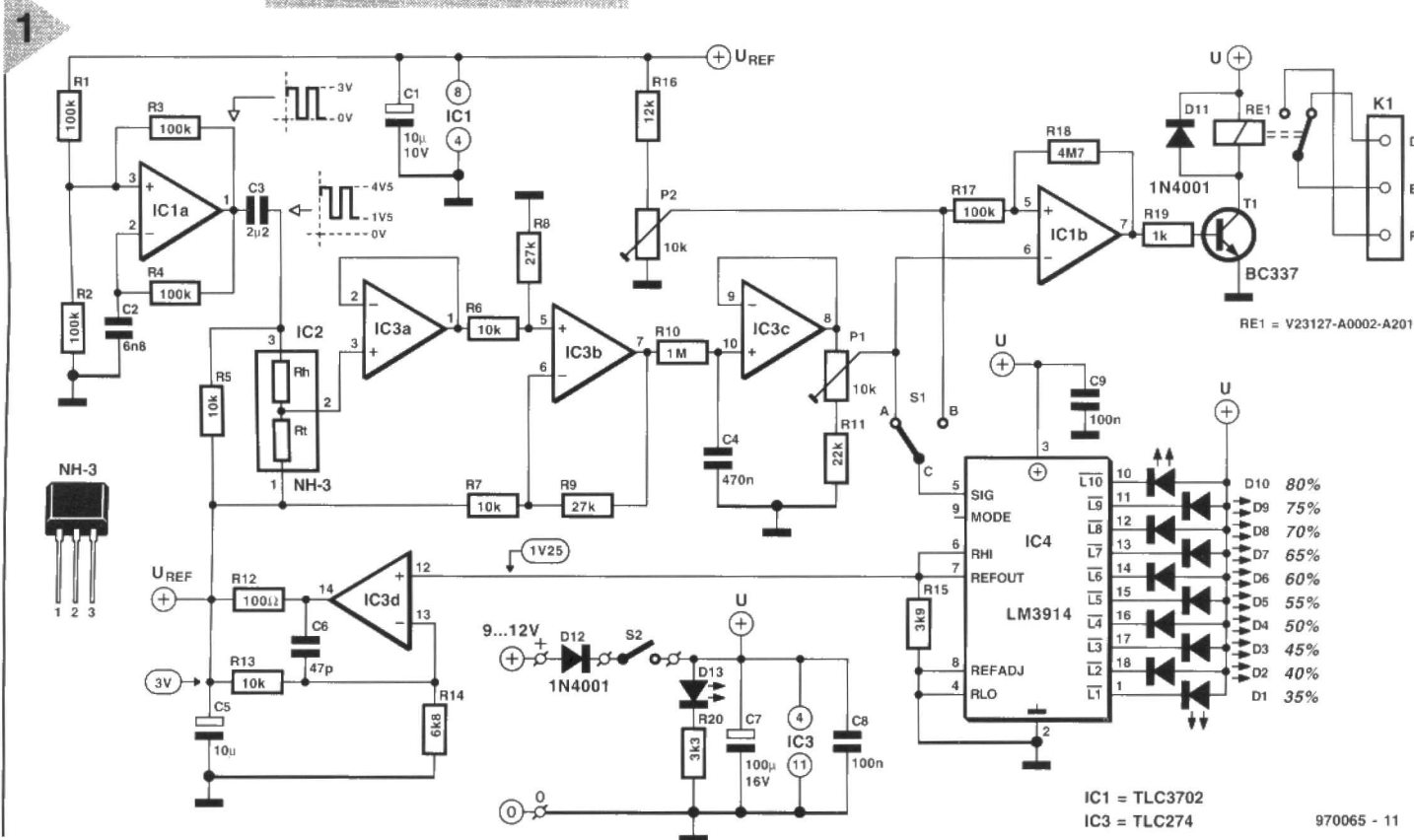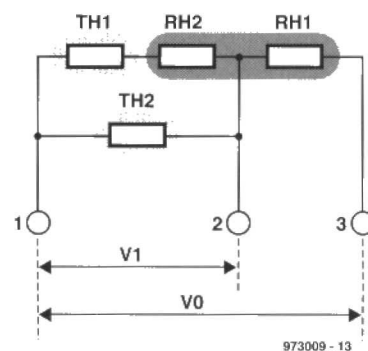

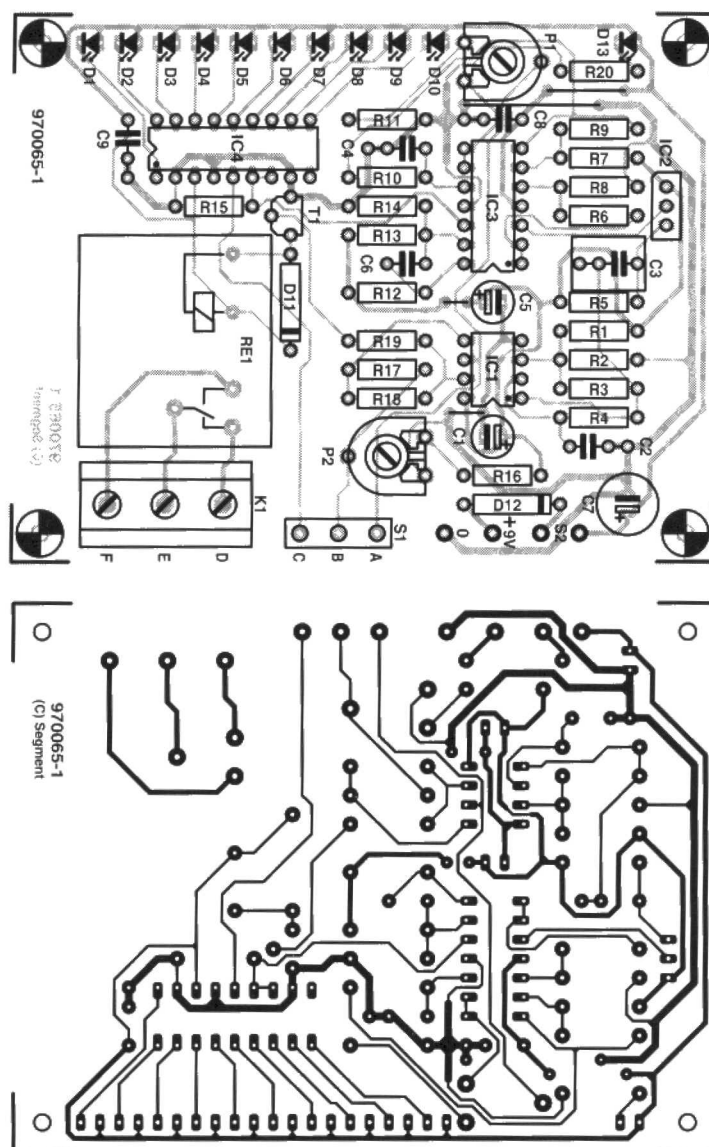


Figure 2. The printed-circuit board for the hygrometer holds all components.

modes (the prototype uses the dot mode).

Normally, the accurate reference voltage, U_{REF} , required for powering the sensor is obtained by a fairly complex arrangement. In the present circuit, it is, however, provided by display driver IC₄ and is available for external applications at pin 7. It is too low for the sensor, and is therefore raised by IC_{3d} to 3 V. The output of the amplifier is compensated for capacitive loads by R₁₂ and C₆.

The switched output is driven by comparator IC_{1b}, which functions as a level detector. The comparator is provided with an hysteresis of about 4 per cent by R₁₇ and R₁₈ and drives relay Re₁ via transistor T₁. The change-over contact of the relay is linked to the outside world via connector K₁.

The reference voltage applied to the non-inverting (+ve) input of IC_{1b} is derived from U_{REF} and set to the required level with P₂. This control thus sets the degree of relative humidity at which the relay is actuated.

The level setting is simplified by switch S₁. When this is set to position B, the sensor signal is interrupted, and in its stead the reference voltage is displayed on the bar of LEDs via IC₄.

CONSTRUCTION

Even less-experienced constructors will find the assembly of the hygrometer on the printed-circuit board shown in Figure 2 a fairly easy affair, since there is no additional wiring and all components are housed on the board. As usual, mind the polarity of the diodes and electrolytic capacitors and fit the ICs in suitable sockets, although this is not strictly necessary.

The assembly may be fitted in any of a variety of suitable ABS (*acrylonitrile-butadiene-styrene*) cases. The really important thing is that the sensor is fully exposed to the ambient atmosphere, and this requires the drilling of a number of not too small holes in the enclosure.

Parts list

Resistors:

R₁–R₄, R₁₇ = 100 kΩ
 R₅–R₇, R₁₃ = 10 kΩ
 R₈, R₉ = 27 kΩ
 R₆, R₉ = 27 kΩ
 R₁₀ = 1 MΩ
 R₁₁ = 22 kΩ
 R₁₂ = 100 Ω
 R₁₄ = 6.8 kΩ
 R₁₅ = 3.9 kΩ
 R₁₆ = 12 kΩ
 R₁₈ = 4.7 MΩ
 R₁₉ = 1 kΩ
 R₂₀ = 3.3 kΩ
 P₁, P₂ = 10 kΩ preset

Capacitors:

C₁ = 10 μF, 10 V, radial electrolytic
 C₂ = 0.068 μF, metallized polyester (MKT)
 C₃ = 2.2 μF, metallized polyester (MKT)
 C₄ = 0.047 μF, metallized polyester (MKT)
 C₅ = 10 μF, 10 V, radial electrolytic
 C₆ = 47 pF, ceramic
 C₇ = 100 μF, 16 V, radial electrolytic
 C₈, C₉ = 0.1 μF, high stability

Semiconductors:

D₁–D₁₀ = LED, red, high efficiency
 D₁₁, D₁₂ = 1N4001
 D₁₃ = LED, green, high efficiency
 T₁ = BC337

Integrated circuits:

IC₁ = TLC3702CP
 IC₂ = NH-3 (Figaro) or equivalent
 IC₃ = TLC274CN
 IC₄ = LM3914N

Miscellaneous:

S₁ = change-over switch
 S₂ = single-pole on/off switch (or push-button type – see text)
 Re₁ = relay, 9–12 V, single change-over contact
 K₁ = 3-way PCB terminal block, pitch 7.5 mm
 PCB Order no. 970065 (see Readers Services towards the end of this issue)

There are two ways of obtaining the requisite power supply. When the instrument is used in a more or less permanent position, it is best to use a standard mains adaptor with an output of 9–12 V. Since the hygrometer draws a current of only 50 mA, such an adaptor need not be a heavy duty version.

For mobile use, it is, of course, necessary to use a 9 V battery instead of a mains adaptor. It is then, however, not possible to use the switched output. Transistor T₁, the relay, and most of the components associated with IC_{1b}, but not R₁₈, may then be omitted. Resistor R₁₈ is necessary for the stability of the op amp.

Ignoring the relay, the circuit draws a current of about 14 mA. Although

this is modest, do not forget to switch off the supply when the meter is not in use, otherwise the battery will soon be discharged. It is, therefore, better, if the meter is always used in mobile form, to replace S_2 by a spring-loaded (push button) on/off switch.

CALIBRATION

If the hygrometer is used (almost) exclusively to switch on a fan or dehumidifier in spaces suffering from damp conditions, the calibration is not terribly important: it then suffices to set P_1 to its centre position.

Where greater accuracy is desired, the instrument must be calibrated (by adjusting P_1) with the aid of a refer-

ence hygrometer.

Performance of the prototype compared reasonably well with that of some commercial hygrometers, at least over the range 40–80% RH. This is in accord with the manufacturer's sensitivity curve shown in Figure 3. It will be noted that the curve has a sharp(ish) bend below about 40% RH, but that its linearity over the remainder of the range is good.

The degree of dampness at which the ventilator or dehumidifier is switched on is set with P_2 . This is best done by setting switch S_1 briefly to position B to display the reference voltage on the bar of LEDs.

[97/065]


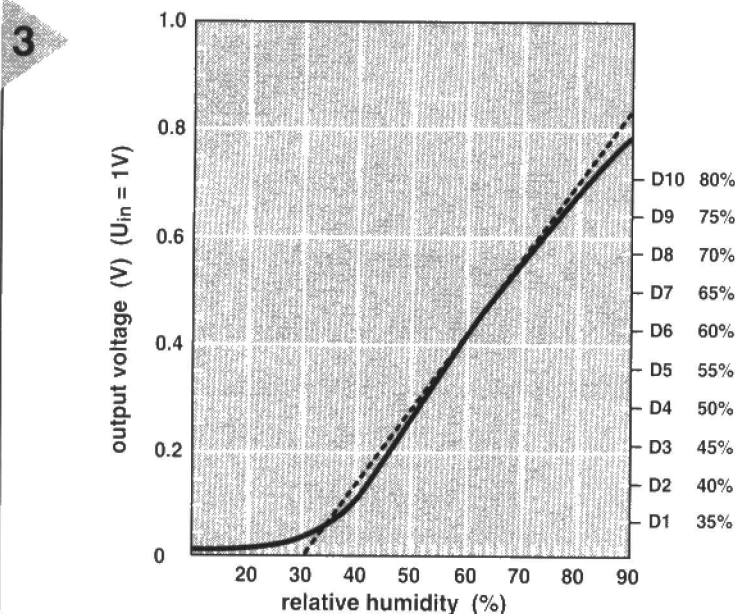


Figure 3. The sensitivity curve of the sensor is linear from 40% RH to 80% RH.

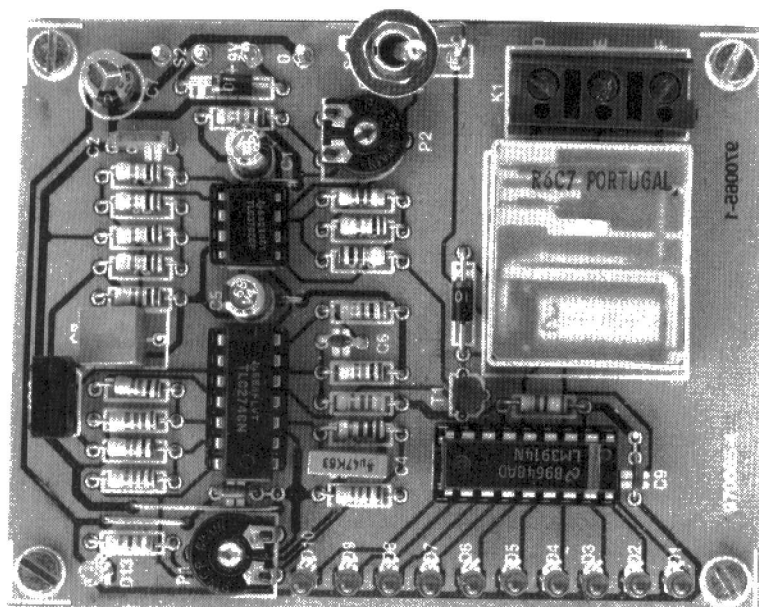

Another fine mess

About half a year ago my wife and I moved to a larger house. Detached, just 8 years old, and in a charming hamlet not too far from our respective work locations. Don't get me wrong, we are very satisfied with our choice (which we were able to make after half a year's intensive house-hunting), and the house is reasonably well built using good quality materials. It has every luxury I personally want (and that's not a lot), and it looks splendid after our most recent undertaking, all-round paint work!

To get to the point, the only trouble with the house is electrical. The previous owner claimed he had 'done a lot himself' to finish the construction of the house. Unfortunately, although reasonably versed in plumbing and other 'coarser' trades like masonry (the results of which far exceed my own capacities), he deserves a very low grade for electrical installation work. While the larger part of the electrical system has been installed by qualified people, the previous owner must have made the odd change and addition here and there after the electricity board inspector approved the system and walked off about 8 years ago.

I now have a collection of A4 sheets on which I have attempted to unravel various attempts at layman's electrical installation. For example, I found that the connection of the central heating boiler to the thermostat fitted in our living room used half a dozen wires of assorted colours and a total length of more than 100 m, travelling up and down the house, either unprotected or through various pieces of plastic conduit. As I opened the old dial-type Honeywell thermostat, I was perplexed. The DIY CH control system was of a fearsome complexity, using a special 24-V transformer, a relay, a hidden switch and a very noisy valve (controlled by a mains extension cable running from the attic down to the scullery) to control the floor heating, and, to cap it all, an antediluvian switching clock which enabled the CH boiler from 7 am to 11 pm, with its vessel thermostat set to 75°C. Although all these components are of industrial quality (I wonder where he got them from), they are superfluous in my view. I removed all the wiring, the relay and the transformer, and installed a modern, intelligent, room thermostat which switches the gas valve using the 24-V supply also fitted inside the CH boiler. As far as I know, this is a standard, safe and approved connection based on just two medium-duty wires to the room thermostat. After a learning period of about one week in spring time, the heating system worked fine, and my efforts have been rewarded with a much reduced gas bill.

A few days ago I decided to install an infra-red (PID) controlled lamp in the front porch. No problem, I thought, until I opened the double switch in the hall and saw many more wires than I had expected, some just entering the switch case and leaving it again without any connection whatsoever. No assorted colours this time: just one: green!

Jan Builing




stereo microphone amplifier

with balanced inputs and phantom power supply

The magnification of very weak audio-frequency signals is and remains a precarious affair. That is why a microphone amplifier good enough for professional applications must have balanced inputs and indisputably good specifications. Foremost, of course, is the faithful transducing of sound.

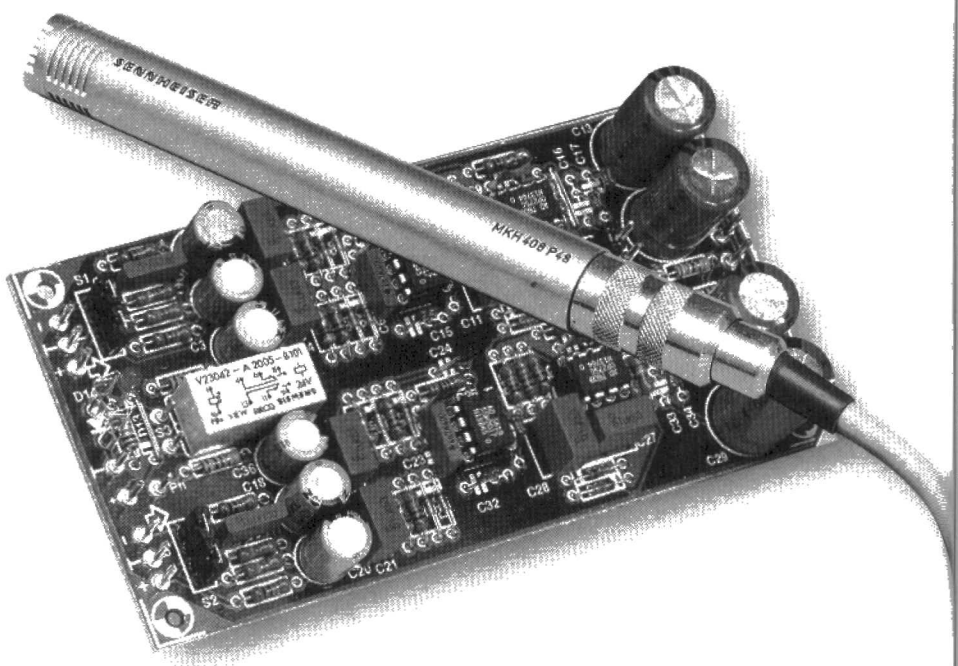Although this is a subjective aspect, it is confidently expected that the design of the amplifier described here will satisfy even professional audio engineers and technicians. It is a stereo model with integral phantom power supply for electret microphones.



INTRODUCTION

There are not all that many good methods to amplify the very small a.f. output signals of a microphone without affecting the quality of the input sound. One of the best is undoubtedly that in which a balanced instrument amplifier, discrete or integrated, is used.

Today, the accent in design is on integrated circuits, ICs, rather than on discrete transistors. One of the many a.f. ICs in the gamut of Analog Devices is the SSM2017, which is eminently suitable for use in a balanced microphone amplifier. This operational amplifier has a small noise factor and low total harmonic distortion, combined with a large bandwidth and high slew rate. Also, its amplification may be set within wide limits.

CIRCUIT DESCRIPTION

From the foregoing, it is clear that basing the design of the microphone amplifier on an SSM2017 is a sound decision. The circuit diagram in Fig-

ure 1 may look extensive, but it should be borne in mind that it concerns a stereo circuit. This means that there are two of every device and component with the exception of those in the power supply. The following description will be limited to the left-hand channel.

The microphone is connected to the balanced input amplifier, IC₁, via terminals L+ and L-. The facility for short-circuiting R₁ and R₂ is provided for cases in which the circuit is to be used as a line amplifier. The switches are then open to provide an attenuation of 10 dB. When the circuit is used as microphone amplifier, the resistors are short-circuited. So, if use as a line amplifier is not envisaged, the switches and R₁, R₂ may be replaced by a wire bridge.

The supply voltage needed by electret microphones is provided via a phantom line. This means that the signal lines are used for carrying the supply voltage, which is, of course, not applied to the amplifier input. The volt-

Features


Bandwidth

> 74 dB (BW 22 kHz linear)
< 0.03% (BW 80 kHz)

120 dB
95 dB
83 dB

> 60 kHz (source 50 Ω)
> 37 kHz (source 600 Ω)

Figure 1. Circuit diagram of the stereo microphone amplifier, which is based on an SSM2017 operational amplifier from Analog Devices.

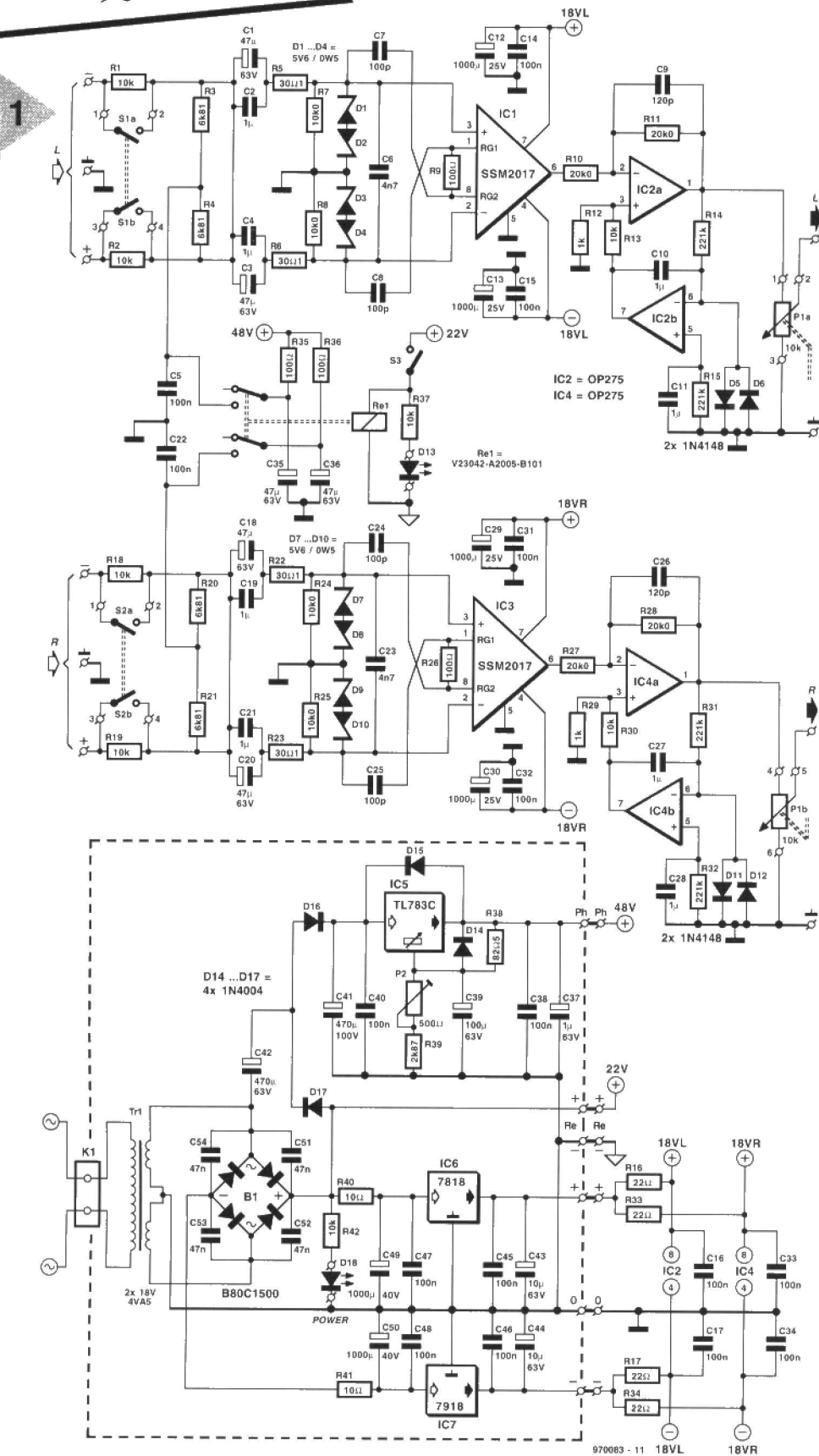

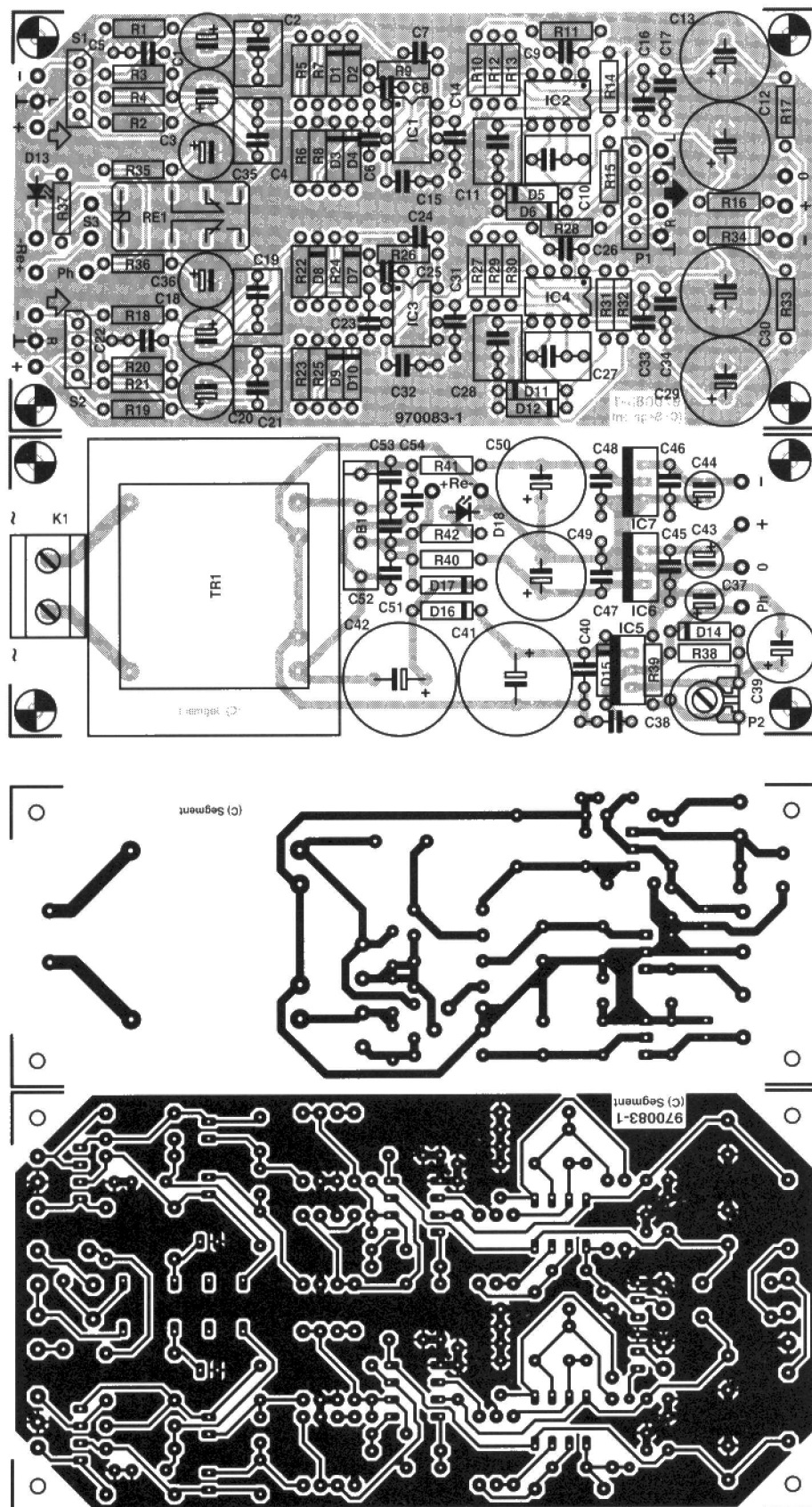


Figure 2. The printed-circuit board is in two parts to enable the amplifier and power sections to be kept isolated.

Parts list

Resistors:

R₁, R₂, R₇, R₈, R₁₃, R₁₈, R₁₉, R₂₄, R₂₅, R₃₀ = 10.00 kΩ, 1%
 R₃, R₄, R₂₀, R₂₁ = 6.81 kΩ, 1%
 R₅, R₆, R₂₂, R₂₃ = 30.10 Ω, 1%
 R₉, R₂₆ = 100 Ω, 1%
 R₁₀, R₁₁, R₂₇, R₂₈ = 20.00 kΩ, 1%
 R₁₂, R₂₉ = 1.00 kΩ, 1%
 R₁₄, R₁₅, R₃₁, R₃₂ = 221 kΩ, 1%
 R₁₆, R₁₇, R₃₃, R₃₄ = 22 Ω
 R₃₅, R₃₆ = 100 Ω
 R₃₇, R₄₂ = 10 kΩ
 R₃₈ = 82.50 Ω, 1%
 R₃₉ = 2.87 kΩ, 1%
 R₄₀, R₄₁ = 10 Ω
 P₁ = 10 kΩ, log, stereo potentiometer
 P₂ = 500 Ω preset potentiometer

Capacitors:

C₁, C₃, C₁₈, C₂₀, C₃₅, C₃₆ = 47 μF, 63 V, radial
 C₂, C₄, C₁₀, C₁₁, C₁₉, C₂₁, C₂₇, C₂₈ = 1 μF, metallized polyester (MKT), pitch 5 mm or 7.5 mm
 C₅, C₂₂ = 0.1 μF
 C₆, C₂₃ = 0.0047 μF
 C₇, C₈, C₂₄, C₂₅ = 0.001 μF
 C₉, C₂₆ = 0.12 μF
 C₁₂, C₁₃, C₂₉, C₃₀ = 1000 μF, 25 V, radial
 C₁₄-C₁₇, C₃₁-C₃₄, C₃₈, C₄₅-C₄₈ = 0.1 μF, ceramic
 C₃₇ = 1 μF, 63 V, radial
 C₃₉ = 100 μF, 63 V, radial
 C₄₀ = 0.1 μF, metallized polyester (MKT), 100 V
 C₄₁ = 470 μF, 100 V, radial
 C₄₂ = 470 μF, 63 V, radial
 C₄₃, C₄₄ = 10 μF, 63 V, radial
 C₄₉, C₅₀ = 1000 μF, 40 V, radial
 C₅₁-C₅₄ = 0.047 μF, ceramic

Semiconductors:

D₁-D₄, D₇-D₁₀ = zener 5.6 V, 500 mW
 D₅, D₆, D₁₁, D₁₂ = 1N4148
 D₁₃ = LED, high efficiency, red
 D₁₄-D₁₇ = 1N4004
 D₁₈ = LED, high efficiency, green

Integrated circuits:

IC₁, IC₃ = SSM2017 (Analog Devices)
 IC₂, IC₄ = OP275G (Analog Devices)
 IC₅ = TL783C (Texas Instruments)
 IC₆ = 7818
 IC₇ = 7918

Miscellaneous:

K₁ = two-pin terminal block, pitch 7.5 mm
 S₁, S₂ = double-pole on switch (or wire bridge - see text)
 S₃ = single-pole on switch
 B₁ = B80C1500 bridge rectifier
 Re₁ = 22 V relay, 2 contacts
 Tr₁ = mains transformer, 2×18 V secondaries, 4.5 VA
 PCB Order no 970083-1 (see Readers services elsewhere in this issue)

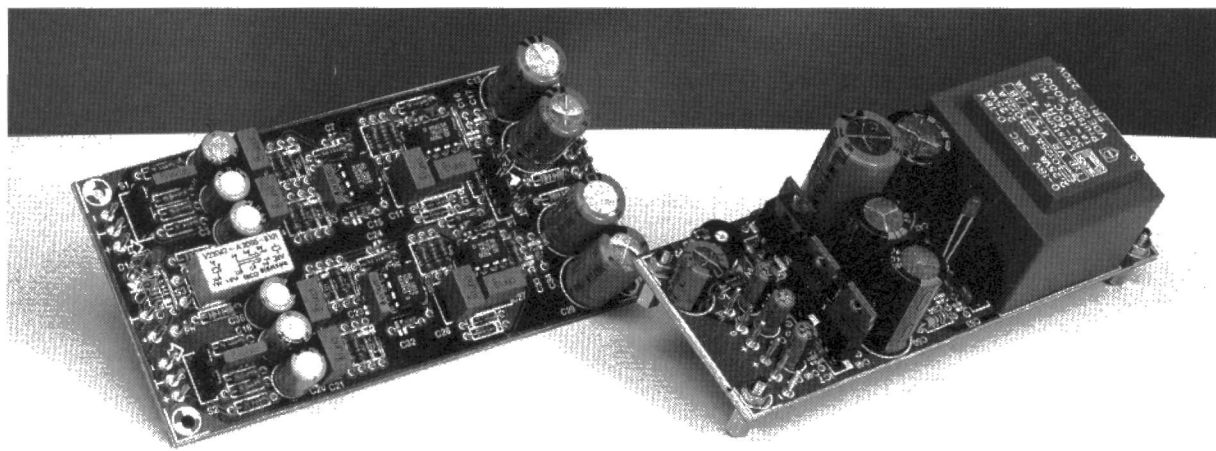


Figure 3. In the prototype, S_1 , S_2 and P_1 have been omitted deliberately – see text.

age is 48 V and is linked to the input lines via relay Re_1 , which is controlled by S_3 . Network R_{35} - C_{35} provides additional smoothing of the supply line. The supply voltage is applied to the balanced microphone lines via potential divider R_3 - R_4 . RF decoupling is provided by C_5 . The lighting of diode D_{13} indicates that the supply is on.

Capacitors C_1 and C_3 prevent any direct voltages from reaching the inputs of IC_1 . They are bypassed for r.f. by C_2 and C_4 .

Resistors R_5 and R_6 , in conjunction with zener diodes D_1 - D_4 , suppress any peaks on the phantom supply lines that may be caused by the operation of S_3 .

Resistors R_7 and R_8 form the input load of IC_1 . As the pass-band of this IC is wide, it needs to be narrowed to reduce noise and distortion and also to largely suppress the effect of any r.f. radiation that may be present. The bandwidth is reduced by capacitors C_6 - C_8 , which must not be ceramic types.

One of the excellent features of the SSM2017 is that its voltage amplification is easily varied without affecting its input impedance and bandwidth. The amplification, α , is determined by the value of R_9 between pins 1 and 8. The relationship between these two quantities is given by

$$\alpha = (10^4/R_9) + 1.$$

With the value of 100 Ω specified for R_9 in the present circuit, this gives an amplification of $\times 100$ (40 dB). For an amplification of $\times 31$ (30 dB), the value of R_9 is 332 Ω , and for $\times 316$ (50 dB), it is 31.6 Ω .

The output of IC_1 is applied to volume control P_{1A} via buffer amplifier IC_{2A} . This buffer is a special type of op amp, an OP275, which functions on the Butler amplifier principle. In this,

a combination of bipolar and junction field-effect transistors is used to provide the low noise of the first and the speed and sound quality of the second. This arrangement results in a device with impressive specifications as regards noise contribution, distortion and slew rate.

The amplification of the buffer is set to unity with R_{10} and R_{11} .

The bandwidth of the buffer is limited by C_9 .

To eliminate the fairly high offset (that is, imbalance) voltage produced by the SSM2017 (which may be as high as 200 mV, depending on the amplification), and since an electrolytic capacitor at the output was considered undesirable, integrator IC_{2B} is used. This op amp compares the potential at pin 1 of the buffer amplifier with that at its inverting input (pin 6). On the basis of this comparison, the integrator adjusts the input to the buffer in such a way that the overall offset voltage at the output is smaller than 1 mV at all times. Diodes D_5 and D_6 protect the integrator against high peak voltages.

POWER SUPPLY

The circuit needs three different supply voltages: a symmetrical one of ± 18 V for IC_1 - IC_4 ; a single one of 22 V for the relay; and a single one of 48 V for the microphone(s).

The ± 18 V is provided by two voltage regulators, IC_6 and IC_7 . The supply lines to the various ICs are bypassed for any noise and interference on the mains supply by resistors R_{16} and R_{17} and capacitors C_{12} - C_{17} (or R_{33} and R_{34} , and C_{29} - C_{34} in case of the right-hand channel).

The supply line for the relay is taken directly from the secondaries of the mains transformer since this need not be smoothed or regulated. Its level of 22 V is sufficient to drive the relay reliably.

Since the output of the mains transformer is not sufficient for directly generating the 48 V line for the microphone(s), a cascade network,

D_{16} - D_{17} - C_{41} - C_{42} is used to boost the voltage across the bridge rectifier to about 70 V (open-circuit). This is reduced to +48 V by the combination of regulator IC_5 and preset P_2 .

Diode D_{18} functions as on/off indicator.

CONSTRUCTION

It is obvious that in view of the very low a.f. input signal levels it is desirable to isolate the amplifier from the power supply, and this is why the printed-circuit board in Figure 2 consists of two parts that should be separated before any construction work is commenced. In the final assembly, the two boards should be kept apart by at least 20 cm (8 in).

The construction itself is fairly straightforward, but a few points need to be borne in mind. Switches S_1 and S_2 , if used, may be connected via 4-pin SIL headers.

In the same way, volume control P_1 may be connected via a 6-pin SIL header. Again, not everyone may deem this control necessary. When the amplification, and therefore the value of R_9 (and R_{26} in the right-hand channel), has been determined, the control is not really required, since the volume is set on the mixer panel or power amplifier. To enhance the signal quality it is then better to omit P_1 and, to protect the outputs, connect a 100 Ω resistor between pins 1 and 2 and 4 and 5 of the SIL connector.


It is advisable to house the power supply section in a well-insulated plastic (Acrylonitrile-Butadiene-Styrene – ABS) case.

The mains cable should be provided with a strain-relief.

The amplifier section is best housed in a metal case. The case should be connected to one of the earth connections on the amplifier board.

Finally, to keep any induced noise and interference to an absolute minimum, intertwine the three wires of the ± 18 V line and earth, and the two wires of the +48 V line and earth.

[970083]

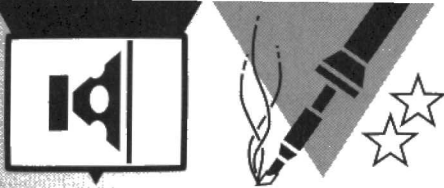

video copy processor

For obvious reasons, the rights owners of Hollywood 'blockbusters' and other films released on video cassettes are doing everything they can to prevent financial losses due to unauthorised copying of their products. Most of these (huge) companies, including Disney, employ an anti-copy process called Macrovision™. In this article we will endeavour to unravel the operation of this technology, as well as describe a pretty intelligent processor* which defeats the pulses and

other purposely introduced interference that prevents VCR-to-VCR copying of Macrovision™-protected VHS/PAL video tapes.



main features

- removes copy interference signals from picture syncs on prerecorded video cassette tapes
- enables legal copying (VCR back-to-back for backup purposes only)
- enhances picture quality in playback mode
- future-proof thanks to programmable EPLD
- low component count
- drop-in unit with SCART or Cinch connectors for easy connection
- designed for VHS/PAL VCRs

According to Macrovision Corp., their video cassette anticopy process is the most effective and widely used technology for preventing 'back-to-back' copying of videos using two VCRs. The technology, they say, has been applied to over 1.5 billion video cassettes worldwide, and is used by virtually every major Hollywood

* The Editors expressly dissociate from any illegal use of this circuit when the copyright vested in video cassettes is violated by removing the prerecorded Macrovision components. If you are the rightful owner of a prerecorded video tape, you are entitled to make one copy of it for backup purposes only. Macrovision™ is a registered trademark of the Macrovision Corporation, Sunnyvale, CA.

Design by W. Foede

studio, as well as by over 1,500 producers of special interest, corporate and educational programming.

Macrovision™ copy protection is available through 100 licensed duplicators throughout the world, including 40 licensed duplicators in the US and Canada.

Macrovision™ is applied to VHS tapes only, and seems to be more common in the US than in Europe. One of the best known videos protected by the system is the UK version of Disney's *Pocahontas*. Although the basic technology is the same, there exist slightly different NTSC and PAL versions of the system. The processor described in this article was designed for use with VHS/PAL tapes only. It has not been tested with VHS/NTSC tapes.

Like many other copy protection schemes and video encryption systems, Macrovision has been subject to a number of revisions aimed to keep the system compatible with evolving technology, in particular, of the video cassette recorder (VCR). Since an early (and very famous) publication in this magazine¹, the system has been improved considerably. The present processor has been designed to reflect all major changes made to the system up to the time of writing this article (August 1997).

WHAT HAPPENS?

Suppose you copy a Macrovision protected tape to a second VCR. Because you are using a good quality tape in the recording VCR, and a fully-wired SCART-to-SCART link between the two machines, you expect the copy to be of reasonable quality. The disappointment comes when you play back the copy: the picture is useless because it is unstable. In some cases, there is colour flickering, or even a virtually dark picture. The sound may also disappear because the TV set detects an unintelligible picture and promptly mutes the audio circuitry. The Macrovision Corp. describes the effect as: 'copies made on most consumer VCRs are degraded to the extent they no longer have any entertainment value'. Neatly put, but obviously forgetting about the fun some electronics enthusiasts may have in defeating the system.

How is it possible that the TV set is not bothered by the Macrovision interference, and the recording VCR goes haywire? The answer is relatively simple. A TV set has a picture synchronisation circuit that employs a kind of flywheel to prevent small irregularities in the received signal upsetting the picture stability. Well, the purposely introduced Macrovision interference

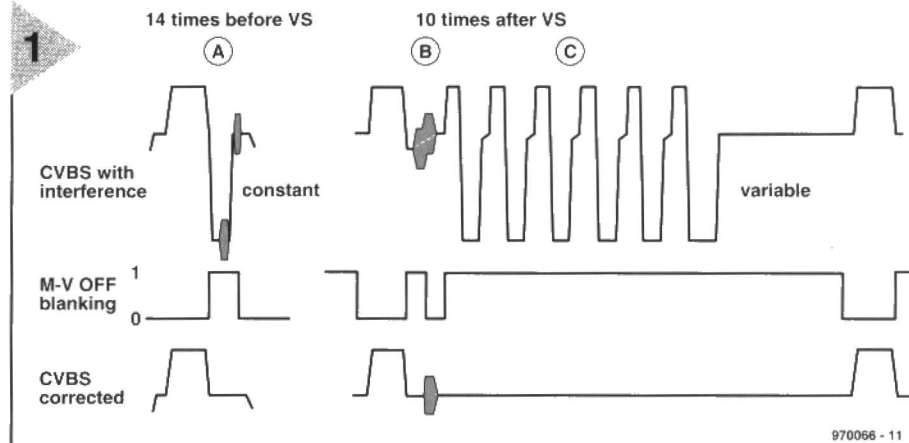


Figure 1. These drawings show the three types of interference (A, B and C) recorded on Macrovision-protected video tapes in order to make tape copying a waste of time. The Video Copy Processor described in this article detects all three types of interference, and kills it with the aid of a magic blanking pulse called M-V OFF. The drawings apply to VHS/PAL only.

(more about it further on) is interpreted as a minor disturbance which most (but not all) TV sets have no problem in overcoming. The interference is definitely there, however. If you happen to have an older TV set available, try this: reduce the vertical picture height, or adjust the vertical sync so that the picture starts to roll slowly. With some luck, you may be able to see the Macrovision signals as bright vertical stripes near the top or bottom of the picture.

The recording signal circuitry in a VCR does not have a 'flywheel' function like the one implemented in a TV set. This function is not required and not appropriate because the recording method is based on FM (frequency modulation). All VCRs do, however, have an AGC (automatic gain control) whose operation is totally messed up by the interference bursts and other spurious pulses introduced by the Macrovision signal. In fact, the interference makes the VCR think that the picture is alternately far too bright and far too dark. In response to this fake information, the AGC reduces the video gain to virtually zero, which results in a darkened picture, and then pumps it again. The speed of the effect is such that the picture is 'murky' and unstable.

WHAT HAPPENS? (GETS TECHNICAL)

For the following discussion it is assumed that you have a basic knowledge of the structure of a composite video signal.

The types of copy interference signal found on the latest pre-recorded video cassettes are shown in Figure 1. The basic thought is the same in all cases. All video recorders use AGC and black-level clamping for their recording circuits. These functions have their timing determined by the front edge of the line sync pulse (HS), and they start working on the rear porch (which starts well before the colour burst).

Interference type A

In a 'clean' signal, the instantaneous level of the rear porch is taken to represent the 'black' reference. Because it is not dependent on the picture (video) contents of the line, the level difference between the bottom of the sync pulse and the black level is an indication of the average video signal level. If the rear porch is pulled to the extreme white level as illustrated in Figure 1 (interference A), the process of establishing the video signal level is disturbed because a very large video signal is expected. As a result, the video gain is reduced to minimum. Because TV sets do not have a comparable gain control circuit in the video amplifier, the actual level is not reduced. None the less, the drive margin is changed considerably as a result of the 'fake' clamping level. As a result, the picture in the affected range becomes darker. A 'peak-white' burst (interference type A) is purposely inserted 14 times before each vertical sync pulse. The result is interference near the bottom of the picture.

The Video Copy Processor to be described further on detects the peak-white burst, and removes it from the rear porch.

Interference type B and C

As opposed to interference type A, types B and C are marked by levels which are varied periodically. This specific feature of the Macrovision system causes some parts of the picture to remain just about recognisable. The main interference is 'C' in the blanking period after the raster sync pulse, where the VideoText information nor-

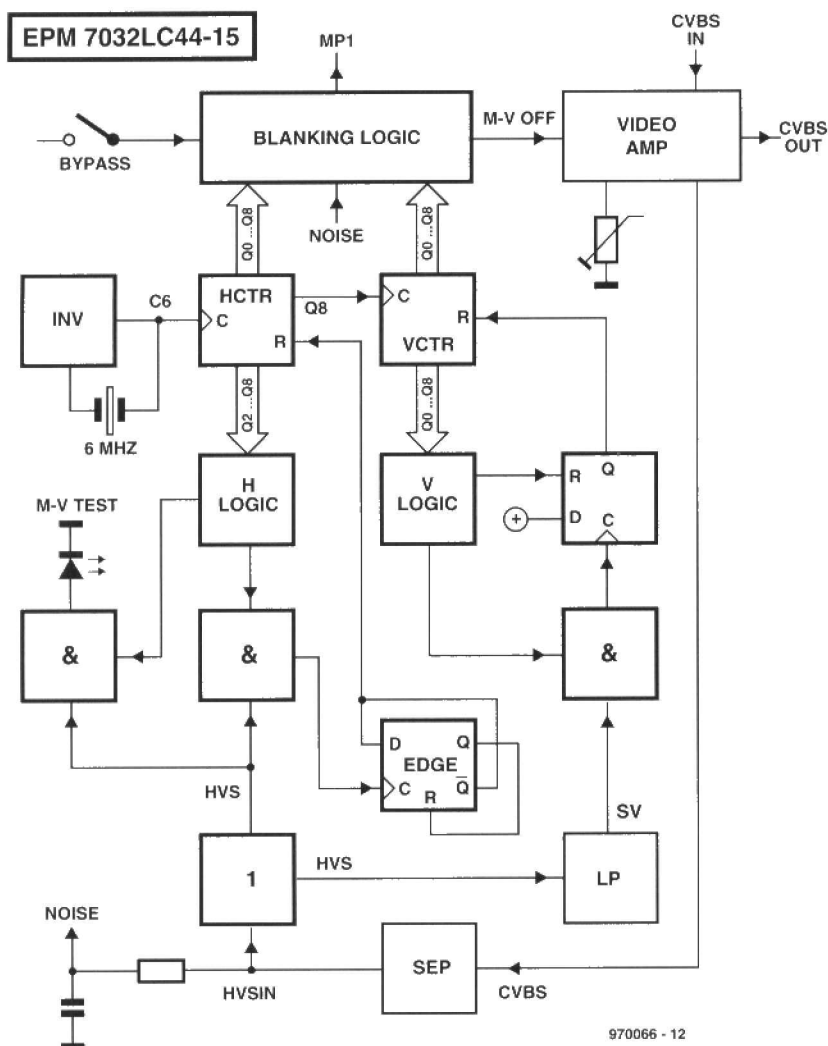


Figure 2. Combined block diagram of the circuit and the logic stashed away in the EPLD7032 chip.

mally resides. By inserting six new line sync pulses and six 'whitened' black references per line, the operation of the AGC circuits is totally disrupted, causing a muddled picture to be recorded: no brightness, no synchronisation! Because the muting circuit is activated, the sound channel with the film also disappears. The interference of type B is accurately matched to type C, so that TV sets show quasi-constant brightness in the upper range of the picture.

Older decoders remove the 'C' interference only, and forget about the 'A' and 'B' components. If only 'B' remains active, there will be a distinct flickering (rapid brightness variations) in the upper picture range. So, both have to be eliminated. Depending on the circuitry used in the TV set, interference type C may cause annoying horizontal picture tearing in the upper picture range when the tape is played back.

The present copy processor removes all three interference types from the composite video signal (CVBS) with the aid of its M-V OFF (Macrovision-Off) signal.

Macrovision on the Internet

The Internet is a great source for further information on Macrovision. It's all there: technical, commercial, hearsay, hacker info, and totally uninformed stuff.

First of all, we should, of course, mention the site run by the Makers of the System. Surprise, surprise, this may be found at <http://www.macrovision.com>.

If you would like to participate in discussions about video-related subjects like the Macrovision anti-copy system, sub-

scribe to the newsgroup *rec.video*. If you are new to this kind of communication, be sure to download, print and read the newsgroup's FAQ (frequently asked questions) before you start posting messages.

A separate, reasonably well informed FAQ (currently version 1.1) on Macrovision has been posted by Antti Paarlahti at <http://www.cs.tut.fi>. The particular strength of this FAQ lies in the sections which explain the operation of the Macrovision system in a technical as well as in a non-technical way. Interestingly, a number of technical references draw heavily on the 1988 Elektor Electronics Macrovision decoder/blanker.

CIRCUIT DESCRIPTION

The heart of the circuit is an EPLD device type EPM7032 from Altera. This 'black box' contains a large number of digital functions which have been programmed into the chip. The IC is available ready-programmed from the Publishers (in combination with the PCB), or from kit suppliers. The main modules which are available in the EPLD, and their interaction, are shown in Figure 2. Mind you, not all of the blocks you see in the diagram are hidden inside the EPLD; some are external, tangible and of 100%-analogue design. Hence, our discussion of the operation of the circuit will cross-refer between the EPLD innards and the circuit diagram in Figure 3. An EPLD device was chosen here to reduce the component count and to defeat future changes to the Macrovision system (if and when they occur), simply by modifying the internal design of the chip.

Normally, an audio/video (AV) output supplies a positive CVBS (colour-video-blanking-synchronisation) signal with a level of about $1 V_{pp}$ into 75Ω . So it is necessary for the video processor to provide a voltage gain of 6 dB (2x), and an output impedance of 75Ω to ensure the same level is available at the output.

Transistors T4 and T3 form a complementary Darlington device whose gain depends on the ratio of (R3/R4) to R8. The polarity of the original signal is not changed by this amplifier. Using diode D1 the CVBS input signal is clamped at a level determined by voltage divider R6-P1-R5. Thanks to the preset, the circuit can be made to respond properly to input signals which are marginally out of spec (i.e., too weak or too strong). The result of the clamping operation is that the signal at the base of T4 has a stable bias level. By way of resistor R7, T4 can be disabled by the M-V OFF (Macrovision-Off) signal, which is digital and generated by the EPLD chip. The values of resistors R4, R3 and R7 are such that the 'off' level corresponds to 'black', while the amplified signal is not clipped at either side.

Emitter follower T2 acts as an output buffer. A simple level detector, T1,

The video copy processor may be



Finally, there are two LED indicators in the circuit: one for the power supply (D7, red), and another which lights when a Macrovision signal is detected (D6, green).

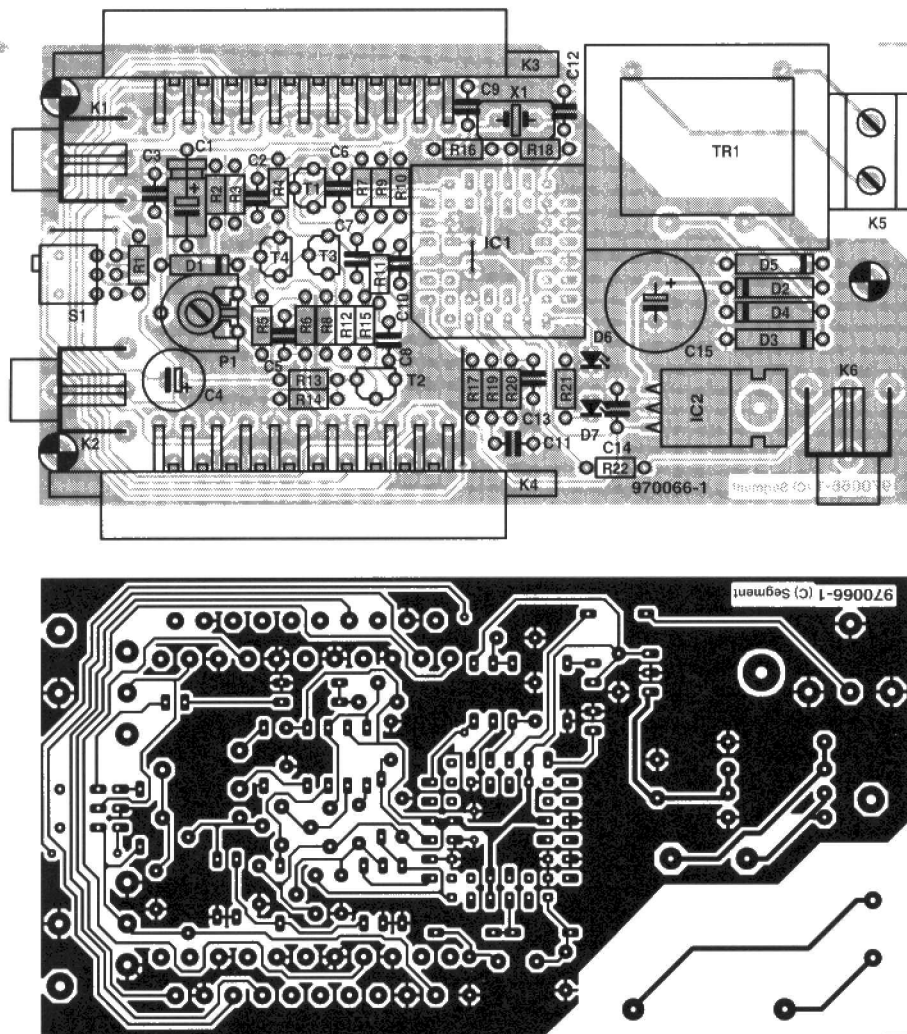


Figure 4. Copper track layout and component mounting plan of the printed circuit board designed for the Video Copy Processor. This board is available ready-made through our Readers Services, together with the programmed EPPLD chip.

CONSTRUCTION

We've designed a very compact printed circuit board for the Video Copy Processor, and would advise anyone intending to build this circuit to use the ready-made board supplied through our Readers Services, or a kit supplier. For your reference, and for those of you who insist on making the board themselves, the artwork of the single-side printed circuit board is shown in **Figure 4**. Mounting the parts specified in the components list is mostly plain sailing. There are three wire links on the board: one under the EPPLD socket, one between switch S1 and connector K1, and between K4 and the EPPLD socket. Before you do anything else, **locate and install these three wires**. Next, it is recommended to stick to this order when mounting the parts: resistors, capacitors, IC

socket, semiconductors, connectors, transformer, crystal. The two LEDs should be mounted at a height that enables them to protrude from the top panel of the case. Watch the orientation of the *polarised* components. Yes, that includes the PLCC socket for the EPPLD chip. Be warned, one error and you'll be spending hours on faultfinding, not even mentioning the cost of a new EPPLD chip.

The dissipation of the 7805 on the board is quite low so that a heat-sink is not necessary. Use an M3 bolt, washer and nut to secure the regulator to the board.

For an exact fit, the size of the board and the position of the connectors demand the use of a type SD20 plastic case from Donau. Alas, there's no way you can avoid cutting, drilling and filing clearances for the SCART sockets, the LEDs, the cinch sockets, the decoder-bypass switch, and the mains input cord. Fortunately ABS plastic is an easy going material.

After a thorough visual check, the board is mounted in the case with the aid of three M3 screws (for which there are holes in the PCB), and 10-mm long PCB standoffs which are secured to the back plate of the case.

As a finishing touch, stick four rub-

ber feet on the back panel to prevent scratches on your furniture.

SETTING-UP, CONNECTING-UP

Apart from preset P1, there are no adjustments in this circuit. Initially, the preset is set to mid-travel. If necessary, adjust it if the output level supplied by the 'playing' VCR is on the high or low side.

The Video Copy Processor is inserted in the AV (audio/video) link

COMPONENTS LIST

Resistors:

R1, R13, R14 = 75Ω
R2, R18 = 100kΩ
R3, R22 = 100Ω
R4 = 220Ω
R5 = 15kΩ
R6 = 22kΩ
R7 = 22Ω
R8 = 390Ω
R9 = 390kΩ
R10 = 2kΩ
R11 = 330kΩ
R12, R16, R19, R20, R21 = 1kΩ
R15 = 560Ω
R17 = 10kΩ
P1 = 2kΩ5 preset H

Capacitors:

C1 = 2μF2 16V
C2, C3, C5, C10, C14 = 100nF
C4 = 220μF 16V radial
C6 = 220pF
C7 = 220nF
C8, C11, C13 = 10nF
C9, C12 = 47pF
C15 = 1000μF 16V radial


Semiconductors:

D1 = 1N4148
D2-D5 = 1N4001
D6 = green LED, high efficiency
D7 = red LED, high efficiency
T1, T3 = BC560B
T2 = BC550B
T4 = BC550C
IC1 = EPM7032 z
IC2 = 7805

Miscellaneous:

K1, K2, K6 = cinch socket, angled, PCB mount
K3, K4 = SCART connector, angled, PCB mount
K5 = 2 way PCB terminal block, raster 7.5mm
S1 = double-pole changeover switch (PCB mount, angled, raster 2.54mm), e.g. Fujisoko AS2D, or Arrow D22-E subminiature, RS Components order code 149-276
X1 = 6 MHz quartz crystal
TR1 = mains transformer, PCB mount, 6V 1.5VA (Monacor/Monarch VTR1106)
Case: type SD20 from Donau. Outside dimensions: approx. 125x70x40 mm.
PCB and programmed EPPLD chip: order code 970066-C (see Readers Services page).

5

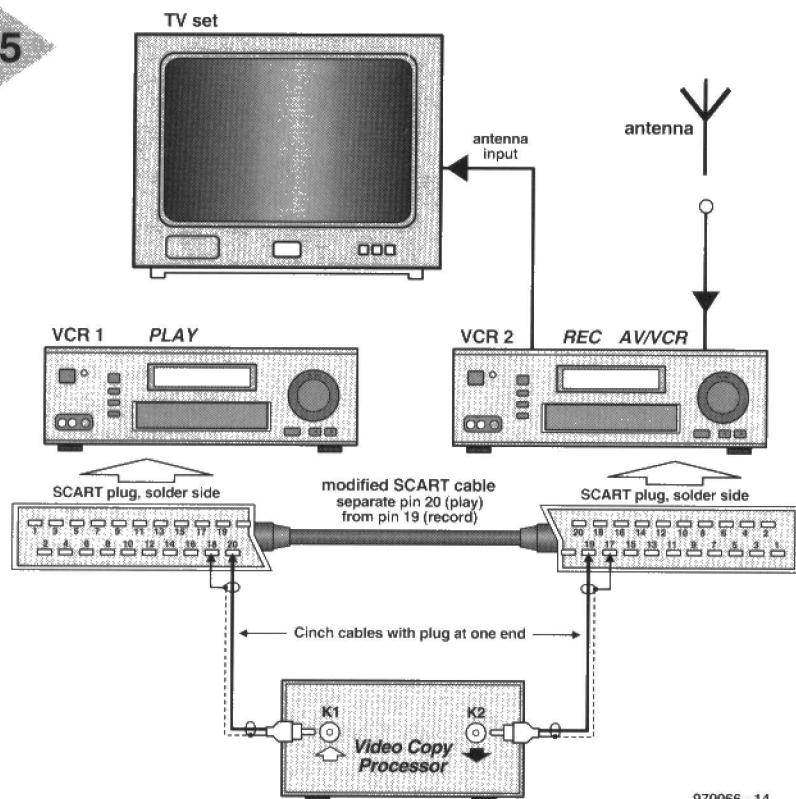

970066 - 14

Figure 5. Use this alternative cabling scheme if for some reason you don't want to use two SCART cables to connect the Video Copy Processor between the two VCRs. The alternative consists of one SCART cable whose plugs are opened and modified to break one of the CVBS links. In this way you enable the CVBS signal to be passed through the Video Copy Processor using two coax cables fitted with cinch plugs. Each SCART plug on the cable so modified has to be marked to make sure it goes to the right VCR ('play' or 'record').

(cinch, BNC, DIN or SCART) between a **playing** and a **recording** VCR. Normally, two SCART cables will be used: one from the playing VCR to the input of the copy processor, and another, from the copy processor output to the recording VCR. This is the easiest solution, as the Copy Processor has two SCART sockets, K3 (input) and K4 (output) available for this purpose.

If you don't want to invest in two SCART cables, you may also make do with one by using the alternative connection scheme illustrated in **Figure 5**.

You have to open up the two SCART plugs, though, and do some soldering inside. It is also necessary to mark the SCART plugs which go the different VCRs to prevent the cable being connected the wrong way around. Basically, the alternative connection boils down to breaking one of the two CVBS wires (pins 19 and 20), and giving it an alternative route through the Video Copy Processor by way of short pieces of coax cable terminated with cinch plugs.

(970066-1)

Reference:

1. Macrovision decoder/blanker, *Elektor Electronics* October 1988.

6


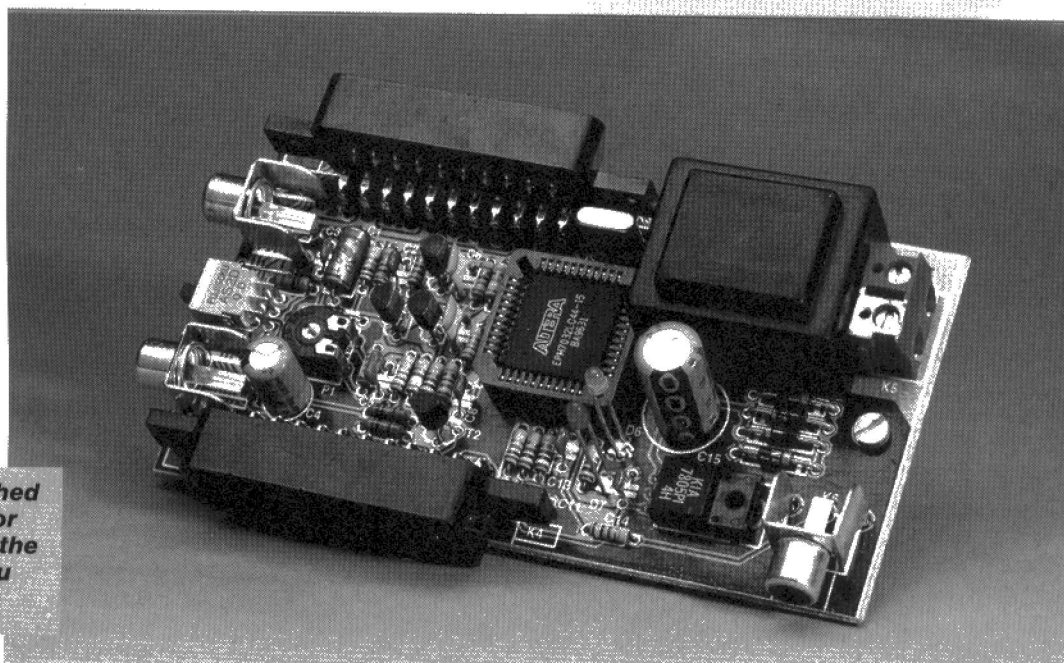


Figure 6. Finished board, ready for mounting into the compact Donau case.

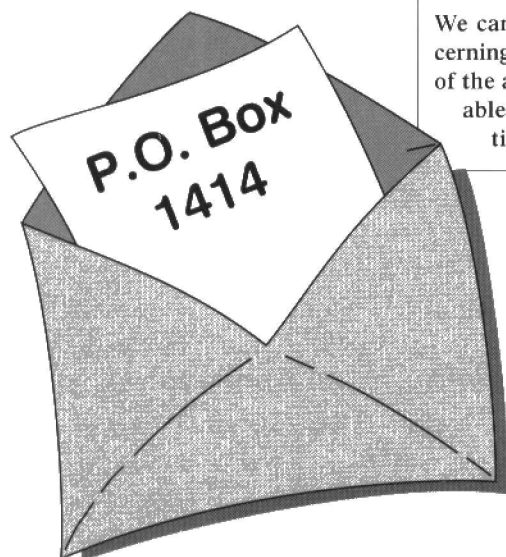

We can only answer questions or remarks of general interest to our readers, concerning projects not older than two years and published in *Elektor Electronics*. In view of the amount of post received, it is not possible to answer all letters, and we are unable to respond to individual wishes and requests for modifications to, or additional information about, *Elektor Electronics* projects.

Sampling rate converter

I am using the Sampling Rate Converter (October 1996) to transfer recordings from a DAT recorder (48 kHz) to a CD recorder (44.1 kHz) to burn my own CDs. This works quite well, only the track numbers seem to drop out of the copy process. How come?

A. Eggert, Germany

Your observation is correct. The SRC only converts the audio samples, that is, audio data only. As you may have seen from the circuit diagram on page 31, the Channel Status, User and Validity bits are not decoded and not transferred. The corresponding serial inputs, C U and V, of the output IC type CS8402A are tied to ground. At the output, the channel status bits may be programmed using the 7 DIP switches in S1. In this way, it is possible to redefine the channel status bits like Copybit, Category code and Generation bit and change between Professional and Consumer mode.

Mini Flash Programmer tip

While building up the Mini Flash programmer described in your October 1996 magazine I stumbled on the error mentioned in the text regarding the Centronics interface (thanks for your helpful note on the signal levels). Because I have a relatively new motherboard which I would not like to change (never change a winning team) I have used two gates from a 4050

package, one is inserted in the DOUT line, the other, in the BUSY line. The inputs of the other four gates in the 4050 are tied to ground. The programmer now works without problems, and without any modification to the PC.

G. Mayer, Austria

Thank you for this useful tip which we hope will benefit other readers as well.

Measuring inductance

I am still riddled by your article 'Simple Inductance Meter' in the February 1997 issue. The principle used by the author is based on measuring the resonance frequency of an L-C network. In the past, I have often measured inductances with the aid of a voltage/current diagram. In this way, one measures the inductance in series with a known (non-reactive) resistance. That allows the R-L network to be supplied with a 50-Hz test frequency using an adjustable transformer (even one for model trains is okay for this purpose). The inductors were soft iron core types with values between 0.1 mH and 0.3 mH. The transformer was set to different output voltages, whereupon the voltage across the network was measured, as well as the current through it. Using the formula

$$L = \frac{1}{\omega} \cdot \sqrt{\left(\frac{U}{I}\right)^2 - R^2}$$

I then calculated the inductance. In the equation, U is the voltage across the R-L network, I the current through the network, and R the non-reactive series resistance. One problem is that the inductance does not appear to be constant. Instead, it shows up small variations depending on the test current. I reckon the effect is caused by the fact that the core permeability is not constant. Consequently, I was wondering if the test current should not be stated along with the inductance.

Regarding your Magnetic-Field Meter project (January 1997), I would like to know if it is possible to extend the measuring range to 3 Tesla, in order to do measurements on large inductors, too. Can I use a pick-up coil for this purpose, or should I go for a Hall sensor?

R. Leurs (Netherlands)

The formula you are using is, in principle, suitable for measuring inductances. However, the test frequency is pretty low, which causes problems with many inductors. In any case, the test currents should not be too high to prevent the risk of core saturation. With large inductors, say, loudspeaker filter coils, the manufacturer therefore states the maximum permissible coil current.


Extending the measurement range of the Magnetic-Field Meter is, in principle, possible by means of a corresponding

reduction of the number of turns of the pick-up coil. For reliable measurements of coil inductances we do, however, recommend a dedicated and accurate test instrument like the Advanced RLC Meter described in the April, May and June 1997 issues of *Elektor Electronics*. This instrument is also useful for measuring unknown capacitors and resistors.

Power-off accelerator

In our article '50 W a.f. amplifier' (November 1996), an option was mentioned that would allow switch-off noises to be eliminated. This, we said, could be achieved by having the 'mute' and 'standby' connections on the board controlled by a small add-on circuit consisting of two diodes and a reservoir capacitor. Apparently that description was not accurate enough for some readers, who wrote in requesting a detailed circuit diagram. Also, this 'simple' solution may still result in switch-off noises because the voltage at the 'mute' and 'standby' pins does not drop fast enough when the amplifier is switched off.

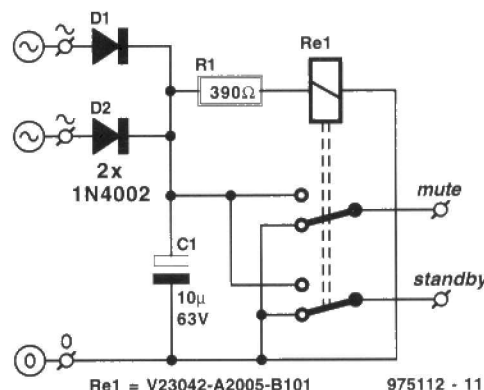The diagram shows a small extension circuit which does the trick. A relay is used to speed up the mute circuit in a reliable manner. Because a 24-V relay is used, it is de-actuated as soon as the transformer voltage disappears. Capacitors C4 and C5



in the amplifier circuit are then allowed to be discharged quickly via R4 or R5 and the relay contacts. The anodes of D1 and D2 are connected to the transformer secondary voltages (22 V each). Instead of the indicated relay type from Siemens (nominal coil voltage 24 V, coil resistance 2210 Ω) you may, of course, use another relay, provided the series resistor R1 is modified accordingly. A relative-

ly light rating is sufficient for the contacts (60 V/10 mA).

Hygrometer

Your July/August 1997 magazine had an article about a hygrometer. I would appreciate if I could get more information about capacitor C1. According to my calculations, it should have a value of the order of 150 pF. My problem is that I do not understand how a capacitor

can function as a humidity sensor, because its case would have to be open to air. Please inform me where this capacitor may be obtained, is the calculated value correct, and what do you call this capacitor?

Jan Nel, South Africa.

In the circuit diagram, the functional symbol given to component C1 is that of a variable capacitor. The actual device is,

however, not a capacitor but a dedicated humidity sensor type H1 from Philips Components. This device, which was already used in a number of our earlier designs, is normally available from our regular advertiser C-I Electronics.

CORRECTIONS & UPDATES

80C537 Microcontroller Board

June 1997 - 970048-1

The pin assignment of the 9-way RS232 socket requires some attention because it is different from the normal configuration. Pin 9 supplies +5 V to enable an external interface (if used) to be powered. Normally, the presence of a supply voltage does not pose problems, because pin 9 is not used for the RS232 connec-

tion. At least one case has been reported to us, however, of serious problems caused on a laptop computer. For safety's sake, cut the +5 V connection to pin 9, and do not restore it until you actually need the +5 V line to power an external device or interface.

Also note that pins 1, 6 and 8 are linked on the 9-way socket. This arrangement may not function on some PCs, causing

(delayed) error reports to the effect that a communication error has occurred. If that happens, it is recommended to change the pinout to reflect the standard zero-modem layout. This is achieved by interconnecting, either in the cable or at the socket, pins 1, 4 and 6, and (separately) 7 and 8.

Alternatively, disable the handshaking in the communication program.

Chipcard Reader/Programmer

September 1997 - 970050-1

The correct order code of the RS Components (ElectroMail) card reader module used in this project is **453-791**. An alternative is the CCM01 2N032 (9320) from ITT-Cannon.

SWITCHBOARD

Switchboard allows PRIVATE READERS of *Elektor Electronics* one FREE advertisement of up to 106 characters, including spaces, commas, numerals, etc., per month. The advertisement MUST relate to electronics, and it MUST INCLUDE a private telephone number or name and address; post office boxes are NOT acceptable.

Elektor Electronics (Publishing) can not accept responsibility for any correspondence or transaction as a result of a free advertisement or of any inaccuracy in the text of such an advertisement.

Advertisements will be placed in the order in which they are received. Elektor Electronics (Publishing) reserve the right to refuse advertisements without giving reasons or without returning them.

FOR SALE EPROM programmer, built (no case), + software, Elektor March 97, at cost price £50. Phone Bill Brown on (0194) 625660.

WANTED National cathode-ray oscilloscope model VP-513A manuals or diagram. Willing to pay. John S. Syros, 26 Kyprou Str., Athens 141-22, Greece.

WANTED Operation manuals for Tascam244 Portastudio recorder and Akai 1721L reel tape recorder. Photocopy will do. Phone J.S. Mundell on (0181) 2418188.


WANTED Microguard 600-40 UPS circuit diagram or service manual details. Phone Angus MacKenzie on (0150) 8493124.

WANTED circuit or device that will telephone my home number when my office burglar alarm is set off. Phone Joe Ruston on (0181) 947 6616

airflow and temperature sensor Type TMP12

*effective monitoring
of cooling systems*

The TMP12 is a silicon-based airflow and temperature sensor designed to be placed in the same airstream as heat generating components that require cooling. Fan cooling may be required continuously, or during peak power demands, e.g., for a power supply, and if the cooling system fails, system reliability and/or safety may be impaired. By monitoring temperature while emulating a power IC, the TMP12 can provide a warning of cooling system failure.

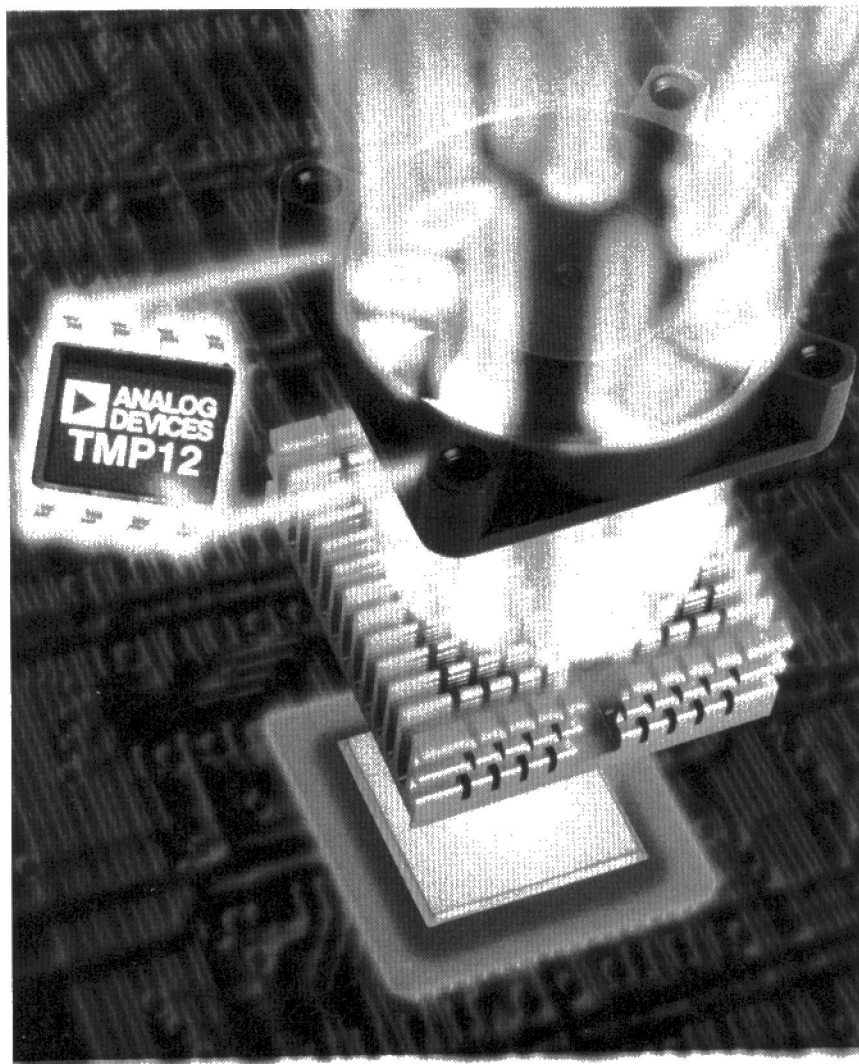

The TMP generates an internal voltage that is linearly proportional to Celsius temperature, nominally $+5 \text{ mV } ^\circ\text{C}^{-1}$. The linearized output is compared with voltages from an external resistive divider – R_1 – R_3 in Figure 1 – connected to the TMP's 2.5 V precision reference. The divider sets up one or two reference voltages, as required by the user, providing one or two temperature setpoints. Comparator out-

puts are open-collector transistors able to sink over 20 mA.

There is an on-board hysteresis generator provided to speed up the temperature-setpoint output transitions, which also reduces erratic output transitions in noisy environments. Hysteresis is programmed by the external resistor chain and is determined by the total current drawn from the 2.5 V reference.

Table 1. Specifications of the TMP12.
 $(V_S = +5\text{ V}, -40^\circ\text{C} \leq T_A \leq +125^\circ\text{C}, \text{sauf mention contraire})$

Parameter	Symbol	Conditions	Min.	Typical	Max.	Units
ACCURACY						
Accuracy (high, low setpoints)		$T_A = +25^\circ\text{C}$		± 2	± 3	$^\circ\text{C}$
		$T_A = -40^\circ\text{C}$ to $+100^\circ\text{C}$		± 3	± 5	$^\circ\text{C}$
Internal scale factor		$T_A = -40^\circ\text{C}$ to $+100^\circ\text{C}$	+4.9	+5	± 3.1	$\text{mV}/^\circ\text{C}$
Power supply rejection ratio	PSRR	$4.5\text{ V} \leq V_S \leq 5.5\text{ V}$		0.1	0.5	$^\circ\text{C}/\text{V}$
Linearity		$T_A = -40^\circ\text{C}$ to $+125^\circ\text{C}$		0.5		$^\circ\text{C}$
Repeatability		$T_A = -40^\circ\text{C}$ to $+125^\circ\text{C}$		0.3		$^\circ\text{C}$
Long term stability		$T_A = +125^\circ\text{C}$ for 1000 hrs		0.3		$^\circ\text{C}$
SETPOINT INPUTS						
Offset voltage	V_{OS}			0.25		mV
Output voltage drift	TCV_{OS}			3		$\mu\text{V}/^\circ\text{C}$
Input bias current current	I_B			25	100	nA
VREF OUTPUT						
Output voltage	V_{REF}	$T_A = +25^\circ\text{C}$, no load	2.49	2.50	2.51	V
	V_{REF}	$T_A = -40^\circ\text{C}$ to $+100^\circ\text{C}$, no load		2.5 ± 0.015		V
Output drift	TCV_{REF}			-10		$\text{ppm}/^\circ\text{C}$
Output current, zero hysteresis	I_{VREF}			7		μA
Hysteresis current scale factor	SF_{HYS}			5		$\mu\text{A}/^\circ\text{C}$
OPEN-COLLECTOR OUTPUTS						
Output low voltage	V_{OL}	$I_{SINK} = 1.6\text{ mA}$		0.25	0.4	V
		$I_{SINK} = 20\text{ mA}$		0.6		V
Output leakage current	I_{OH}	$V_S = 12\text{ V}$		1	100	μA
HEATER						
Resistance	R_H	$T_A = +25^\circ\text{C}$	97	100	103	Ω
Temperature coefficient		$T_A = -40^\circ\text{C}$ to $+125^\circ\text{C}$		100		$\text{ppm}/^\circ\text{C}$
Max. continuous current	I_H	Guaranteed but not tested			60	mA
POWER SUPPLY						
Supply range	$+V_S$		4.5		5.5	V
Supply current	I_{SY}	Unloaded at +5 V		400	600	μA
		Unloaded at +12 V		450		

The TMP12 airflow sensor also incorporates a precision, low-temperature coefficient $100\ \Omega$ heater resistor that may be connected directly to an external 5 V supply. When the heater is actuated, it raises the die temperature in the DIP package to about 20°C above ambient (in still air).

FUNCTIONAL DESCRIPTION


The TMP12 temperature sensor section consists of a bandgap voltage reference which provides both a constant 2.5 V output and a voltage that is proportional to absolute temperature (VPTAT). The VPTAT has a precise temperature coefficient of $5\text{ mV}/^\circ\text{C}$, and is 1.49 V (nominal) at $+25^\circ\text{C}$. The

comparators liken VPTAT to the externally set temperature trip points and generate an open-collector output sig-

nal when one of their respective thresholds has been exceeded.

The heat source for the TMP12 is

Figure 1. The main elements of the TMP12 are a temperature-dependent voltage source, two comparators, and a heater resistor.

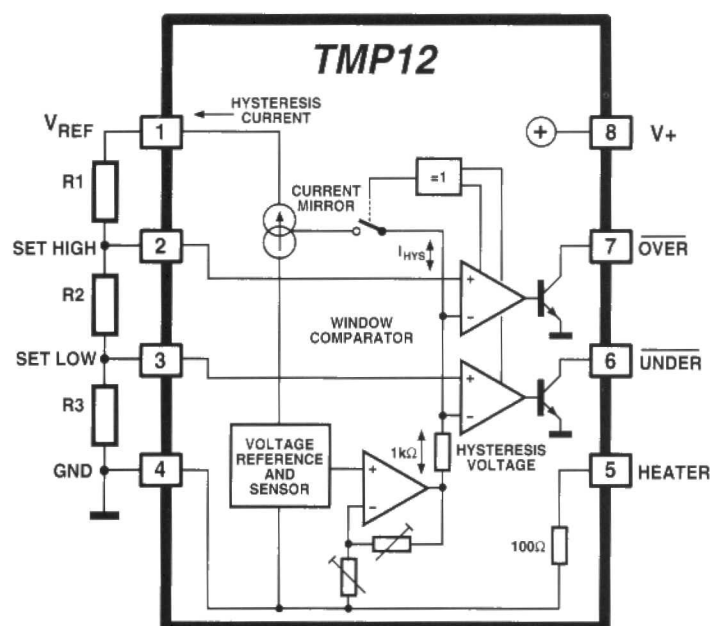

970080 - 11

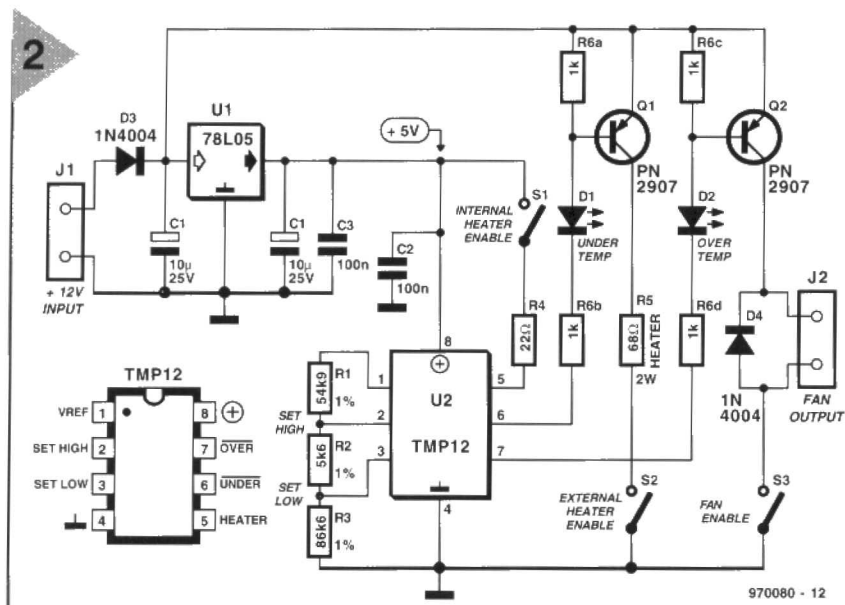


Figure 2. Typical basic application of the TMP12 (called Evaluation Board by Analog Devices).

an on-chip $100\ \Omega$ low temperature coefficient thin-film resistor. When this is connected to a 5 V source, it dissipates

$$P_D = V^2/R = 5^2/100 = 0.25 \text{ W},$$

which generates a temperature rise of about 32 °C in still air and about 22 °C in an airflow of 2.3 m s⁻¹. By selecting a temperature setpoint between these two values, the TMP12 can provide a logic-level indication of problems in the cooling system.

A proprietary, low temperature coefficient thin-film resistor, in conjunction with production laser trimming, enables the TMP12 to provide a temperature accuracy of $\pm 3^\circ\text{C}$ (typical) over the rated temperature range.

The open-collector outputs are capable of sinking 20 mA, allowing the TMP12 to drive small control relays directly.

Operating from a single +5 V supply, the quiescent current is only 600 μ A (max), without the heater resistor current.

PROGRAMMING THE TMP12

The basic thermal monitoring application requires only a simple three-resistor ladder voltage divider to set the high and low setpoints and the hysteresis. These resistors are programmed in the following sequence.

1. Select the desired hysteresis temperature.
2. Calculate the hysteresis current, I_{VREF} .
3. Select the desired setpoint temperatures.
4. Calculate the individual resistor divider ladder values needed to develop the desired comparator setpoint voltages at the Set High

and Set Low inputs.
The hysteresis current is calculated from

$$I_{\text{HYST}} = I_{\text{THREE}} = 5 \mu\text{A}^\circ\text{C}^{-1} + 7 \mu\text{A}.$$

For example, to produce 2°C of hysteresis, I_{VREF} should be set to 17 μ A.

The setpoint voltages, V_{SET} are calculated from

$$V_{\text{SET}} = (T_{\text{SET}} + 273.15)(5 \text{ mV } ^\circ\text{C}^{-1}).$$

This equation is used for both V_{SETHIGH} and V_{SETLOW} . A simple three-resistor network, as shown in Figure 1, determines the setpoints and hysteresis value. The equations to calculate the resistors (in k Ω) are:

$$R_1 = (V_{\text{REF}} - V_{\text{SETHIGH}}) / I_{\text{VREF}};$$

$$R_2 = (V_{\text{SETHIGH}} - V_{\text{SETLOW}}) / I_{\text{VREF}};$$

$$R_3 = V_{\text{SETLOW}}/I_{\text{VREF}}.$$

SELECTING SETPOINTS

Choosing the temperature setpoints for a given system is an empirical process, because of the wide variety of thermal issues in any practical design. The specific setpoints are dependent on factors such as airflow velocity in the system, adjacent component location and size, PCB thickness, location of copper ground planes, and thermal limits of the system.

TYPICAL APPLICATION

The circuit in **Figure 2** is a typical application of the TMP12 (it is called 'Evaluation Board' by Analog Devices). In this, the IC needs a single 12 V supply for operation, which is, however, required only for the fan and under-temperature heater. The 5 V line

required by the TMP12 is produced by an on-board regulator, U_1 .

Three switches are provided to (1) connect the internal heater; (2) disconnect the under-temperature heater; (3) disconnect the on-card fan.

The setpoint temperatures provided by the (unmodified) circuit are $\geq 40^\circ\text{C}$ (TMP12 junction temperature) for cooling fan ONm and $\leq 20^\circ\text{C}$ for heater ON. Thermal hysteresis is set to 2°C . Different setpoint and hysteresis values may be set by changing the values of R_1 – R_3 using the equations given earlier in this article.



The preset trip temperatures will cause the fan to cycle ON and OFF (in typical laboratory temperatures) with the TMP12's internal heater enabled.

Resistor R_4 is provided to adjust the internal power dissipation of the TMP12; this resistor should be removed when the pin-compatible low-power, programmable version of the IC, TMP01, is used.

The low-setpoint or heater function is used primarily for the TMP01 in heating/cooling control applications. However, the low-setpoint function is also included on the TMP12 airflow sensor as the function is easily changed to a second high-setpoint by inverting the logic output polarity (using an external gate). In that way, the TMP12 can provide actuation for primary and secondary cooling fans, or an auxiliary fan control plus over-temperature warning.


ELEKTOR ELECTRONICS

EXTRA

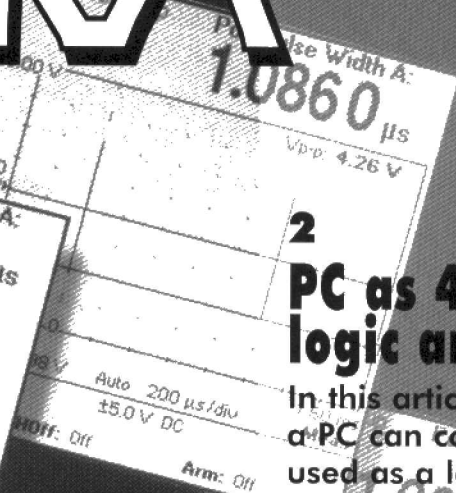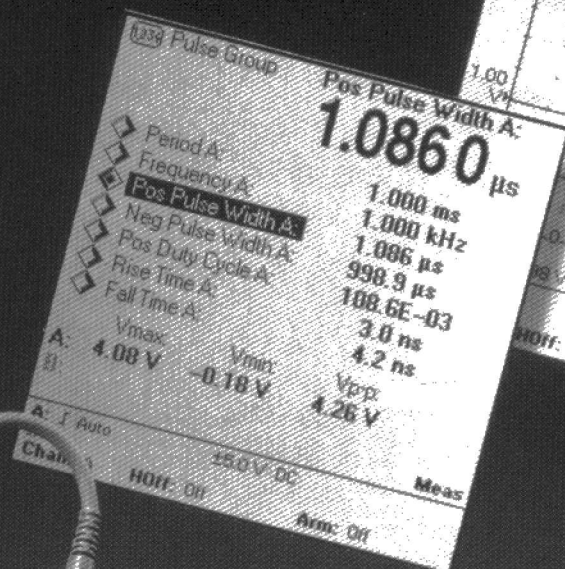

2 PC as 4-channel logic analyser

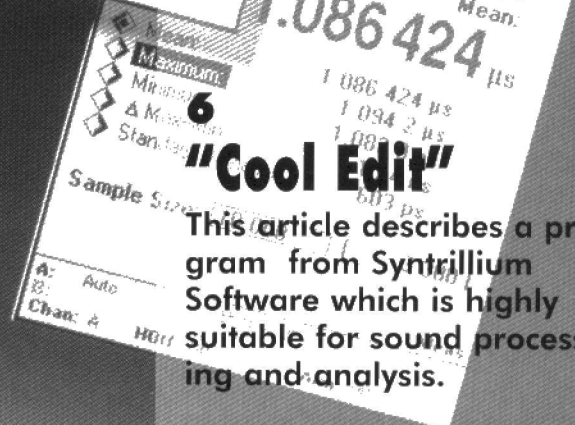In this article we show how a PC can conveniently be used as a logic analyser.




10 Trigger techniques

New trigger techniques are described that have had to be developed for a range of modern equipment.

14 "ASCOPE"

This computer program enables the transfer of asynchronous signals between two pieces of equipment to be monitored and, if desired, saved for later analysis.

TEST & MEASUREMENT

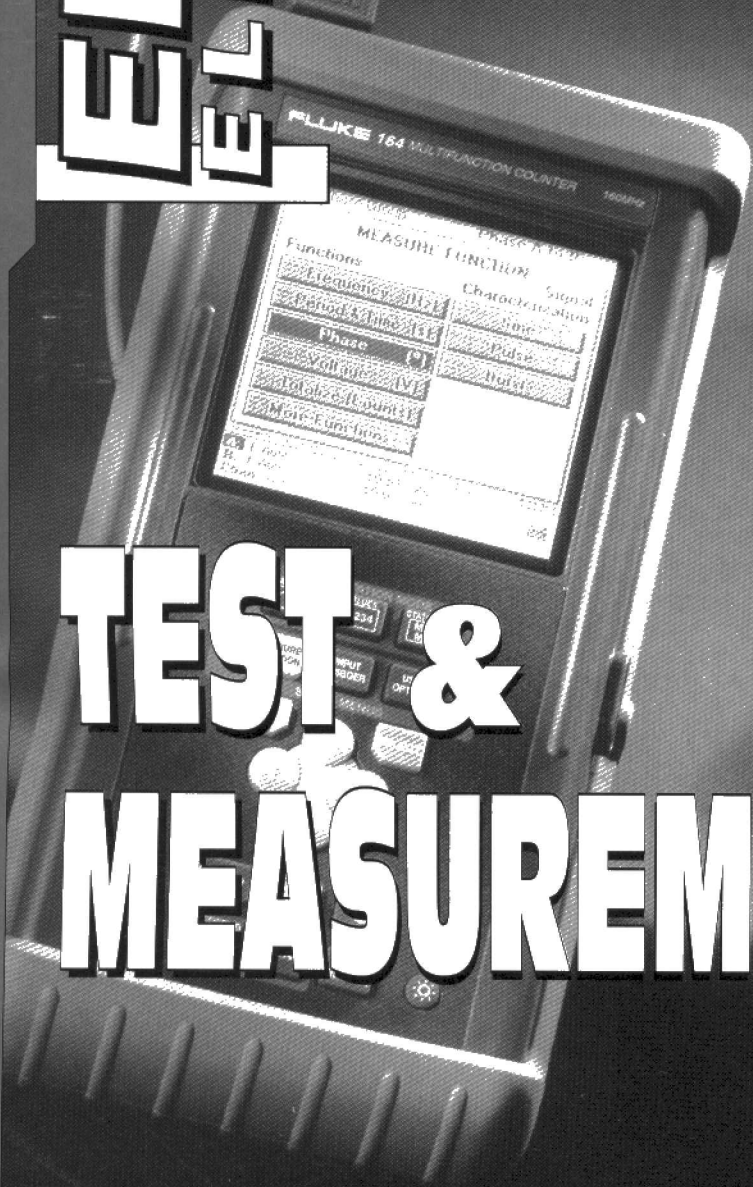

It is well known that a PC can be used to measure electronic quantities by making it behave as an oscilloscope through suitable software. Since a logic analyser is a variation of a digital oscilloscope, it stands to reason that a PC with its parallel inputs that can be scanned at high speed and its depth of memory to compute the measurement values is eminently suitable for use as a logic analyser. But where an oscilloscope displays real-time waveforms of signals, logic analysers store the signal for display in a non-real-time way.

Software design by Schröder

PC as 4-channel logic analyser

with or without electrical isolation

The number of input channels a logic analyser has defines the instrument's potential. If, for instance, the instrument is to be used to analyse an 8-bit micro-processor system with, say, a 16-bit address bus, an 8-bit data bus, and five or six control lines, the minimum number of input channels it needs is about 30. Unfortunately, a PC has normally only five parallel inputs so that the present logic analyser is restricted to four input channels.

The logic level at the four inputs is sampled at a rate of up to 1.2 MHz and saved in packets of 40 kbytes. Note that the sampling rate depends on the PC used: for instance, one that uses a 486 processor running at 33 MHz cannot go over 150 kHz.

The program makes three trigger modes available. There is also a 255 byte pre-trigger memory that determines the time interval before the trigger mode is set. The displayed diagrams may be printed or saved. There are numerous other facilities, such as scrolling, zooming, scanning of the display, and setting of the period and frequency. All four channels may be used for frequency measurement. Channel 1 may be used for the measurement of pulses, pulse width and pulse spacing. The results of measurements are shown in separate windows.

hardware

The only hardware needed for the logic

analyser is for the protection of the Centronics interface and for preventing that this interface overloads weak signals. This is because the Centronics inputs draw a current that in certain circumstances may exceed the output capabilities of the signal source.

There are two circuits available, one with electrical isolation (Figure 2) and the other without (Figure 1).

In the circuit in Figure 1, resistors R_1 – R_5 limit the input current to about 0.4 mA (from a supply line of 5 V). Circuit IC₁ is a transistor array with common emitter and open collector. The pull-down resistors, which are in parallel with the internal pull-up resistors and may, therefore, in some cases be omitted, prevent the bases of the transistors from functioning as antennas

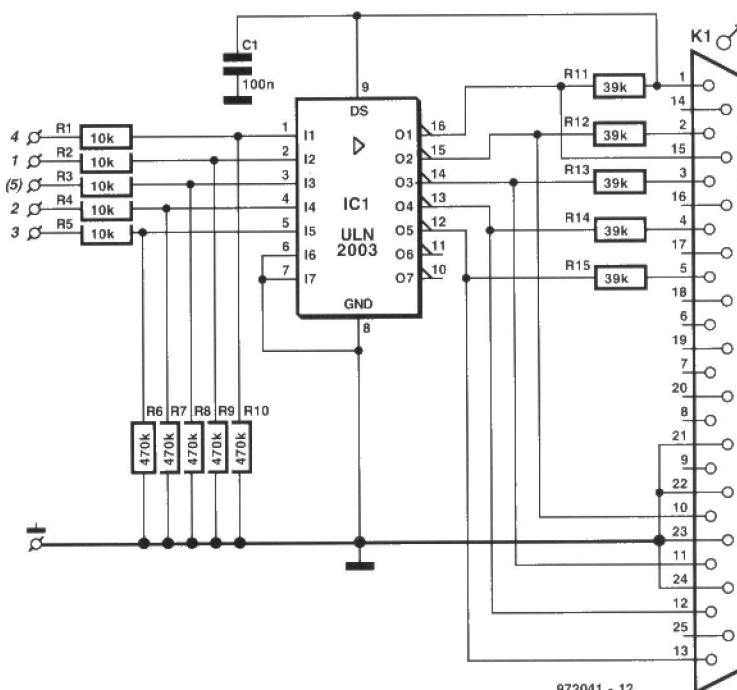


Figure 1. Circuit of the logic analyser hardware not providing electrical isolation.

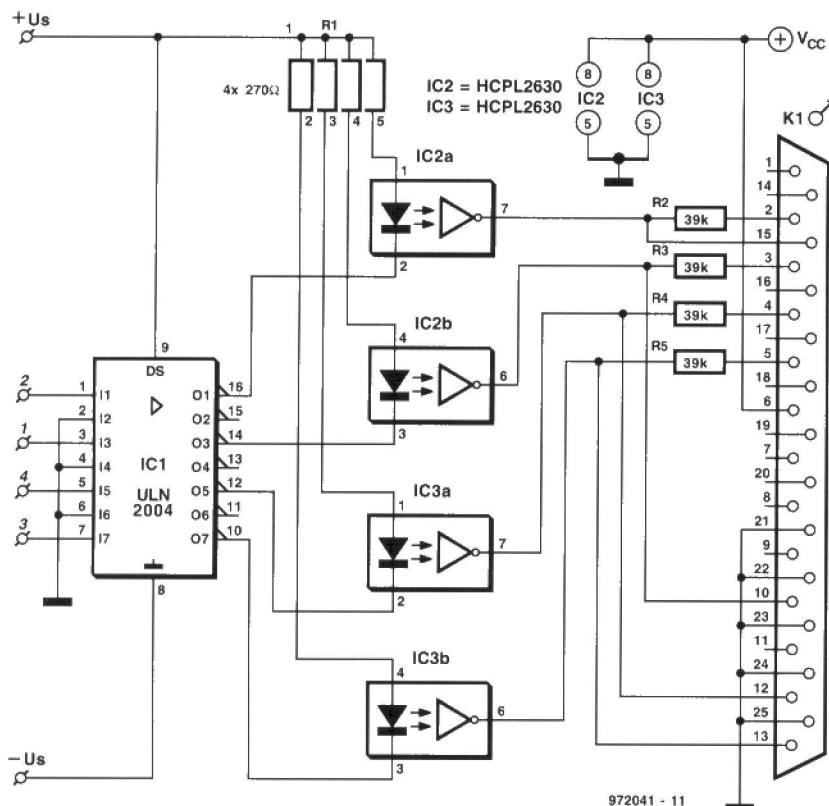


Figure 2. Circuit of the hardware for the logic analyser providing electrical isolation.

tors are omitted since IC₁ has internal 10.2 kΩ series resistors. The output (at the collectors) of the internal transistors in the IC are linked to optoisolators in IC₂ and IC₃.

The optoisolators are not standard in that they have common ground and V_{CC} terminals and two open-collector outputs. To ensure 100% electrical isolation, the transistor array must be powered by the circuit on test via terminals +U_s and -U_s.

When the input level is high, the outputs of IC₁ go low so that the LEDs in IC₂ and IC₃ light and the Schottky transistors at the outputs of these two ICs are on. The control lines, which are normally logic high owing to the pull-up resistors in SIL array R₁, are then pulled low.

The optoisolators have switching times of nanoseconds and are thus highly suitable for operation at high frequencies.

Figure 3 shows the printed-circuit board layouts for both circuits.

software

The logic analyser function is called "Logic_An" and runs under DOS or in the DOS window of Windows 95. For satisfactory operation of the analyser, the computer should be an AT with VGA graphics and DOS 3.3 or better.

The program provides a three-part window as shown in Figure 4. On the right of this, the functions are represented by icons. When one of these is

Parts list (Figure 1)

Resistors:

R₁-R₅ = 10 kΩ
R₆-R₁₀ = 470 kΩ
R₁₁-R₁₅ = 39 kΩ

Capacitors:

C₁ = 0.1 μF

Integrated circuits:

IC₁ = ULN2003 (Sprague)

Enclosure: to personal taste

Parts list (Figure 2)

Resistors:

R₁ = SIL array, 4x270 Ω
R₂-R₅ = 39 kΩ

Integrated circuits:

IC₁ = ULN2004 (Sprague)
IC₂, IC₃ = HCPL2630 (Hewlett Packard)

Enclosure: to personal taste

when the inputs are open-circuited. The pull-up resistors, which are linked to the data lines of the Centronics port, cause the collectors at the output to be logic high. Note that terminal (5) is not used.

In Figure 2, the current-limiting resis-

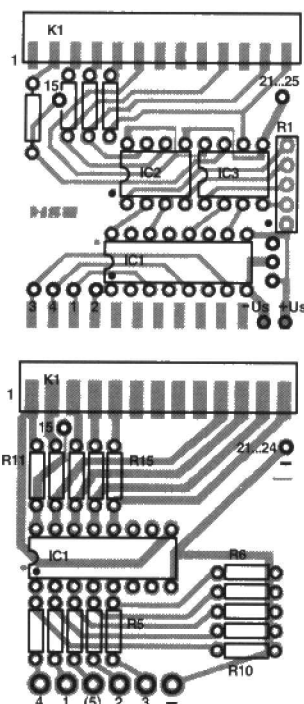


Figure 3. Printed-circuit boards for the hardware in Figures 1 and 2.

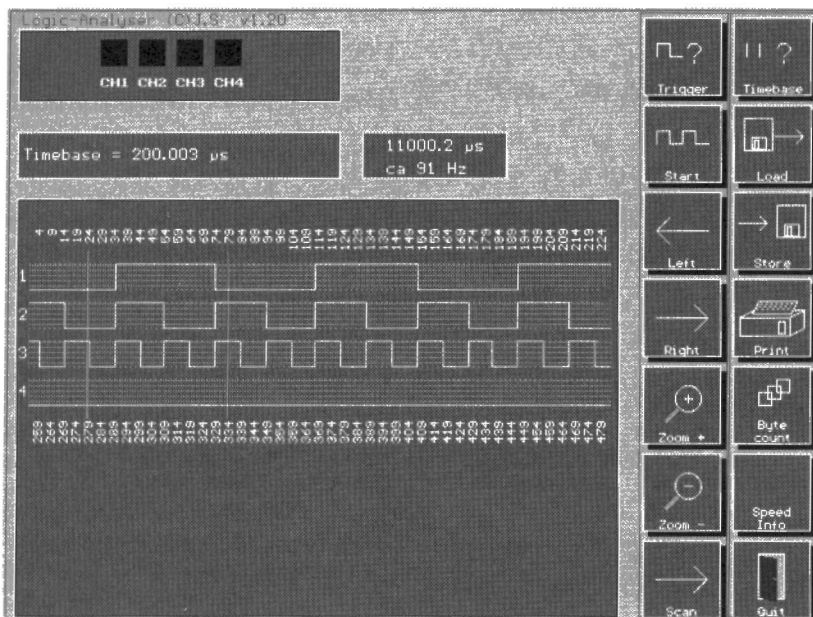


Figure 4. Main monitor screen of the logic analyser.

Hot keys

<key (n)>	function	<ESC>	stop help
<CTRL> <←>	left	<F1>	frequency measurement in channels 1-4
<CTRL> <→>	right	<F2>	frequency measurement in channel 1
<S>	scan (sample)	<shift> <F2>	pulse counting pulse interval
<+>	zoom +	<F3>	
<->	zoom -	<F4>	
<CTRL> <Pos1>	start of plot		

actuated, the desired action is enabled, or a menu is shown via which the wanted function can be selected or set. Selection is carried out with the aid of the arrow-keys and <enter> or by clicking the left-hand button on the mouse.

The integral help function can be selected with <F1>.

Triggering

There are three ways of starting the analyser: (1) by changing the instantaneous value of the sample bit; (2) by selecting a certain group of bits, and (3) by setting the status of a bit. In the case of (2) and (3), a small window is displayed in which the desired bit(s) can be selected with the relevant numeric key and set to low (grey) or high (yellow).

Start

This starts the plotting in the selected trigger mode. If a different one is selected, a window with the relevant trigger mask is shown. Start is stopped when any key is pressed.

Left/right

This shifts the window with the plotted data to the left or right as the case may be.

Zoom+/zoom-

This enlarges or diminishes the scale of the display of plotted data starting at the centre of the window.

Scan

This searches for the next position that is not in accord with the group of bits shown at the right-hand side of the window.

Time base

This sets the sampling value in microseconds, although this also depends on the ICs in the PC. Valid and exact values are ascertained empirically.

Load/save/print

This causes the plot to be loaded, saved or printed. The type of printer is set in the CFG (configuration) file.

Memory capacity

The largest number of bytes that can be saved is 40,000. The wanted, or expected lowest, number can be set as appropriate.

Speed info

This gives information on the length of time it takes for the important functions. INC and PORT IN to be executed, as well as on the approximate sam-

pling frequency.

Stop

This terminates the program.

To determine the cycle time and the frequency, two help lines may be inserted into the measurement window with the mouse. This is done by pressing the left-hand mouse button at the start, hold it down and move the cursor to the stop position. As long as the mouse button is held down, a window is displayed with the cycle time and the corresponding frequency. Here again, the accuracy depends to a large extent on the specification of the PC.

auxiliary functions

The program also provides a number of auxiliary functions which can be selected with the relevant keys as follows.

<F1> switches the previously opened help window giving basic information and procedures to the program. When <enter> is pressed a second window with search masks is shown. The help window is disabled by pressing <ESC>.

<F2> starts the frequency measurement. It opens a window in which the frequencies in the four channels are shown online. <shift> <F2> does the same but only as far as the frequency in channel 1 is concerned. The measurement is ended by pressing <ESC>.

<F3> switches on the pulse counting function for channel 1. The pulses are summed until <ESC> is pressed.

<F4> switches on the pulse interval measurement for channel 1. The interval is displayed online until <ESC> is pressed.

further comments

In the configuration file LOGIC_AN.CFG there are program parameters that can be modified with any ASCII editor.

- 1 :Printer No.: [1, 2]
- 1 :Density of graphics print (1-3) (only in the case of the Epson ink-jet printer).
- 2 :[1]=Epson (9/24 ink-jet); [2]= HPPCL printer (e.g., Laserjet II).

The address of the status register (port address + 1) of the used printer interface must be entered into address file ADR.DAT. The relevant hexadecimal number must be preceded by the \$ sign (\$379 for LPT1 and \$279 for LPT2).


[9/2001]

"Cool Edit", a program from Syntrillium Software Corporation, was originally developed for the recording, processing and analysis of sound. It therefore contains a large number of assembly functions, filters and effects. In the course of time many other facilities have been added so that today the program is very suitable for carrying out measurements on sounds.

By Cees Ruytenberg

"cool edit"

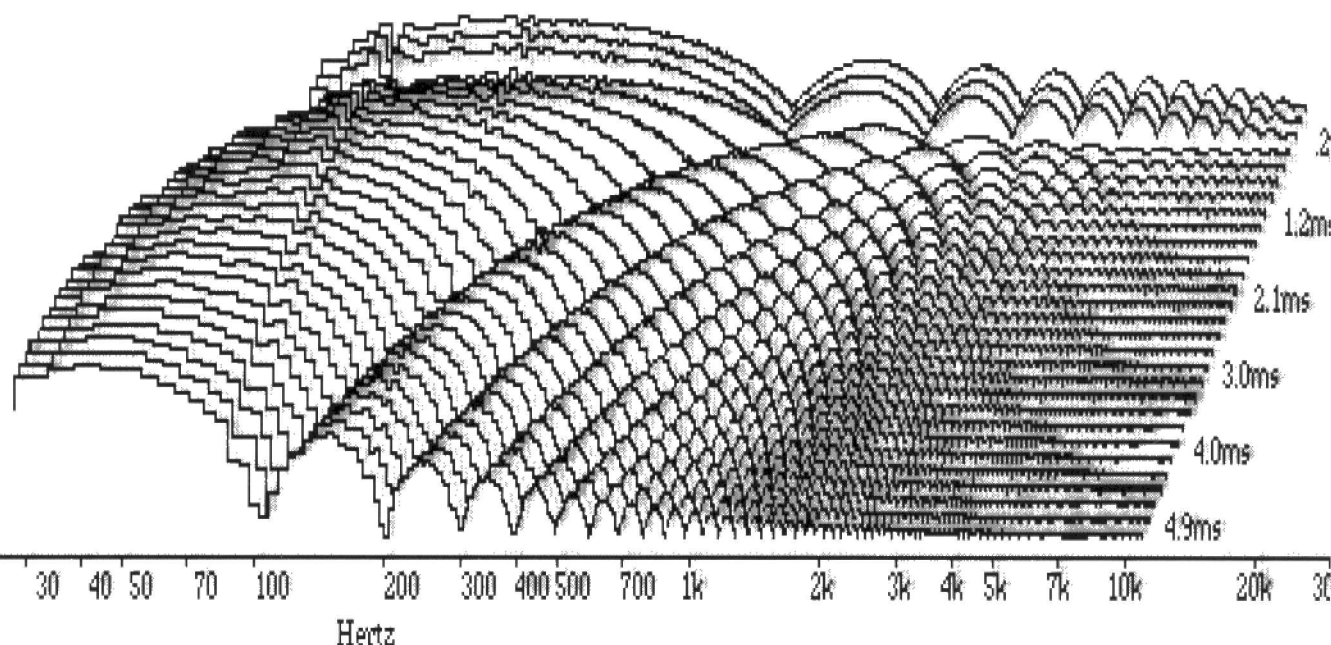software for sound processing and analysis



Although the program can in no way be compared or compete with a spectrum analyser, it offers the PC user a number of interesting facilities for carrying out measurements on audio equipment. The hardware required for this is a PC running Windows 95 or Windows NT and a soundcard supported by Windows. The properties and facilities of the program depend entirely on the type of soundcard.

The simplest setup is through the use of an inexpensive soundcard that is triggered by an external source, such as a test signal from a signal generator. Depending on whether the measurements are acoustical or electrical,

additional requirements are an attenuator, preamplifier and standard test microphone.

Modern soundblaster cards in conjunction with a special driver provide a duplex function, which enables the simultaneous and mutually independent use of the signal generator (output) and the recording section (input).

To obtain a better signal-to-noise ratio, it is possible (with Windows 95) to use two soundcards that operate on different I/O (input/output) addresses and DMA (direct memory access) channels. In this setup, one card is used as generator at all times and the other as measuring card. The accuracy of the

measurement depends primarily on the distortion and noise floor of the sound card used, although harmonics radiated by the computer also have some effect. For instance, the soundblaster 16 Value PNP has a noise floor of around -95 dB and a distortion factor of 0.001 per cent, which is lower than that of many generators. All this means that the properties of the soundcard do not set a limit to many applications.

noise suppression and spectrum analysis

The additional facilities of the program are particularly valuable in the case of

very precise measurements. A typical example is the process of noise suppression. In this, the statistical content of a recorded signal can be ascertained, and stored or erased. This may concern a recording of an instrument amplifier with short-circuited input, or a recording of the quiet just prior to the arrival of a test signal. The information obtained in both cases may be superimposed on the test signal and subsequently subtracted from it so that a clean test signal without spurious elements remains. This may result in a noise reduction of up to 20 dB without loss of quality. In the case of weak signals, this may make it possible to measure well below the noise floor (down to -120 dB). The associated window is shown in **Figure 1**.

The spectrum analysis function offers several interesting possibilities. The amplitude scale (in decibels) is divided according to a manual setting. The frequency scale is determined by the selected sampling rate and may be displayed linearly or logarithmically, as required. The number of FFT (fast Fourier transform) points may be set between 2^7 (128) and 2^{16} (65536).

When the program starts for the first time, the spectrum analysis is displayed in a window the size of about a quarter of the monitor screen. The window may be enlarged to full screen size in the usual manner with the cursor and the left-hand knob of the mouse to make reading the scale more accurate.

Figure 2 shows an example of an analysis of the output signal of an external sine wave generator at a frequency of 1000 Hz (FFT = 8192 points). The second and third harmonic at -90 dB and -84 dB are clearly visible. After the data has been accepted, downsampling and vertical scale adaptation are carried out. When the mouse pointer is placed within the window that shows the spectral content, the frequency and amplitude for that point are displayed. If part of the recording is selected with the editor, the analyser measures and displays the spectral content at the centre of the selected section.

All frequencies occurring within the entire selected section are measured with the function 'scan'. In the presence of noise, this results in a levelling of the curve and gives a good display of the transition in the case of measurements with a sweep signal. 'Scan' is, in fact, the differentiation of a number of spectra that fall within the selected time interval.

Figure 3. Correction curve to linearize the descending characteristic of pink noise (saved as antipink).

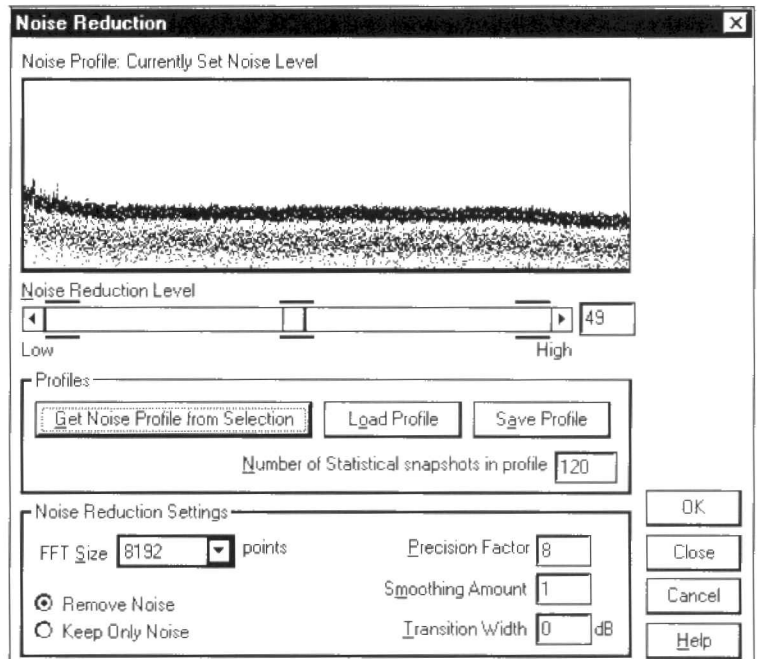


Figure 1. This window provides the noise reduction facilities. The profiles may be saved for later use.


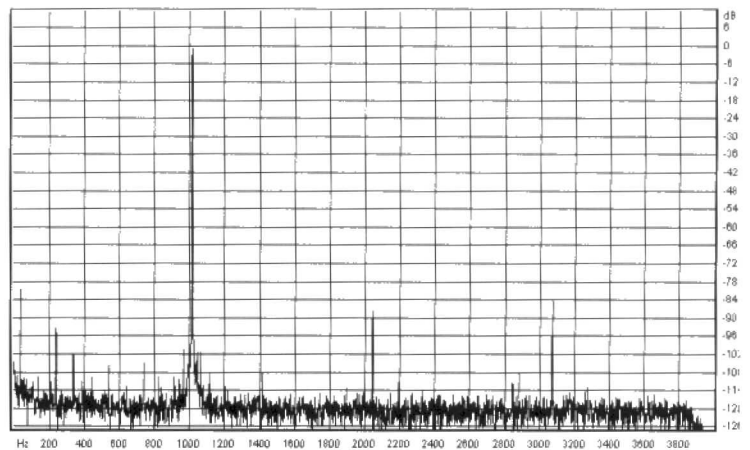


Figure 2. Harmonic distortion of the 1000 Hz output signal of an external generator (FFT=8192 points).

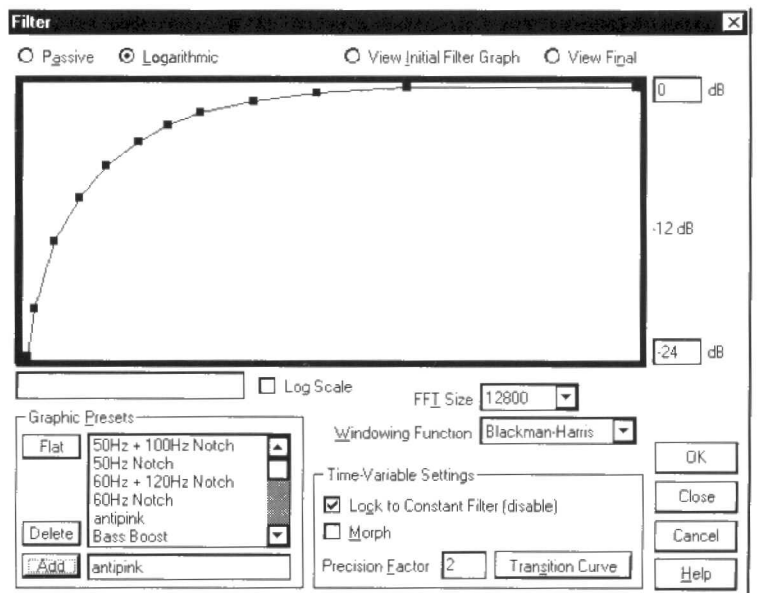

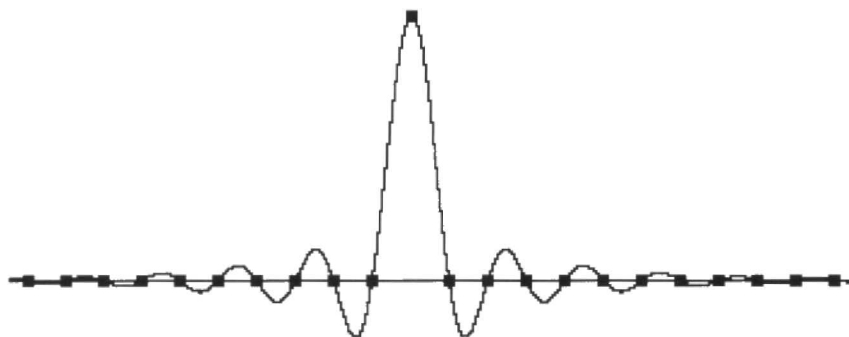


Figure 4. Approximation of a $\sin(x)/x$ function. The sampling points are indicated by squares.

filter functions

Specific interference, such as hum, can be eliminated with the filter function. This function enables the accurate setting of the rolloff and the frequency. The number of FFT points on the filter response characteristic may be chosen on the basis of the wanted accuracy. Unusual rolloffs and a number of filter types, such as pass-band, stop-band, notch, peak, low-pass, high-pass, or combinations of these, are available with the graphics interface.

Spectrum analysis will show a descending characteristic when measurements using pink noise are carried out. This results from the decreasing energy contained in the signal with rising frequency. This aspect should be borne in mind when loudspeaker systems are being tested. Fortunately, with "cool edit" it is possible to correct the slope of the characteristic after the measurements have been taken. The relevant correction curve is shown in **Figure 3**; it may be stored permanently and recalled

at all times.

Curves for linearizing the measurement system may be obtained in a similar manner.

generator function

The generator function enables almost any kind of waveform to be produced.

In the first place, quiet may be generated for any length of time depending on the available space on the hard disk and on the RAM.

Signals such as a burst of $\sin(x)/x$ pulses, or a constant tone – rectangular, sinusoidal, sweep – may be generated for a given time. When such a signal is replayed, it is available at the output of the soundcard. It may be replayed continuously by replaying it in the loop mode. Therefore, signals need not be generated for longer than a second. By setting the duration intelligently or by editing the ends of the waveform suitably, a seamless, endless signal may be obtained. This is also possible with unusual

waveforms.

As an example, see the graphical representation in **Figure 4** of approximating a $\sin(x)/x$ pulse whose first pole lies above the audio range. For this, a sinusoidal signal at a frequency of 10 kHz is selected for one-half period, that is, for 50 μ s. In the case of a burst of pulses (see **Figure 5**) a certain frequency applies to one or more cycles inserted into a quiet of 1 s.

Depending on the measurement, normal replay or loop mode may be selected for the reproduction. Other choices are brown noise, white noise, and pink noise, for which the same processing options may be used.

When the generator function is used at the same time as the soundcard is used for recording (duplex operation), the sampling rates must be the same. Owing to the limited mixing facilities of some soundcards, it is advisable to generate via the right-hand channel and to use a mono configuration during the recording, which automatically causes the recording to be done via the left-hand channel. This arrangement ensures that crosstalk is minimized.

When very clean measurements are needed, it is advisable to use a second card, an external generator, or a second computer with suitable soundcard.

After the desired waveforms have been generated, samples may be picked up with the mouse and placed elsewhere (see **Figure 6**). This gives a wide choice of possibilities to manipulate waveforms or create new signals.

downsampling

Downsampling, that is, 'convert sample type', enables the resolution of spectral measurements to be enhanced greatly.

Measurements taken at a high sampling rates (44.1 kHz or 48 kHz) contain much unnecessary detail if analyses of low frequencies are required (1 cycle at 100 Hz takes about 400 samples). Unfortunately, in FFT analysis the range is divided linearly so that a measurement of 1024 at the lower end of the range leads to coarse steps of about 20 Hz. When the measurements points are then linked, the resultant curve, if plotted on a logarithmic scale, will show a number of 'kinks'.

True, the number of FFT points may be increased to 2^{16} (65536) resulting in frequency steps of only 0.3 Hz, but this has the disadvantage of causing long computation times when a slow computer is used, or the 'scan' function is selected.

The use of downsampling results after anti-aliasing and conversion of the samples in a new waveform from which all high frequencies, except those lower than half the sampling rate, have been

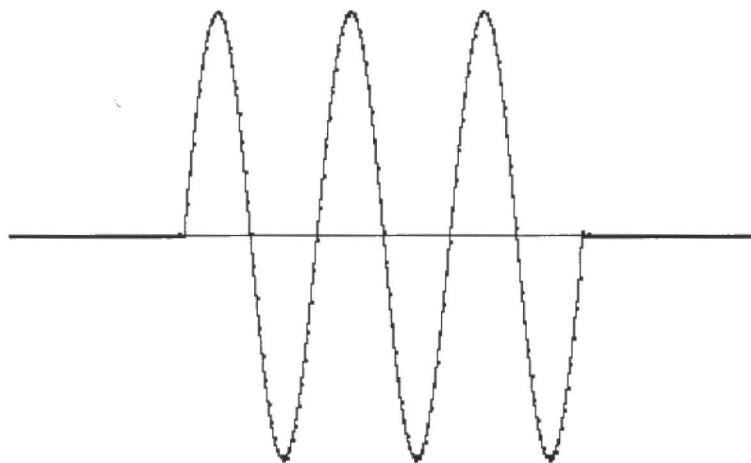


Figure 5. To obtain a burst of pulses, one or more cycles of a given frequency are superimposed on to a quiet of 1 second.

removed. The scale of the spectrum analyser adapts itself to this, so that low frequencies are more clearly displayed.

In this way, a sampling rate of 6000 Hz results in a frequency scale of not more than 3000 Hz, so that in case of an FFT of 1024 points the resolution is 2.9 Hz. In downsampling, there is no obligation to use the sampling rates allocated by the manufacturer, because the soundcard is not really used for the measurements. These are just arithmetical operations that after computation can be represented by a waveform or range of frequencies. Therefore, if downsampling down to 400 Hz or even lower is selected, low frequencies can be read accurately (as required, for instance, during the measurement of a woofer in its enclosure).

transfer measurements with a logarithmic scale

The logarithmic scale enables the user to carry out transfer measurements of which, in contrast to the linear scale, all frequencies can be read clearly. However, the discrete measurement points at low frequencies can be seen, so that for a satisfactory measurement not fewer than 2^{12} (4096) test points are needed. When a very high resolution at low frequencies is wanted, downsampling may be used.

As an illustration, consider an experiment in which three different test signals are applied to a 17 cm woofer (see **Figure 7**). The inputs are measured with the aid of the duplex function of the soundcard, combined with the generator functions in the software, and stored in a file.

All signals were applied to the system at such a level that the linearity was not jeopardized. The soundcard was driven to just below the saturation level (up to 16 bits). The pink noise was converted to white noise via an electronic correction network so as to obtain a real measurement (this would also have been possible with filter setting 'antipink'). After this, the 'scan' function was used for the selected 2 seconds.

In the second case, a linear sweep was applied for half a second, after which the 'scan' function was used to obtain the transfer characteristic.

In the third case, a $\sin(x)/x$ pulse was applied. Since only a single pulse was used, a quiet of a few seconds was measured (test signal removed from the loudspeaker), after which the test signal was applied to the woofer. Additionally, a record was made of the quiet, which was then saved with the functions of 'noise suppression'.

Subsequently, the program computed the statistical content of this signal. The resultant signal was then superimposed

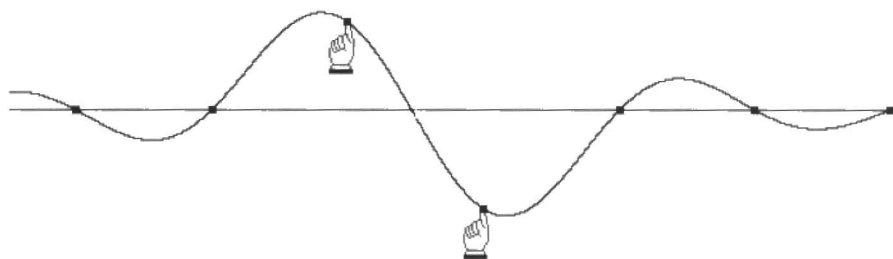


Figure 6. The separate samples may be picked up and relocated with the mouse.

on to the test signal and subtracted to yield a clean test signal. (This method is much faster than that of other systems in which typically 100 measurement results are superimposed on to one another and then differentiated). Afterwards, the time window was superimposed on to the test signal and closed before echoes from the measurement range could distort the measurement result.

As will be seen in Figure 7, the energy content (signal-to-noise ratio) of the pink noise measurement is clearly the highest of the three, followed by the linear sweep. The $\sin(x)/x$ method is the worst as far as energy is concerned. However, this gives more information about the system being tested since spurious reflections from the measurement range are removed (the time window determines the purity of the measurement and the lowest frequency to be measured).

This signal may also be used to analyse the pulse response.

finally

In taking measurements, the knowledge, experience and insight of the operator are just as important as the quality of the hardware: the soundcard, preamplifier, and test microphone.

The facilities of 'cool edit' will, no doubt, be extended and enhanced in future versions. Therefore, any feedback from present users to the manufacturer is of great value. Internet users may obtain more information and an evaluation copy from

<http://www.syntrillium.com>

[972043]

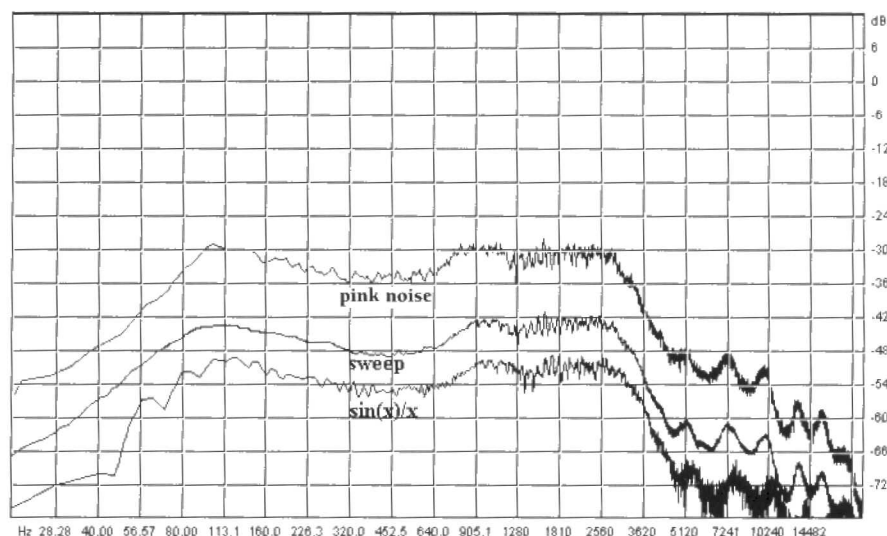



Figure 7. The result of three measurements on a 17 cm woofer with different test signals.

Until not so long ago, triggering was used only in oscilloscopes to make certain parts of a signal visible. With the advent of new measuring instruments, new trigger techniques have had to be developed. Today, apart from in oscilloscopes, special trigger techniques are used in counters, scopemeters, and graphical multimeters. This article discusses several trigger techniques used in modern measuring instruments from Fluke*.

Fluke (UK) Limited

trigger techniques

no longer confined to oscilloscopes

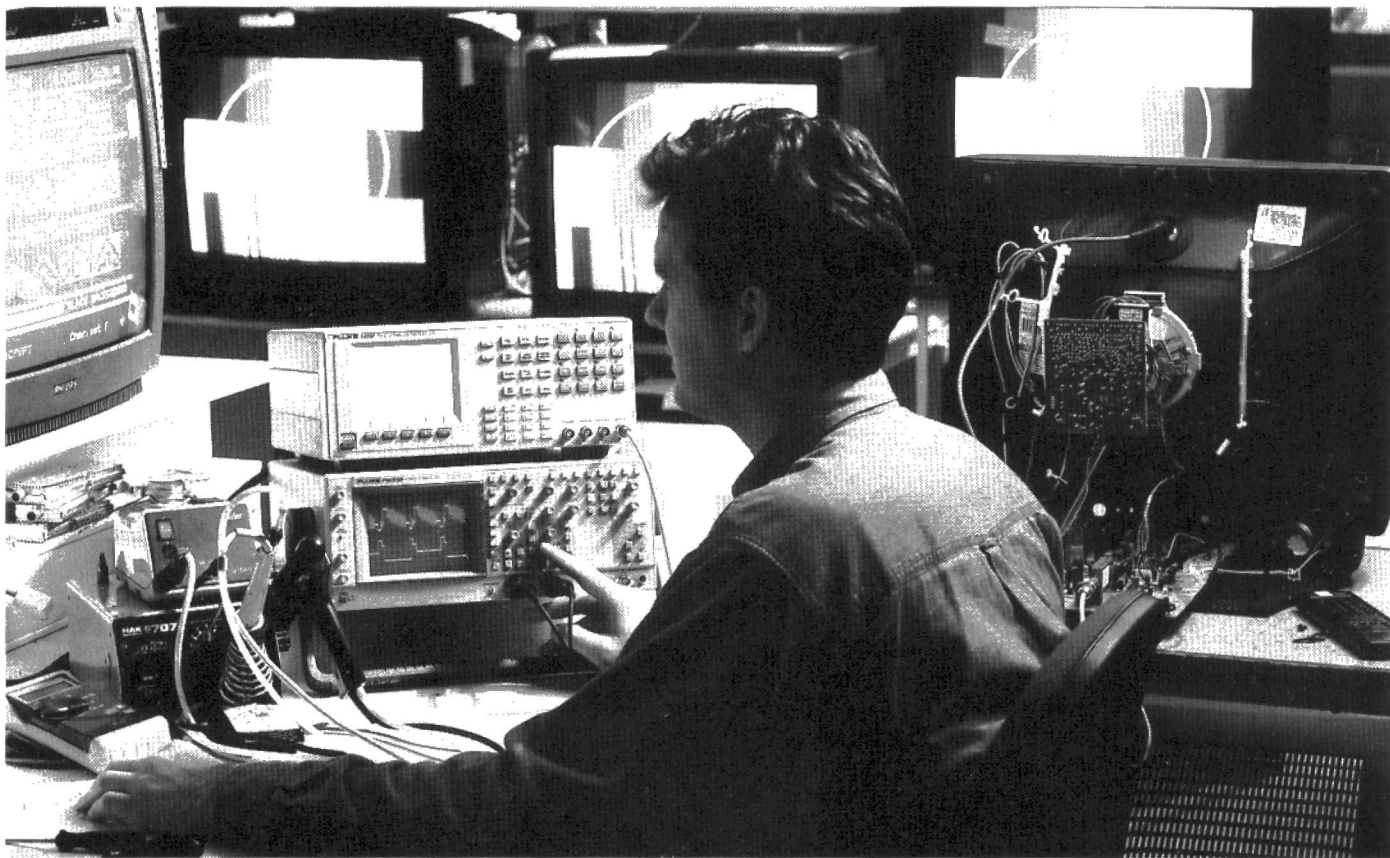

The function of a trigger circuit in a measuring instrument is simply to find a reference point in a repetitive signal at which the time base (that is, the measurement) can be started. The user may add a number of peripheral conditions.

Figure 1 shows basically how triggering is achieved in an analogue oscilloscope. Not only is the voltage level at

which a trigger pulse must be output variable, but the polarity of the signal edges, rising or falling, is selectable. If desired, a hold time may be observed after the trigger point has been reached.

There are variants of the basic trigger circuit that take the type of input signal into account. Even analogue oscillo-

* Fluke (UK) Ltd
Colonial Way
Watford, Herts
England WD2 4TT.
Telephone +44 (0)1923 240511;
Fax +44 (0)1923 225067

scopes are equipped with TVL(ine), TVF(rame), LF-rej(ect), HF-rej(ect) facilities on the trigger control, which enable certain frequencies to be filtered from the signal, so that triggering at other, wanted, frequencies is more readily achieved.

Additional functions are AC and DC coupling with which the direct voltage component in the input signal may be passed or blocked. Because of these functions, the user is able to determine exactly where the time base of an oscilloscope is to be triggered.

digital oscilloscopes

Most digital oscilloscopes feature pre- and post-trigger delay to enable a signal to be analysed at both sides of the trigger point, but the Fluke ScopeMeter has two additional delay modes. The first is delay by events and the second is delay by n cycles.

Consider the latter first. When using an oscilloscope, you will run across waveforms that just will not trigger well. At times, they appear stable, but at other times they jitter across the screen. A typical example of such a signal is shown in **Figure 2**. If triggering would take place at every zero crossing, the result would be a jittery signal in which various waveforms would be superimposed on to one another. In this case, triggering with a delay of n cycles is used. With this, an instruction is given to wait for n cycles before another trigger pulse is given. If in Figure 2 $n = 3$, triggering will take place at identical pulses.

Meters that are used for the analysis of automotive electronics systems often have to cope with complex repetitive signals in which, for instance, each 4th, 5th, 6th or 7th pulse is missing. Here also, the n -cycle trigger mode comes to the aid of the user, because there is a risk that automatic triggering (autoset) will lead to chaos. The delay with this mode renders the image stable again. For instance, if the 4th pulse is missing, choose a delay of 3 cycles.

In the event mode, use is made of two input signals: the master trigger and the event trigger, which is used to increment an event counter. In this mode, it is, of course, the intention that the two signals are in some way related to one another. A rather similar situation occurs when the armature voltage of a motor is connected via an attenuator box to a generator.

Therefore, the measuring instrument can be informed that the master trigger is enabled only after a certain number of events has taken place. This com-

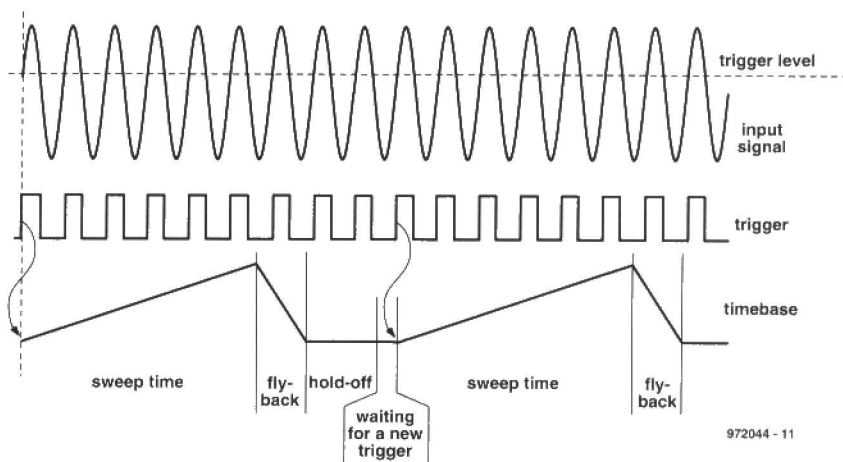


Figure 1. Triggering is a central function in an oscilloscope. Today, trigger circuits are also found in some multimeters and counters.

plex and relatively tedious way of triggering may be used in exceptional cases to obtain a stable image on the screen.

peak detector

The input voltage in a digital oscilloscope is sampled by an analogue-to-digital converter (ADC), which at pre-

determined intervals measures and quantizes the value of a voltage. Provided that the sampling rate is high enough, it is possible to reconstruct a signal. Normally, at least 5–10 samples per input cycle are needed to obtain an acceptable representation of the input waveform.

The only problem that remains is that spikes (very short pulses) remain unde-


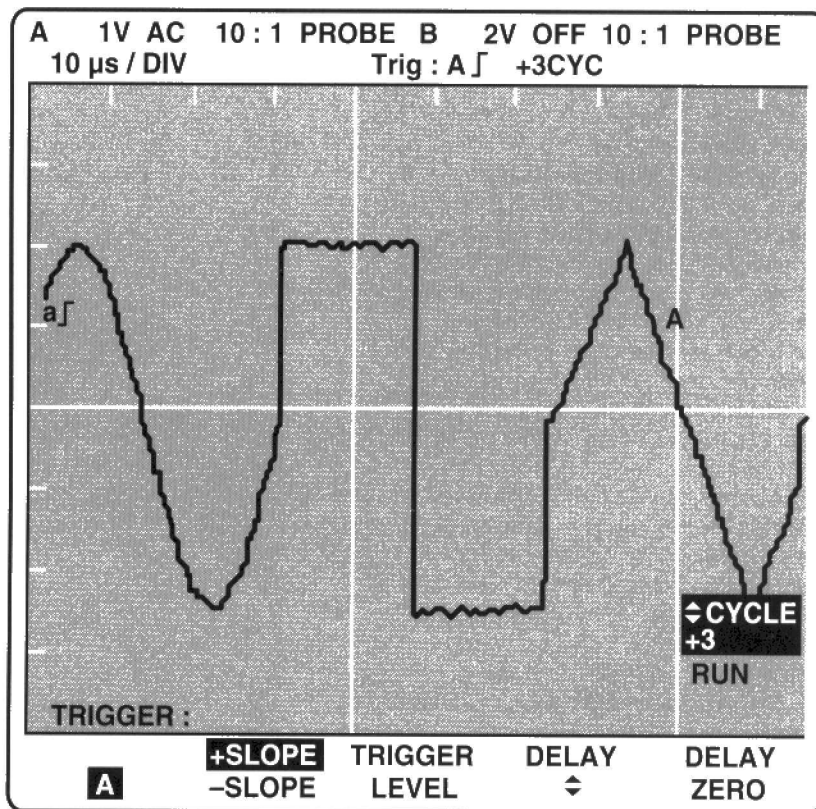


Figure 2. The n -cycle function enables the display of complex, repetitive signals on the screen. Spurious signals are ignored.

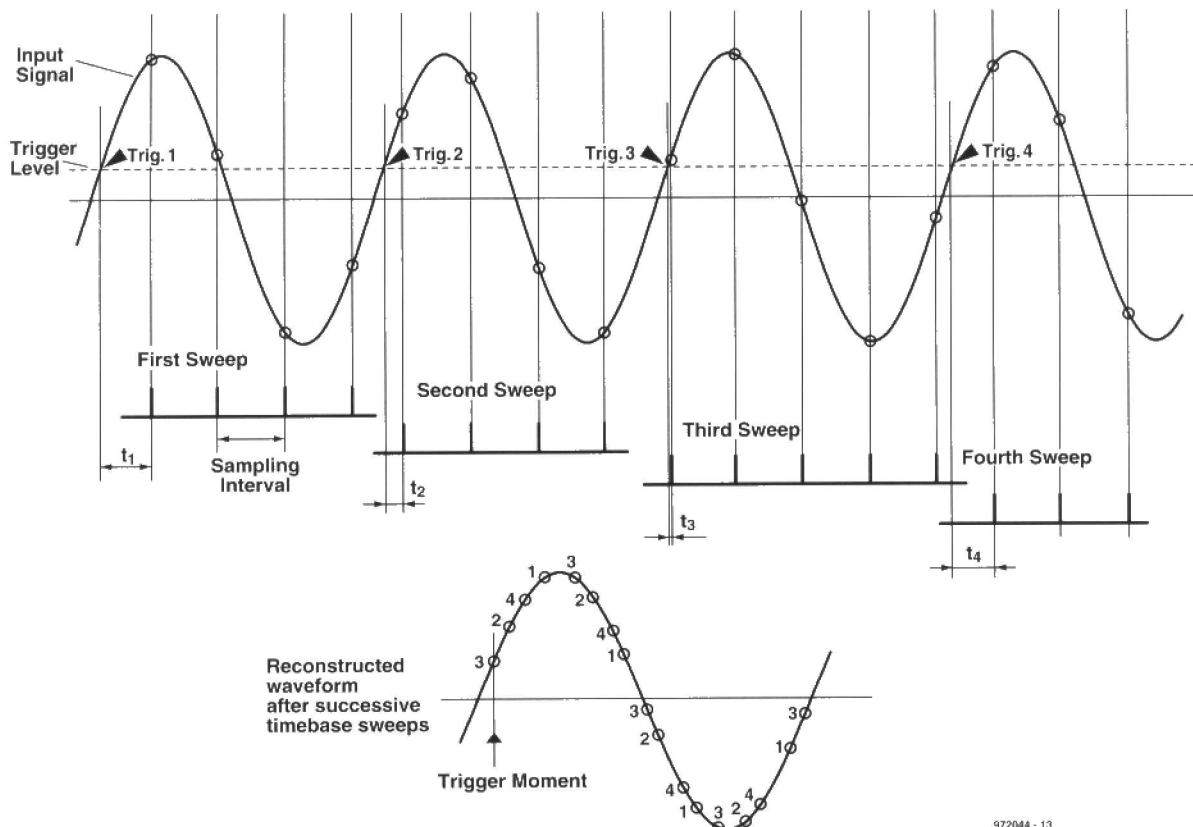

972044 - 13


Figure 3. Repetitive sampling of a periodic quantity makes high sampling rates possible.

tected. If these occur between the samples taken, they will not be visible on the screen. This problem is obviated in a modern oscilloscope by a good-quality digital peak detector. This circuit samples the signal at a high rate, say, 200 megasamples s^{-1} , which gives a resolution of 5 ns.

Using repetitive techniques on a stationary signal in which additional measuring points are gathered, an equivalent or effective sampling rate of one or several gigasamples s^{-1} is possible (see **Figure 3**). This means that the time resolution is of the order of 1 ns. The limited memory depth in which samples are stored means that this high resolution is only possible at the fastest timebase setting. At lower timebase settings, the sampling rate is reduced to a value at which the memory can store all the samples corresponding to that time base setting. A limitation of repetitive sampling is therefore that signals with a low duty factor, particularly narrow pulses, are difficult to analyse, unless the earlier mentioned peak detector is used.

counters, a case apart

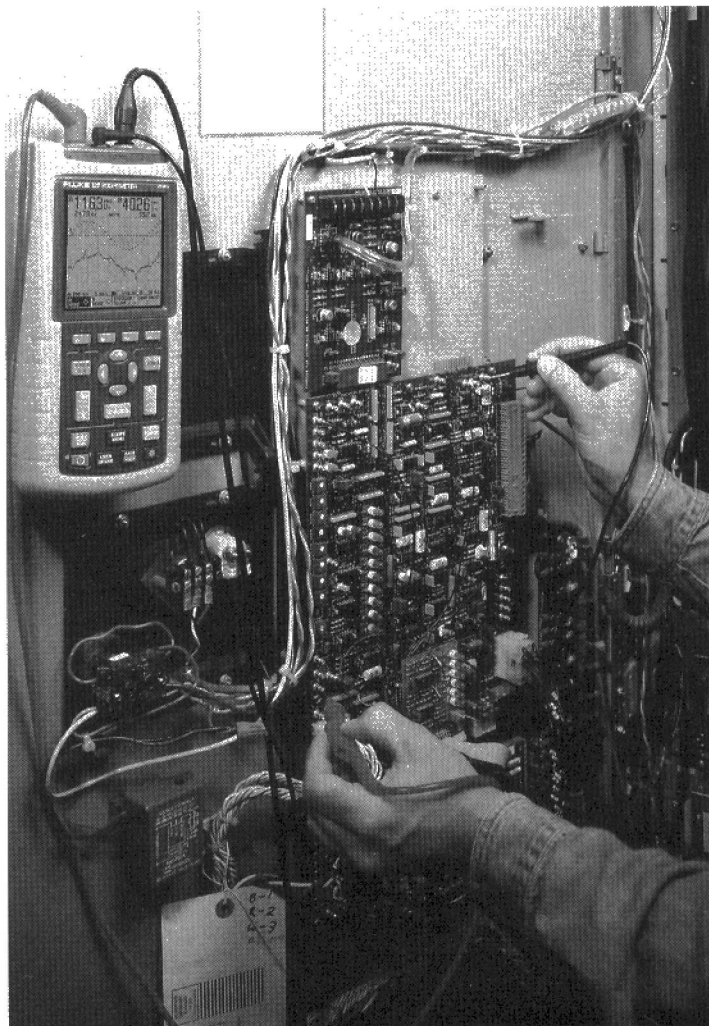Today, oscilloscope functions are integrated not only in graphic multimeters, but also in multifunction counters. Such a counter measures multiple time inter-



vals, all running from a unique start trigger point of the signal to several stop trigger points at various trigger levels. The stop trigger point is incrementally scanned over the input signal. The multifunction counter then measures the successive time intervals.

Interesting examples of such counters are contained in the Fluke 160 Series of MultiFunction Counters. Where in an oscilloscope a test signal is sampled horizontally, that is, in the time domain, in these counters sampling takes place vertically, which is called voltage sequential sampling. In this, the time intervals between different voltage levels are measured. The resolution of the measured time interval is always <1 ns; not just at the fastest timebase setting as with traditional DSOs. The magic here is that vertical sampling inherently produces a sampling density over time that depends on the need to capture signal variations.

See **Figure 4** for a comparison of the two modes of sampling.

The designers of the counter have turned the world through 90° to better digitize timing signals. Although this technique appears expensive since use cannot be made of standard components, part of the extra cost of the requisite trigger and sampling circuits is compensated by the much simpler design of the display driver circuits.

In vertical sampling, a large number of trigger levels are used and measurements taken of the time intervals when a given trigger level is exceeded or not met. For this it is necessary to use a repetitive signal so that multiple measurements, each at a different trigger level, can be taken.

The interesting point about this technique is that by definition time intervals are measured that match the parameters of the input signals. If no signal variations occur, for instance, at the flat top of a pulse, no sampling takes place. In other words, samples are taken and stored only if they contain factual information.

A dot joiner is used to connect two measurement points on the screen to render the constant voltage visible.

The output signal in vertical sampling is a two-dimensional array that contains a number of measurement points that describe the waveform. Each point in the array contains information as to time (x coordinate) and as to the signal level (y coordinate).

The resolution of the voltage measurements, depending on the setting of the internal attenuator, is 1, 10, or 100, which is more than sufficient for most applications.

It is clear from the foregoing that this trigger and sampling technique is eminently suitable for the detection and measurement in an inexpensive manner of narrow pulses and glitches in repetitive analogue and digital input signals, such as in a counter. Another application where this is of great use is in the calibration of radar pulses. Such pulses are $1 \mu\text{s}$ wide and have a PRF (pulse repetition frequency) of 1 ms, resulting in a duty factor of 1:1000.

connect and view

The 'autoset' function in modern analogue and digital oscilloscopes has simplified triggering immensely. When this function is selected, the incoming signal is analysed and disassembled into its constituent components. On the basis of this, the optimum setting is selected automatically.

In the latest generation of Fluke's scopemeters, this function has been enhanced by the addition of 'connect and view'. This automatically ensures

that as soon as a signal is applied to the input terminals an autoset instruction is given. Any change in the input signal automatically actuates a new autoset instruction.

This facility enables the triggering of signals at frequencies down to 1 Hz. Its chief advantage is that no control needs to be touched to obtain good plots of the signal on the screen. This is especially useful when measurements are taken in difficult conditions.

[972044]

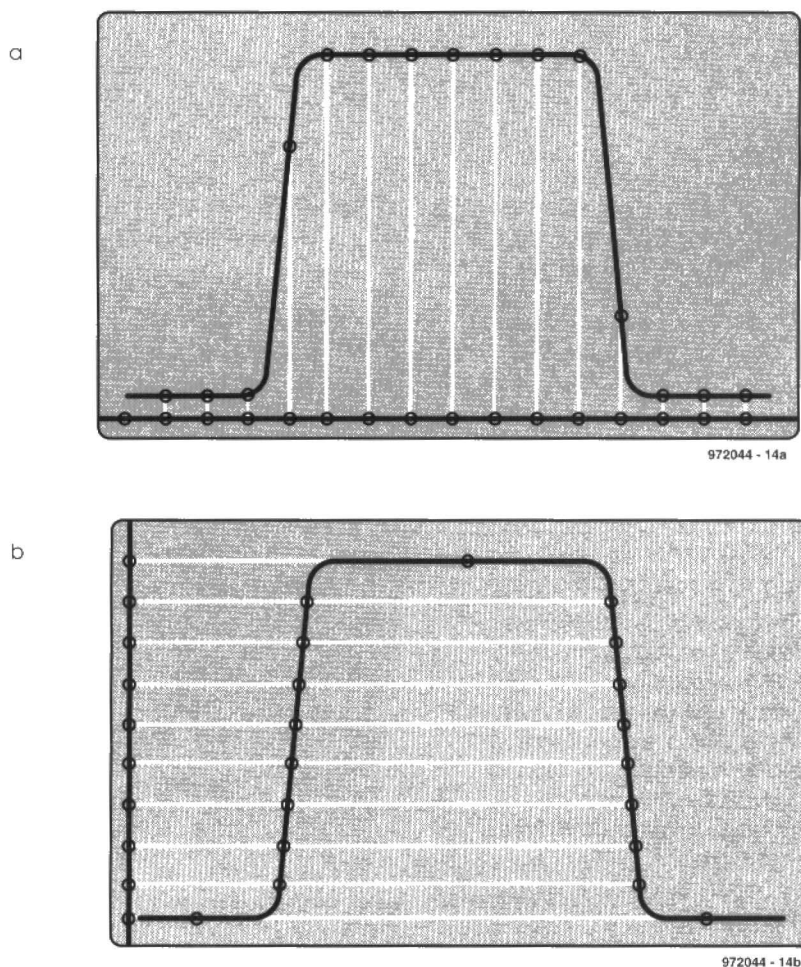


Figure 4. Comparison of (a) conventional horizontal sampling, and (b) vertical sampling.

"ASCOPE" is a computer program that enables the transfer of asynchronous signals between two pieces of equipment to be monitored and, if required, saved for later analysis. In this, use is made of the standard serial port(s) COM₁ and COM₂ of the PC. Other than a simple test cable, no specific hardware is needed.

By J. Clerx

"ASCOPE"

measuring analogue signals with a PC



the screen. The program is written largely in Turbo C from Borland. Only a few, time-critical, routines are in assembler (MASM).

properties of the program


Facilities provided by, and properties of, the program are as follows.

- Simple operation via selection of

There are not many simple aids available for monitoring digital traffic over serial links, such as an RS232 link. In this article, an IBM compatible PC is considered of which one serial port is connected to the unit whose signals are to be controlled or inspected. If a second serial port is available, this may also be used to enable the traffic in both directions to be monitored.

The test cable is a very simple adjunct (see **Figure 2**).

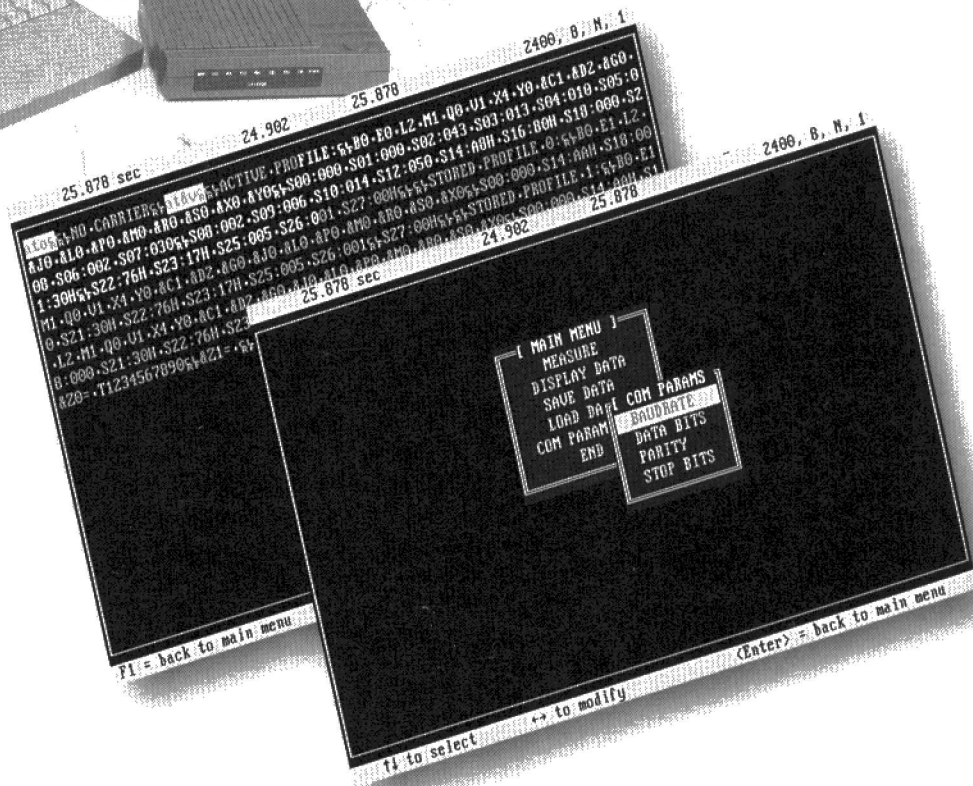ASCOPE (acronym for asynchronous oscilloscope) is a DOS program specially written for this application. It arranges the correct test settings and the display of the measured signals on



menu-listed items.

- During the measurement there is an indication of the time, in seconds, elapsed since the onset of the measurement cycle.
- Simultaneous measurement in two directions. The direction is indicated by 'normal' or 'negative' colour display on the screen.
- For each character, in both directions, the time is registered with a resolution of 1 ms.
- Control characters, such as STX (start of text), ETX (end of text), LF (line feed), etc., are displayed by means of an adapted character set.
- The measured data may be analysed after the measurement has been completed. The cursor may be moved freely through the measured data with the aid of PgUp, PgDn, and the arrow keys. The time of registration is displayed at all times with a resolution of 1 ms.

Cyclical buffers ensure that the last measured characters are retained for further analysis.

Data may be saved under an arbitrarily chosen name.

- Start and stop markers may be placed to enable only the important parts of information to be saved.
- Earlier saved data are available for analysis at all times. Markers may be placed on these to enable only those of interest to be recalled for a future analysis.
- Parameters such as baudrate, parity, number of databits and number of stopbits may be set via the menu.
- Status lines at the top and bottom show a number of data, such as available keys.

operation

The program is started simply by the instruction

ASCOPE <enter>, whereupon the first window with general information appears. Pressing a key causes the main menu to be displayed. The arrow keys enable the desired selection to be made and executed via <enter>. The choices then available are as follows.

Measurement

When 'measurement' is selected, the measurement is started. However, if there are data in the buffer that have not yet been saved, a message is displayed asking whether these data should be saved for later use.

When the measurement is started, each character that passes the measurement line is immediately displayed

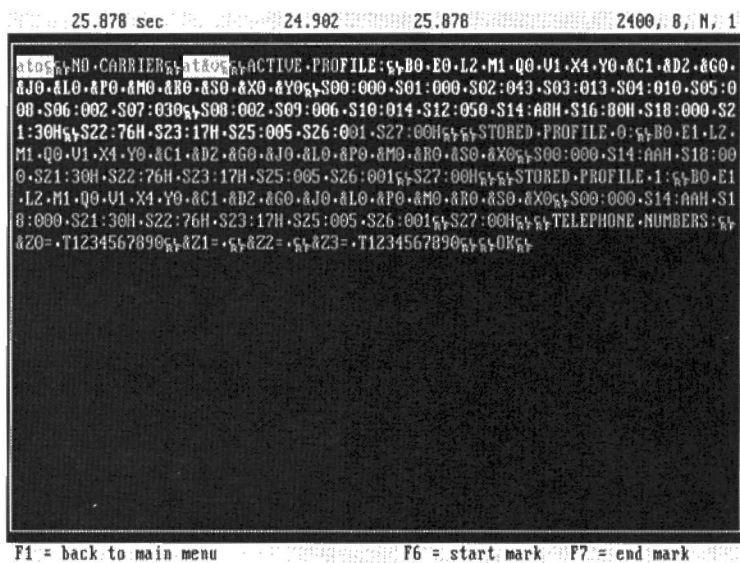


Figure 1. The "ASCOPE" program measures asynchronous (RS232) signals and displays them on the screen of the monitor. Afterwards, they may be saved as a data file.

on the screen. The direction of the data stream determines the kind of display (normal or high intensity).

The correct setting of the parameters is described in COM parameters later on. The appropriate value of the parameters is shown at the right-hand side of the upper status bar.

New data are constantly added at the bottom, while older ones are removed from the screen when this is full by scrolling.

Measurements are ended when the F1 key is pressed, whereupon the main menu is displayed again.

Display data

When display data is selected, the data that are in the buffer (via Measurement or Load data) are displayed. The cursor may be moved through these with PgUp, PgDn and the arrow keys.

The upper status line shows the time, in seconds and milliseconds, of the first character in the buffer, the last character in the buffer, and the character on which the cursor is placed. This may be very useful when it is desired to measure the exact response times in the communication between the two

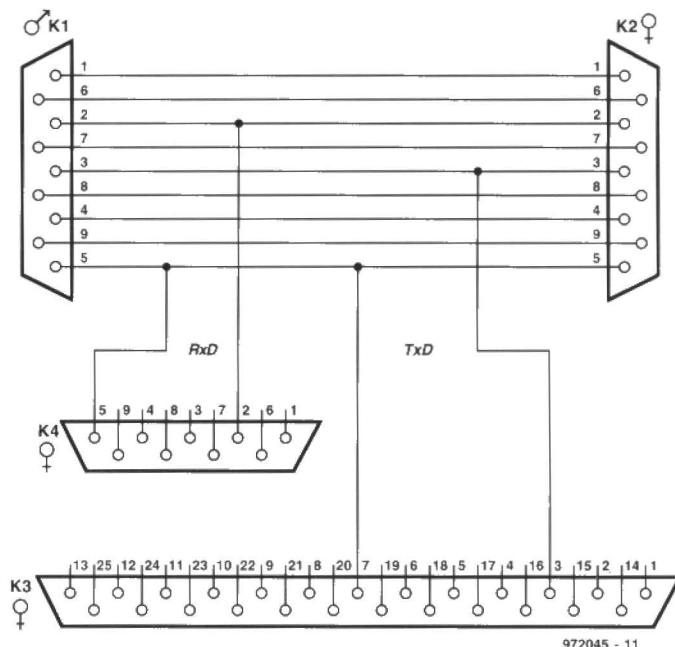


Figure 2. Construction of the test cable. See Figure 3 for other types of connector.

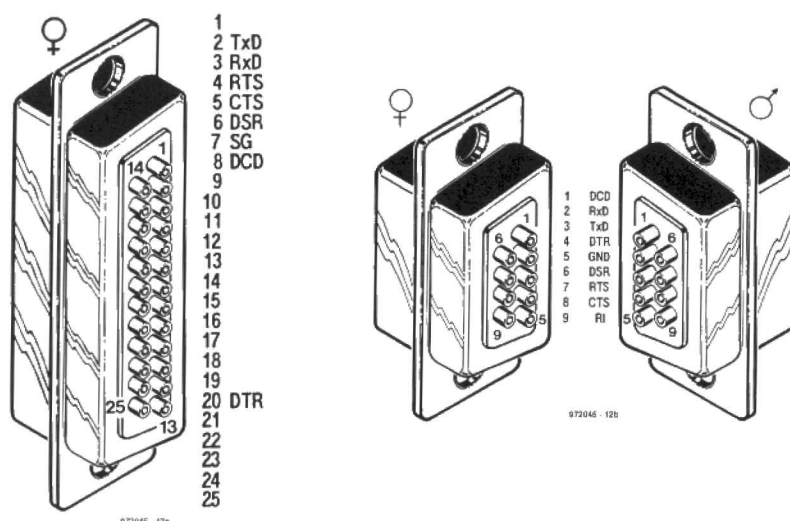


Figure 3. Pinouts of a 9-pole and a 25-pole RS232 connector.

pieces of equipment.

A certain portion of the data may be marked. To do this, place the cursor at the beginning of the portion to be marked and press F6. Then, place the cursor at the end of the portion of the data to be marked and press F7. The portion so marked is shown markedly different. When these data are saved (see 'save data'), only the marked portion will be saved.

Pressing F1 reverts to the main menu.

Save data

With 'save data' selected, it becomes possible to save information contained in the buffer. The name, and if desired, the name of the disk and name of the

pad, have to be entered. If a portion of the information has been marked, only that portion will be saved.

Load data

When 'load data' is selected, data already on the disk will be loaded anew. Apart from the name of the data, the name of the pad and that of the disk on which the data is stored may be entered.

COM parameters

When 'COM parameters' is selected, a submenu will be displayed. This contains the various parameters that are to be set in accordance with the settings of the signals on the link which are to be measured. This means that the baudrate, the

number of data bits and stopbits, as well as the parity setting must be known. Selection is made with the keys marked with the up and down arrows; modifications are made with the keys with left-hand and right-hand arrows. The selected value is shown at the upper status bar. The submenu is replaced by the main menu with <enter>.

End

When 'end' is selected, the program is terminated.

hardware needed

To use the datascope, a PC and a suitably adapted test cable terminated in Sub-D connectors are required.

When a PC has two serial ports, one of these normally has a 9-pole connector and the other a 25-pole connector. It is obviously advisable to use one type of connector for the two measurement links (both female). The interconnecting cable is provided with a male and a female connector, so that it can always be used as an extension cable.

It is also possible to use an adaptor of which a variety of different kinds is available. The adaptor is inserted between one of the pieces of equipment and the cable. The link to the measurement PC is via this adaptor. The adaptor may be 9-pole-to-25-pole or vice versa to adapt the cable for the kind of measurement to be carried out.

The "ASCOPE" program can be found on the CD-ROM *Electronics software 96-97*, Order no. 976003, available through our Readers Services found towards the end of this issue. The relevant files are found in NL/23.

19/2045

B.BAMBER ELECTRONICS

Tektronix Oscilloscope Type TDS350, Dual channel, 200mhz, 1GS/s.	£2200.00
Philips Oscilloscope Type PM3217, Dual channel, 50mhz.	£350.00
Laplace Spectrum Analyser Adaptor Type SA450B, for use with a low frequency oscilloscope to display signals from 10 khz to 450 mhz.	£320.00
Black Star Orion PAL TV/VIDEO colour pattern generator, output RNC.	
and DIN switchable to 1V or TTL. Band 111. UHF Bands 1V and V.	£185.00
Black Star Meteor 600 mhz frequency counter, mains and battery.	£95.00
Thurby Thandar 1.3ghz frequency counter Type TF820.	£95.00
Iwatsu Oscilloscope Type SS5121, Dual channel, 100mhz.	£450.00
Farnell Tripple output power unit Type TOPS3D, 4-6v at 4A, 5-17v at 1A.	£120.00
Time DC Voltage Calibrator Type 2003S.	£250.00
Time DC Current Calibrator, 0 - 10mA.	£250.00
Marconi AF Oscillator Type TF2102M, 3hz - 30 khz.	£75.00
Kingshill Power Unit Type NM10300, 100vdc at 3A.	£95.00
Avo AC/DC breakdown leakage & Ionisation Tester Type RM215-L2.	£400.00
Image Powerverse mains analyser.	£600.00
Avo Megohmmeter Model RM290.	£220.00
Weir Bench Power Units Type 460, 0-60v at 1A.	£70.00

FREE DELIVERY, NO V.A.T.

DON'T MISS OUR MONTHLY SURPLUS SALE CATALOGUE OF EQUIPMENT AND COMPONENTS CALL NOW!

5 STATION ROAD, LITTLEPORT, CAMBS. CB6 1QE
PHONE: (01353) 860185 FAX: (01353) 863245



IF AN ADVERT IS WRONG, WHO PUTS IT RIGHT?

We do. The Advertising Standards Authority ensures advertisements meet with the strict Code of Advertising Practice. So if you question an advertiser, they have to answer to us.

To find out more about the ASA, please write to Advertising Standards Authority, Department X, Brook House, Torrington Place, London WC1E 7HN.



This space is donated in the interests of high standards in advertisements.

radar-controlled door opener

This article provides suggestions and other useful data to help you design a door or lock opener system based on a ready-made X-band (10-GHz) radar module. Movement of any object or person within the radar's range is detected using the Doppler effect and a simple evaluating circuit which controls a relay.

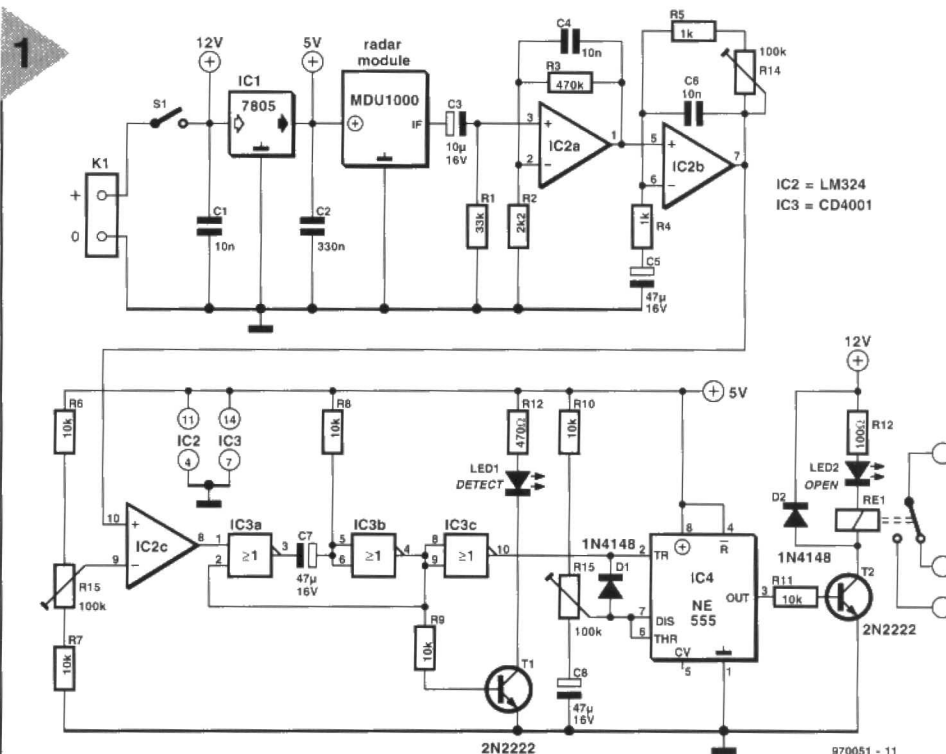


Figure 1. Circuit diagram of the radar-controlled door opener.

PRINCIPLE OF OPERATION

The microwave detector which provides the switching information for the door opener is a volumetric radar designed to detect persons or objects within a specified area. On detecting anything that moves within its range, the system energizes a relay which, in turn, opens a door or provides access in another way.

The radar module used here is a Doppler type operating in the X-band (3cm, 10-GHz). In theory, the unit is capable of measuring object velocity between 50m/h (approx. 14cm/s) and 500km/h. Electronic evaluation of the (Doppler-shift) output frequency supplied by the radar module enables the system to reliably detect walking or running persons, or moving objects (like a car on the garage driveway).

In terms of sensitivity and reliability, the performance of this type of detector is superior over that of PID (passive infra-red) detectors because it is not in the least affected by fog, rain, darkness or intense sunlight. Also, thanks to the fact that microwaves tra-

verse many materials like (plain) glass, wood and ceramics, without appreciable attenuation, the unit can be mounted out of sight, which is not normally possible with PIDs.

CIRCUIT DESCRIPTION

The complete circuit of the radar-controlled door opener is given in Figure 1. The heart of the circuit is the microwave radar module Type MDU1000. The Doppler-shift signal supplied by its IF (intermediate frequency) is first filtered by R1 and C3 which help to eliminate low-frequency components. Next, the signal is amplified by two opamps with respective gains of $210 \times$ (IC2a) and $1-100 \times$ (IC2b). The latter gain is adjusted with preset R14, and determines the detection range of the system. In the opamp amplifiers, capacitors C4 and C6 provide some bandwidth limiting by passing high-frequency components. An electrolytic capacitor, C5, in the second opamp stage serves to decouple the d.c. component.

The detection sensitivity of the system is adjusted with preset R15 which controls the bias at the - input of the third opamp in the circuit, IC2c, which is wired as a comparator.

If a significant Doppler shift occurs, the output of IC2c swing high and enables a monostable multivibrator (MMV) built from two of the four gates in IC3 to generate a 'person detected' pulse with a length of about 0.5 s. The delay, T , is expressed as

$$T = 1/(R8 \cdot C7) \quad [s]$$

The resulting control pulse at the output of gate IC3b causes driver transistor T1 to be switched on, so that the green 'detect' indicator LED1, lights.

The same pulse is inverted by IC3c, triggering a second (this time re-triggerable) MMV, IC4. The good old NE555 used in this position controls the 'on' time of relay Re1 via driver transistor T2. This time may be set to any value between 0.5 s (not very useful, we reckon, except of course to let the RoadRunner in, or a very fast cat) and about 5 s. The relay contact is used to switch on the door opener motor. A red indicator, LED2, lights when the motor is switched on.

The signal processing electronics

are powered from a regulated 5-volt rail provided by a 7805 voltage regulator. The relay is powered by the unregulated 12-V voltage.

The total power consumption of the system is about 80 mA.

DESCRIPTION OF THE RADAR MODULE

The MDU1000 supplies a transmit power of about 13 decibel-milliwatt (dBm), or 20 mW. The IEEE C95.1-1991 standard specifies a maximum exposure level of 7 mW/cm² at a frequency of 10 GHz. At a distance of 1 m from the face of the MDU1000 radar module, the radiation level will be about 0.72 μ W/cm², or about 10,000 times lower than the norm.

The distribution of the transmitter power in the horizontal (H) and vertical (E, elevation) planes is shown in Figure 2. Note that the indicated power levels are relative, i.e. 0 dB in the graph corresponds to the maximum transmitter power of +13 dBm. The side lobes in the H-plane are normal for a microwave exciter designed for wide radiation in the X-band, i.e. without a WG16 waveguide flange. The -3-dB (half-power) angles are 36° and 72° for the H and E plane, respectively.

The detection threshold (sensitivity) of the receiver inside the MDU1000 is specified at -86 dBm by the manufacturer. This threshold (specified in dBm relative to an isotropic antenna) is shown as the straight line in Figure 3. Theoretically, a sensitivity of -86 dBm gives a radar range of 20 m. In practice, however, this figure will be derated to 15 m or so.

As shown in the mechanical drawing in Figure 4, the MDU1000 radar module is pretty flat and compact. There's nothing to adjust on the module, which has only three connections, IF out, +5 V and ground.

FINAL NOTES

According to the author, the MDU1000 Doppler radar module, as well as a complete kit of the system described here, are available from Saphir SARL, 9 Rue des Myosotis, F-94320 Thiais, France. Tel./fax (+33) 1.48.52.78.92.


A possible replacement for the MDU1000 is a microwave sensor from Conrad Electronics, order code 1081 11-99. Note that this replacement was not tested by the author.

Warning.

The installation and use of low-power X-band microwave radar systems for person detection like the one described here may be subject to radio and/or health regulations applicable in your country. In the UK, contact the DTI for further information.

(970051-1)


2

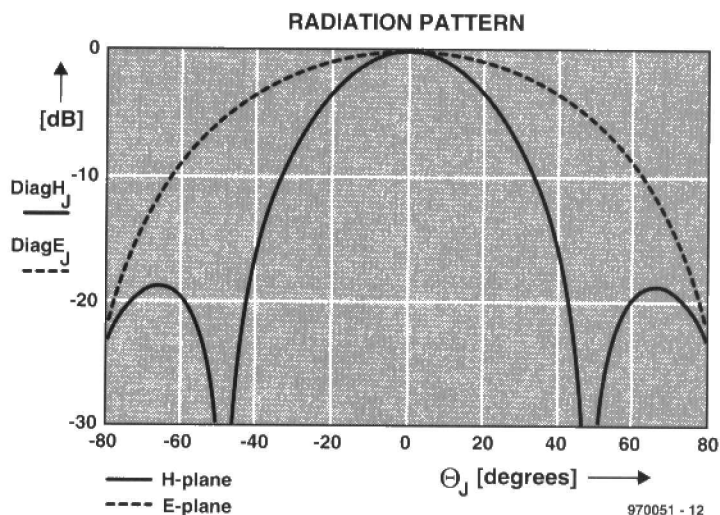

970051 - 12

Figure 2. Radiation patterns of the MDU1000 in the horizontal (H) and elevation (E) planes.

3

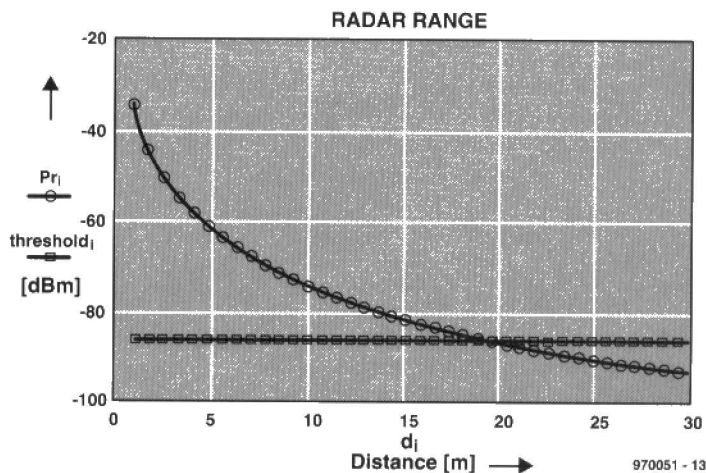


970051 - 13

Figure 3. At a sensitivity of -86 dBm, the radar module has a theoretical range of 20 m.


Figure 4. Mechanical outline of the MDU1000 X-band radar module.

4

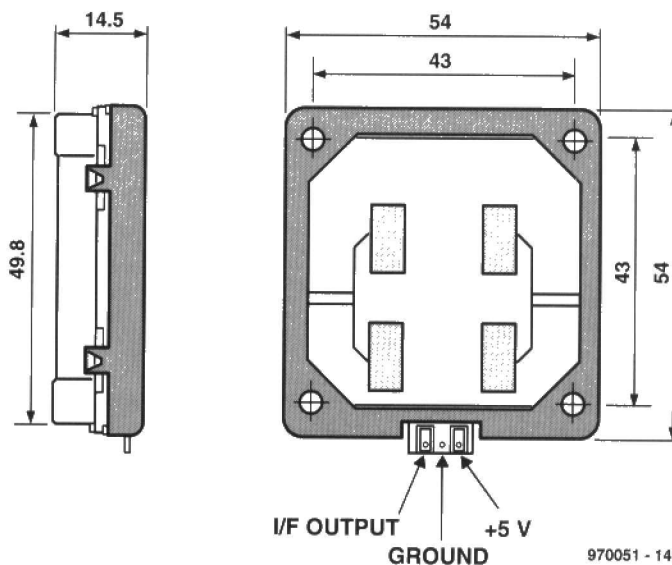

970051 - 14

digital signal processing

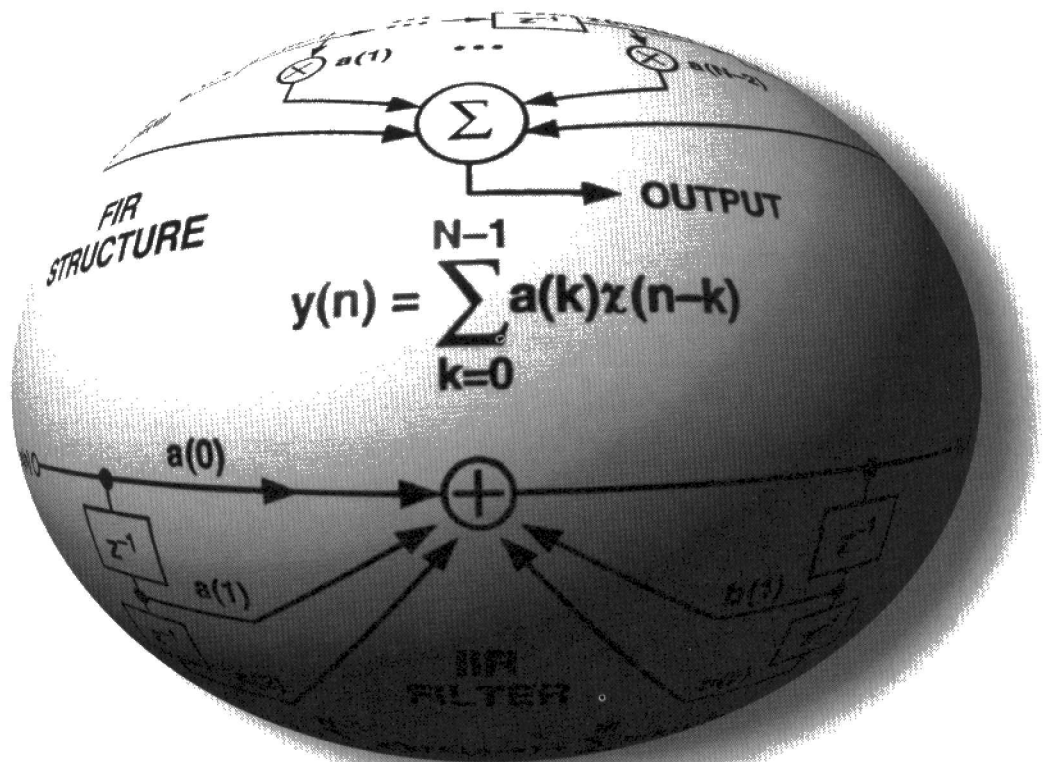

Digital signal processors (DSPs) are used in many modern electronic systems to process analogue signals digitally. In essence, the hardware, software, and instruction sets of these devices are optimized for high-speed numeric processing tasks. In this article*, the design considerations for developing a DSP system are considered.


*This article is based on parts of 'Why use DSP' by D Skolnick and N Levne which originally appeared in *Analog Dialogue*, Vol. 31, Number 1, 1997, published by Analog Devices.

INTRODUCTION

To get an idea of the functioning and possible applications of a digital signal processor – DSP – it is instructive to compare an analogue and a digital circuit on the basis of a filter function.

An analogue filter is built from resistors, capacitors, inductors, and possibly active elements such as an operational amplifier – op amp. Such a filter is inexpensive and easily assem-

Figure 1. An ideal bandpass filter and second-order approximations.

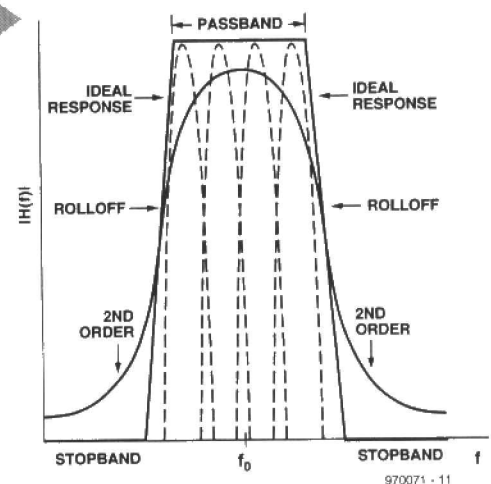

By our editorial staff

bled but difficult to calibrate, modify, and maintain, and this difficulty increases exponentially with filter order. The use of a digital signal processor is therefore advisable in many instances. Such a processor enables a virtual filter to be effected by means of software. Such a filter is more flexible, easily repeated and more reliable than an analogue one. A further advantage is that if a higher order is desired, this affects the software only. In contrast to discretely built filters, the hardware remains unaltered.

As a practical example, consider an ideal bandpass filter. Such a filter has a frequency vs amplitude characteristic as shown in Figure 1. The response within the passband would be flat with zero phase shift, and in the stopbands there would be infinite attenuation. Useful additions would include passband tuning, bandwidth control, and stopband rolloff control.

It is clear from the characteristic that an analogue design would require a number of staggered 2nd-order high-Q sections. The tuning and adjusting of these would present great difficulties.

FILTER WITH DSP

With digital signal processing software, there are two basic approaches to filter design: the finite impulse response (FIR) and the infinite impulse response (IIR). The functional layouts of the two types of filter are shown in Figure 2.

The FIR filter's time response to an impulse is the straightforward weighted sum of the input signal and a finite number of previous samples. Since there is no feedback, the filter's response to a given sample ends when the sample reaches the 'end of the line'. An FIR filter's frequency response has no poles, only zeros.

By comparison, an IIR filter is called infinite because it is a recursive function, that is, its output is a weighted sum of the inputs and outputs. Since it is recursive, its response can continue indefinitely. An IIR filter's frequency response has both poles and zeros.

In Figure 2, x represents the input samples, y the output samples, a the input sample weighting, b the output sample weighting, n the present sample time, and M and N the number of samples programmed, that is the filter's order. Note that the arithmetic operations indicated for both types are simply sums and products. In fact, multiply-and-add is the case for many DSP algorithms that represent mathematical operations of great sophistication and complexity.

Approximating an ideal filter consists of applying a transfer function with appropriate coefficients and a

2

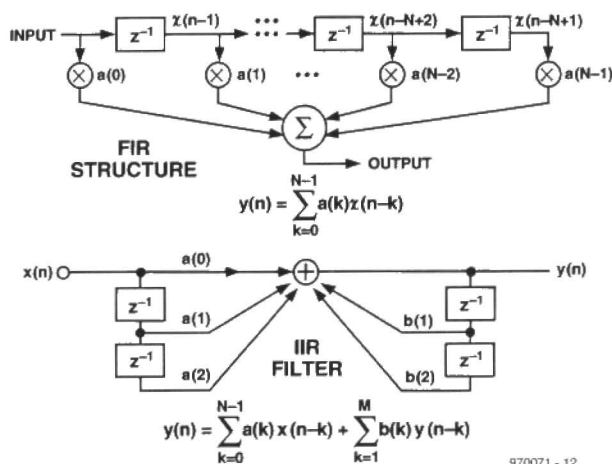


Figure 2. Filter (both FIR and IIR) equations and delay-line representation.

high enough order, or number of taps (considering the train of input samples as a tapped delay line).

Figure 3 shows the response of a 90-tap FIR filter compared with sharp-cutoff Chebyshev filters of various orders: 2, 4 and 6. The 90-tap example suggests how closely the filter can approach the ideal. Within a DSP system, programming a 90-tap FIR filter, like that in Figure 3, is not difficult. By comparison, attempting this level of approximation would be a very tedious affair. A further bonus of the use of a DSP to approximate the ideal filter is long-term stability.

REAL-WORLD SIGNALS

Real-world signals are analogue – the continuously changing energy levels of physical processes like sound, heat,

light, electricity, magnetism. A transducer converts these levels into manageable electrical voltage and current signals, and an analogue-to-digital converter (ADC) samples and converts these signals to digital bits for processing. The conversion rate, or sampling frequency, of the ADC is critically important in the digital processing of real-world signals.

The sampling rate is determined by the amount of signal information that is needed for processing the signals adequately. In order for an ADC to provide enough samples to accurately describe the real-world signal, the sampling rate must be at least twice the highest-frequency component of the analogue signal. For example, to accurately describe an audio signal containing frequencies up to 20 kHz, the sam-

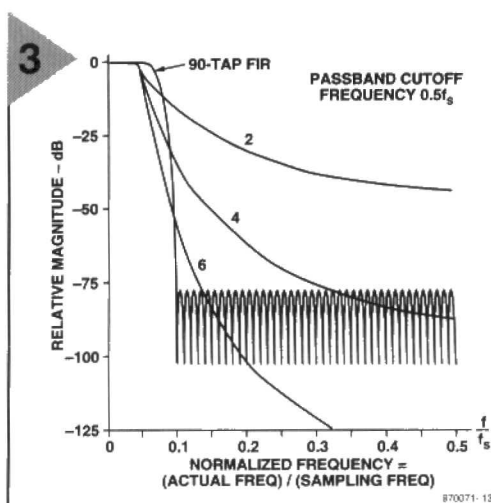


Figure 3. Filter response of sharp cutoff Chebyshev filters compared with that of a 90-tap FIR filter.

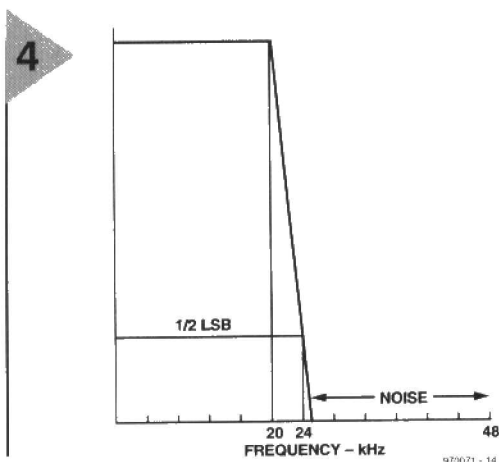


Figure 4. Response of an ideal anti-aliasing filter.

pling rate must be not less than 40 kHz. Since arriving signals can easily contain component frequencies above 20 kHz (including noise), they must be removed before sampling by feeding the signal through a low-pass filter ahead of the ADC. Since this filter, known as an anti-aliasing filter, has a finite frequency rolloff, additional bandwidth, say 2–4 kHz, must be allowed for the filter's transition band. This means that in practice the sampling rate must be higher by this bandwidth than the theoretical double value.


Figure 4 depicts the filter response needed to reject any signals with frequencies above half of a 48 kHz sampling rate. Rejection means attenuation to less than 1/2 least-significant bit (LSB) of the ADC's resolution. The curve in Figure 4 reaches this level at about 24 kHz. One way to achieve this level of rejection without a highly sophisticated analogue filter is to use an oversampling converter, such as a sigma-delta ADC. This typically obtains low-resolution (e.g., 1 bit) samples at megahertz rates – much faster than twice the highest frequency component – greatly easing the requirement for the analogue filter ahead of the converter. An internal digital filter restores the requisite resolution and frequency response.

PROCESSING

REAL-WORLD SIGNALS

Once the system bandwidth requirements and the sampling rate have been established, a suitable DSP must be chosen. Since there are a number of these devices on the market, what are the necessary parameters?

Figure 5. (a) Example of continuous processing of samples in a digital filter; (b) Example of batch processing of a block of data.

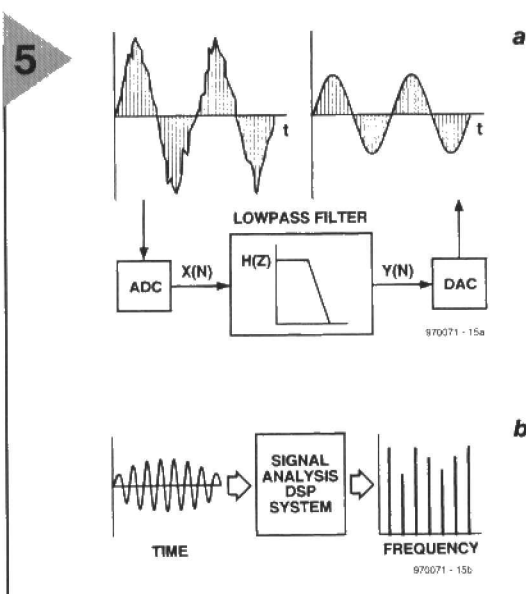

Processing speed at a required sampling rate is influenced by algorithm complexity. As a rule, a DSP needs to finish all operations relating to the first sample before receiving the second sample. For instance, a 48 kHz sampling rate corresponds to a 20.833 μ s sampling interval.

Next, consider the relation between the speed of the DSP and the complexity of the algorithm (that is, the software containing the transform or other set of numeric operations). Complex algorithms require more processing tasks. Because the time between samples is fixed, higher complexity calls for faster processing.

For example, suppose that the algorithm requires 50 processing operations to be performed between samples. Assuming a sampling rate of 48 kHz (sampling interval 20.833 μ s), the minimum required speed of the DSP in millions of operations per second (MOPS) is $50/20.833 = 2.4$ MOPS.

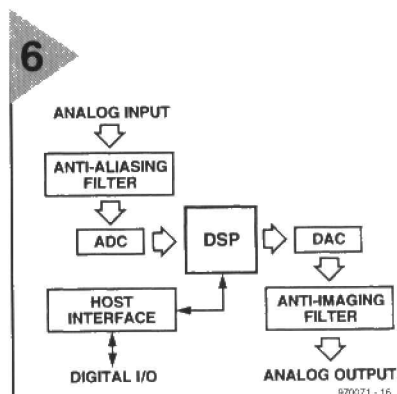


Figure 6. Block diagram of a DSP system. Its simplicity is due largely to the functionality of the programmable DSP.


Note that the two common ratings for DSPs, based on millions of operations per second (MOPS) and millions of instructions per second (MIPS), are not the same, since an operation may consist of several instructions.

SAMPLING

REAL-WORLD SIGNALS

There are two basic ways to acquire data: one sample at a time or one frame at a time (continuous processing vs batch processing). Sample-based systems, like a digital filter, acquire data one sample at a time. As shown in Figure 5a, at each tick of the clock a sample comes into the system and a processed sample is output.

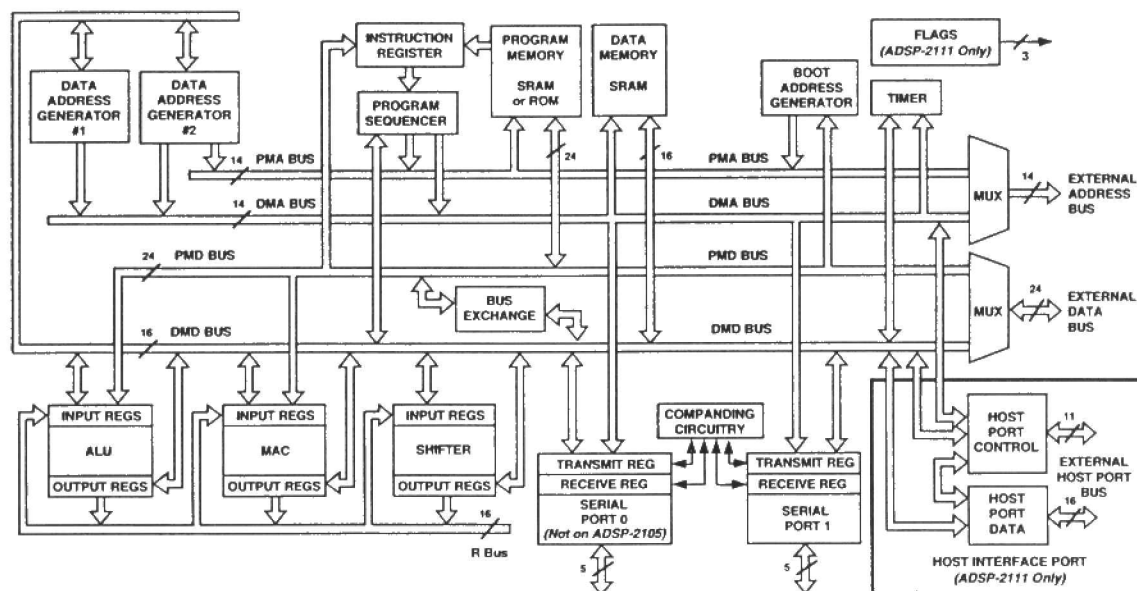Frame-based systems, like a spectrum analyser, which determines the frequency components of a time-varying waveform, acquire a frame, or



970071-17

Figure 7. Internal block diagram of a modern DSP in the ADSP-21xx series from Analog Devices.

block, of samples. Processing occurs on the entire frame of data and results in a frame of transformed data as shown in Figure 5b.

For an audio sampling rate of 48 kHz, a processor working on a frame of 1024 samples has a frame acquisition interval of 21.33 ms (that is, $1024 \times 20.833 \mu\text{s} = 21.33 \text{ ms}$). Here, the DSP has 21.33 ms to complete all the required processing tasks for that frame of data. If the system handles signals in real time, it must not lose any data; so, while the DSP is processing the first frame, it must also be acquiring the second frame. Acquiring the data is one area where special architectural features of DSPs come into play: seamless data acquisition is facilitated by a processor's flexible data-addressing capabilities in conjunction with its direct memory-accessing (DMA) channels.

RESPONDING TO REAL-WORLD SIGNALS

It cannot be assumed that all the time between samples is available for the execution of processing instructions. In reality, time must be allowed for the processor to respond to external devices, controlling the flow of data in and out. Typically, an external device (such as an ADC) signals the processor by way of an interrupt. The DSP's response time to that interrupt, or interrupt latency, directly influences how much time remains for actual signal processing.

Interrupt latency (response delay) depends on several factors of which the most dominant is the DSP architecture's instruction pipelining. An instruction pipeline consists of the number of instruction cycles that occur between the time an interrupt is

received and the time that program execution resumes. For example, if a processor has a 20 ns cycle time and requires 10 cycles to respond to an interrupt, 200 ns elapse before it executes any signal-processing instructions. In continuous processing, this 200 ns overhead will not hurt if the DSP finishes the processing of each sample before the next arrives.

In batch processing, however, an interrupted system wastes processor instruction cycles. For example, a system with a 200 ns interrupt response time running a frame-based algorithm, such as the FFT (Fast Fourier Transform), with a frame size of 1024 samples, would require 204.8 μs of overhead. That amounts to more than 10,000 instruction cycles wasted to latency. This waste is easy to avoid in DSPs having architectural features such as DMA and dual memory access: these let the DSP receive and store data without interrupting the processor.

DEVELOPING A DSP SYSTEM

Now the role of the processor, the ADC, the anti-aliasing filter, and the timing relationships between these components have been discussed, it is time to look at a complete DSP system. Figure 6 shows the building blocks of a typical DSP system that could be used for data acquisition and control.

Note how few components make up the system, because so much of the system's functionality comes from the programmable DSP.

Converters, both analogue-to-digital (DAC) and digital-to-analogue (DAC), funnel data in and out of the DSP. The ADC timing is controlled by a precise sampling clock.

To simplify system design, many converter devices available today combine some or all of the following: an ADC, a DAC, a sampling clock, and filters for anti-aliasing and anti-imaging.

There are some other points that need to be borne in mind to arrive at a final design. For instance, the bandwidth of the anti-aliasing filter depends on the input signals used. Whether the interfacing between the ADC and DSP is serial or parallel depends on the desired speed. Parallel takes more space (both as regards board tracks and terminal pins), but is faster. Serial is slower, but much more compact and normally less expensive.


The incoming data is handled by the DSP's algorithm. When the processor completes the requisite calculations, it sends the result to the DAC. Because the signal processing is programmable, considerable flexibility is available in handling the data and improving system performance with incremental programming adjustments.

The DAC converts the DSP's digital output into the desired analogue output at the next sample clock. The converter's output is smoothed by a low-pass anti-imaging filter (also called a reconstruction filter) to produce the reconstructed analogue signal.

[970071]


Reference

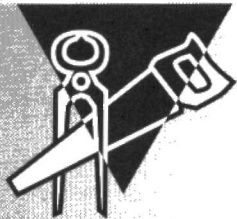Analog Interface and DSP Sourcebook by Alan Clements, McGraw-Hill (1993), ISBN 0 07 707694 x (reviewed in the May 1993 issue of this magazine).



make your own front panels

for a nice finish, the inexpensive way

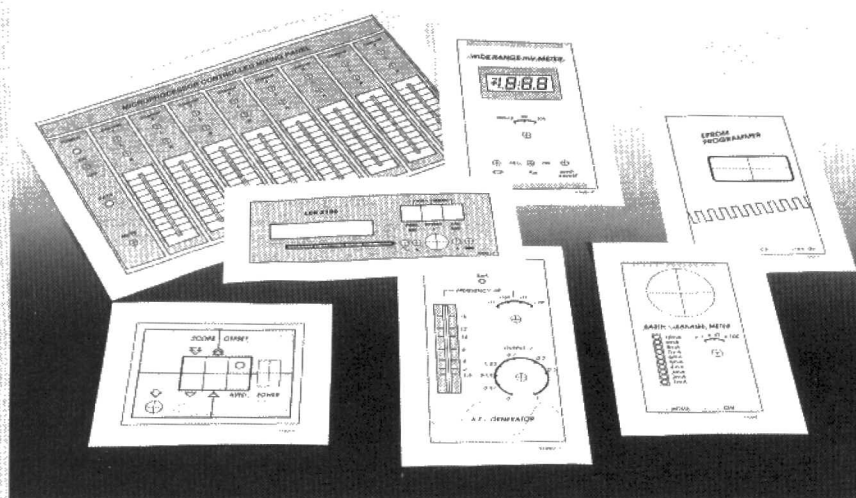

imum sales volume can be achieved. Hence, this product is now rarely seen in our product lists. The good news is that many of you have a computer and (access to) a colour printer of the inkjet type (e.g., an Epson, Canon or Hewlett-Packard printer). These two 'tools' form a perfect basis for making front panels with a professional look, and not expensive, either! Let's examine the production steps one by one.

Figure 1. A modern inkjet printer enables you to produce a good looking front panel foil without too many problems.

When building your own electronic equipment, finishing the case with a smart looking front panel is often a problem. Because a ready-made front panel foil is rarely available through our Readers Services, most of you will be forced to produce one by yourselves. Fortunately, making your own front panels is relatively easy if you have a computer and a colour printer, or access to such a combination. In the Elektor Electronics laboratory, this technique is applied for finishing off prototypes which appear on photographs in the magazine.

It is only by means of a properly finished case and a suitable front panel that a home-brew project can be given the 'professional look'. These days, a variety of metal and ABS cases is available from electronics shops and by mail order, and finding a type which allows a published circuit to be housed will not be too difficult, especially if the outside dimensions and material are

known from the relevant construction article. Designing and making the front panel, however, is much more of a problem, mainly because every project has its own requirements as regards the number of controls, type and position. And then we're not even mentioning scales to be printed around knobs, and other special treats.

Unfortunately, designing, producing, storing and selling a ready-made front panel foil through our Readers Services is only viable if a certain min-


Step 1. Use a drawing or photo retouching program (say, Corel Draw or Paintshop Pro) to design the front panel layout at true size. Where possible, use saturated colours, and no variable shades. Although modern inkjet printers offer quite acceptable results for screens in the backgrounds, actually printing these patterns remains difficult.

If you intend to use a certain enclosure for different applications, then a basic ('master') layout can be designed and saved as a kind of template for use later.

Step 2. Print the front panel design, using self-adhesive white foil sheets (suitable for the printer, of course), or glossy paper. Ordinary foil is not suitable in most cases because it does not absorb the ink properly. Allow the foil to dry completely after printing. Suitable foil or paper is available in relatively small quantities from stationers or computer shops (in some cases, by the sheet, else in boxes of 25 or 50 sheets).

Step 3. Glue the printed foil on a piece of solid paper (120-150 g). This is done to make the front panel more solid, and to be able to hide small surface irregularities. Glossy paper may be secured with two-component glue. If a

By our laboratory staff

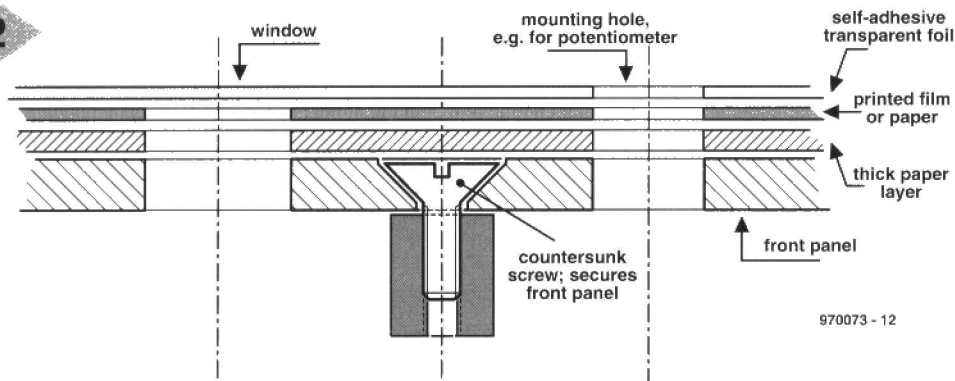

970073 - 12

Figure 2. Basic construction of the front panel. On top, the self-adhesive transparent foil, then comes the front panel as printed on film or paper, and, finally, a layer of thick paper for extra strength, and to allow irregularities in the surface to be eliminated. The whole is glued on to the actual (metal or ABS) front panel supplied with the enclosure.

transparent window is required, this is the right moment to cut it out of the foil or paper layer using a sharp hobby knife. Next, cut the front panel exactly to size, so that it fits accurately on the (metal or plastic) front panel of the enclosure. This panel has to be completely drilled, filed and sandpapered before the front panel foil can be glued on. In this respect, it is important to carefully remove any burrs from the front panel. This is best done with a fine-grade sandpaper.

Step 4. Cover the front panel with a piece of transparent self-adhesive foil. Use a small paint roller (a clean one!) or a large pen to remove all bubbles

from the surface. Cut off the foil around the panel, using a wide margin (at least 1 cm), and make all required holes. Next, wrap the excess foil around to the back of the front panel. If you can find a suitable glue, it is also possible to stick the panel, complete with the foil on it, directly on to the front panel. That does, however, require some experimenting!

The main function of the thick paper layer is to enable small irregularities in the front panel surface to be ironed out. If the surface is absolutely level, then the extra paper layer is not required.

Although the quality of the ink

used in modern inkjet printers is constantly improving, discolouring does occur as a result of exposure to UV light. It is therefore useful to apply a transparent self-adhesive foil with a built-in UV filter. Ask your supplier about this specification. Obviously, when storing the equipment it is best to avoid a position where it is exposed to direct sunlight.

If you use a laser printer instead of an inkjet printer, you will have grey tones only. On the positive side, you don't have to worry about UV light affecting the durability of the front panel foil.

(970073-1)

Circuit simulation can be seriously good fun

Those
Engineers Ltd



When you have the engineering edge, enjoy your work and catch subtle circuit behaviour before it's too late, you can afford to be light hearted. Add to this technical support from practising engineers who take a genuine interest in your work and you are really laughing.

With a free evaluation kit, you can test SpiceAge on your own circuits. The kit comes with an introductory booklet to show you how.


To hear more about this and other nice touches in SpiceAge, please contact the friendly people at Those Engineers Ltd, 31 Birkbeck Road, LONDON NW7 4BP.

Tel 0181 906 0155

FAX 0181 906 0969


Email those_engineers@compuserve.com

Web <http://www.spiceage.com>

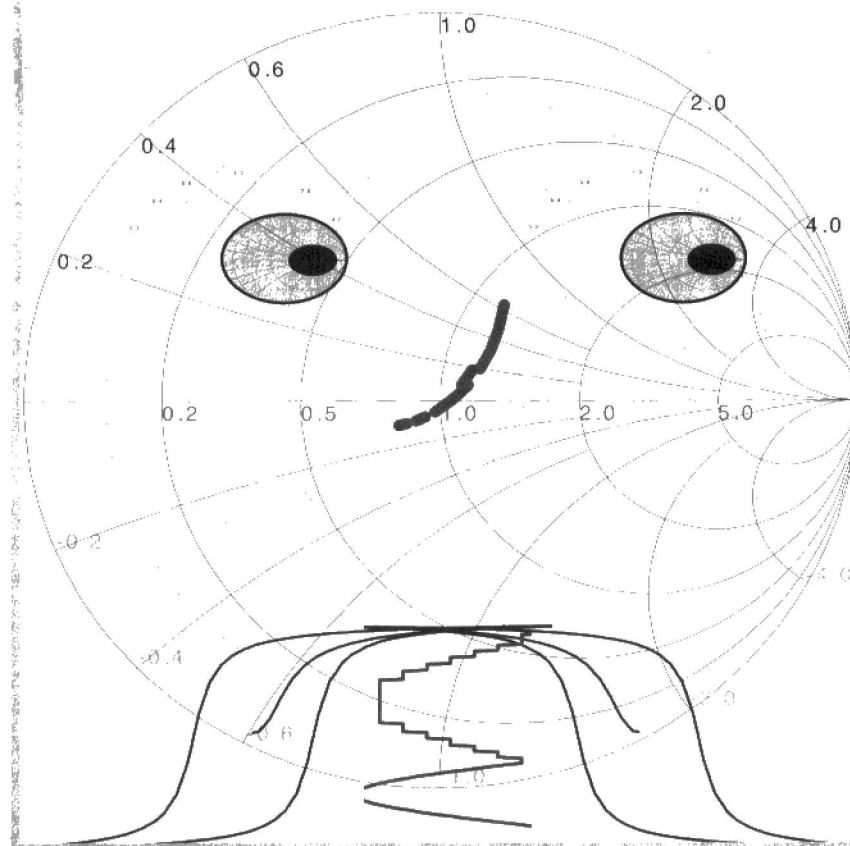



the wall box

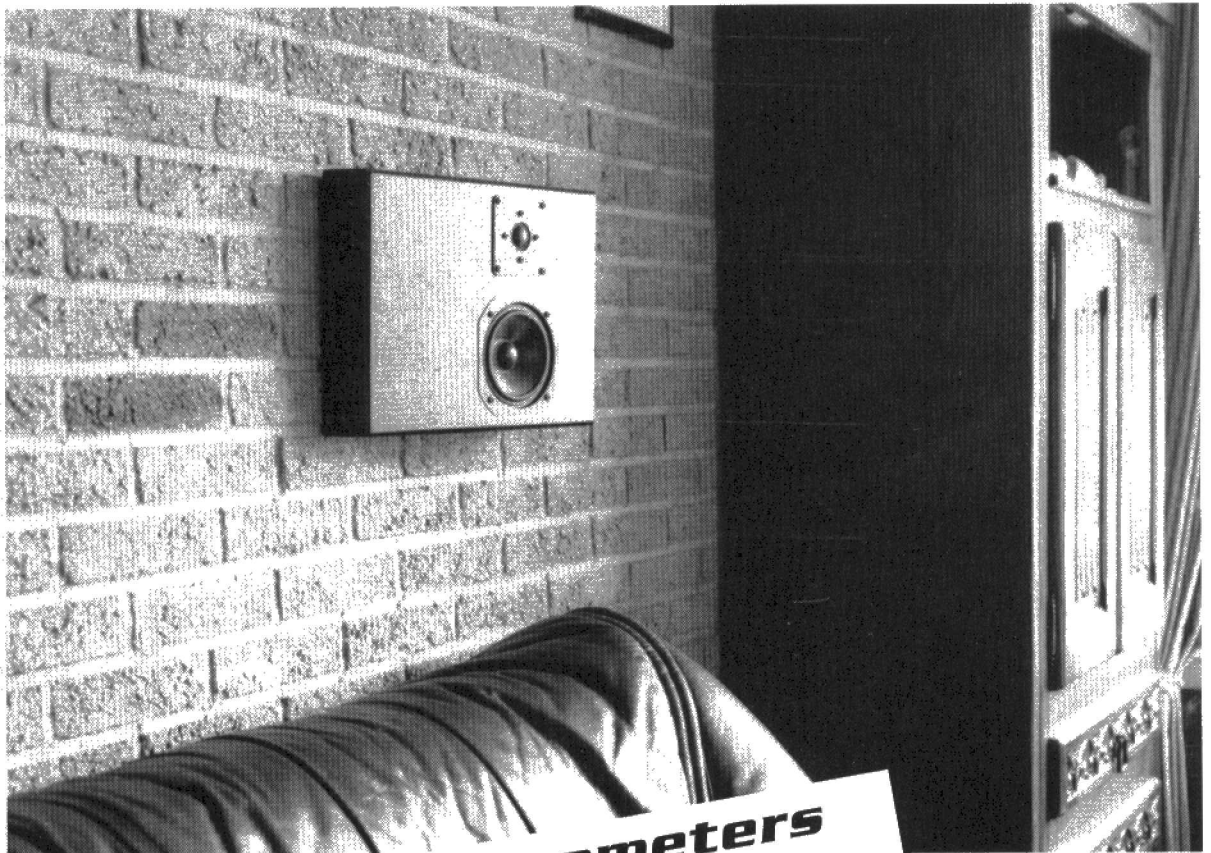

Brief parameters

Design
Woofer
Tweeter
Wideband driver
Frequency range
Crossover frequency
Music power
Nominal impedance
Volume
Dimensions
Special aspects

Two-way or three-way, vented
WS13BF (Visaton)
DTW95NG (Visaton)
FRWS5 (Visaton)
70 Hz – 20 kHz (–3 dB)
About 2 kHz
60 W
4 Ω
5 litres
300×418×138 mm (H×W×D)
Wideband unit provides
sideways radiation

In these days of miniaturization, few people seem to feel a need for large loudspeakers in their living room. But, although they want small boxes, they still want good quality. The wall box presented in this article meets those requirements. It is a two-way system housed in a small, shallow enclosure that is inconspicuous in the living room.

Design by H. Baggen

There are many signs in the retail figures of the audio/hi-fi industry that the real hi-fi period of separates has peaked. These days, most customers specify a small or medium-sized system (mini towers are particularly popular right now) from which they expect exactly the same performance as from yesteryear's large installations. Loudspeakers are not excluded. Small, inconspicuous ones are wanted, but these must sound good and, more particularly, produce a good bass. Unfortunately, the unyielding laws of nature do not allow good bass reproduction from a small enclosure.

Nevertheless, if good drive units are used in a well-designed medium-sized box, good sound, small(ish) dimensions and affordability can go

hand in hand, and this is what the present design is all about.

In the design, account was also taken of the fact that some people may use the present loudspeaker in a surround-sound system. Additional loudspeakers at right angles to the line connecting listener and main loudspeakers broaden the stereo reproduction.

The enclosure is intended primarily to be hung from a wall: it is tuned for that purpose.

DESIGN CONSIDERATIONS

As mentioned earlier, the design specification includes reasonable cost, good sound reproduction that fits in well with a modern (stereo) TV receiver or hi-fi system, and is not too conspicuous in the living room. The result is a medium-sized, shallow box intended for wall mounting.

The requirement of providing good bass response from a medium-sized,

Figure 1. Circuit diagram of the crossover network for the wall box. The filter for the woofer and tweeter is a second-order one, while that for the wide-band unit is simply a capacitor.

not too expensive loudspeaker makes the choice of drive units highly critical. In the prototype, a 130 mm diameter bass/mid-range unit, a WS13BF, a 25 mm diameter tweeter, a DTW95NG, and a 50 mm diameter wideband unit, a FRWS5 are used. All three units come from the Visaton stable.

The Thiele/Small parameters of the WS13BF make it eminently suitable for use in a medium-sized box. It has a coated paper cone with a foam rubber surround and a 25 mm diameter voice coil.

The tweeter has a square mounting flange that goes well with the mid-range unit. It has an impregnated woven dome and heavily damped surround. The air gap is filled with magnetic ferrofluid, which provides good cooling and additional damping. Its frequency response is almost flat over the range 1.5–20 kHz.

The FRWS5 enhances the stereo effect. Strictly speaking, it may be omitted where this enhancement is not needed. However, in the prototype, it helped to produce a wide-angle stereo sound, which is particularly noticeable at the sides of the listening angle.

CROSSOVER NETWORK

The filter has also been kept as simple as possible without too many compro-

mises. Its circuit diagram is shown in **Figure 1**. The network was designed with the aid of a computer simulation program that, based on the measured frequency and phase response of the drive units in the enclosure, calculates the overall response of the system including the crossover network. It also takes into account the positioning of the drive units and their radiation pattern.

The design of the network is a slightly modified second-order Butterworth filter with a few impedance corrections. This results in a second-order

low-pass filter, L_1 - C_1 , for the woofer. Capacitor C_1 has another function as well: in conjunction with R_1 it provides the requisite impedance correction for the woofer, which is necessary for good filter performance.

The high-pass filter for the tweeter is formed by L_2 - C_2 , which, in conjunction with the response of the tweeter itself, results in a third-order rolloff. Resistors R_2 and R_3 lower the output of the tweeter by about 3 dB to match its output level to that of the woofer.

The cross-over frequency between woofer and tweeter is at about 2 kHz.

The 'filter' for the wideband unit is simply a 22 μ F bipolar electrolytic capacitor in parallel with the filters for the other two units. This cuts off the response of the wideband unit below about 800 Hz, which results in a satisfying additional spatial effect.

ENCLOSURE

The shallow box has a net volume of five litres and yet the 3 dB cut-off frequency is as low as about 68 Hz.

It will be seen from the introductory photograph and the construction plan in **Figure 3** that the woofer and tweeter are pointed slightly towards

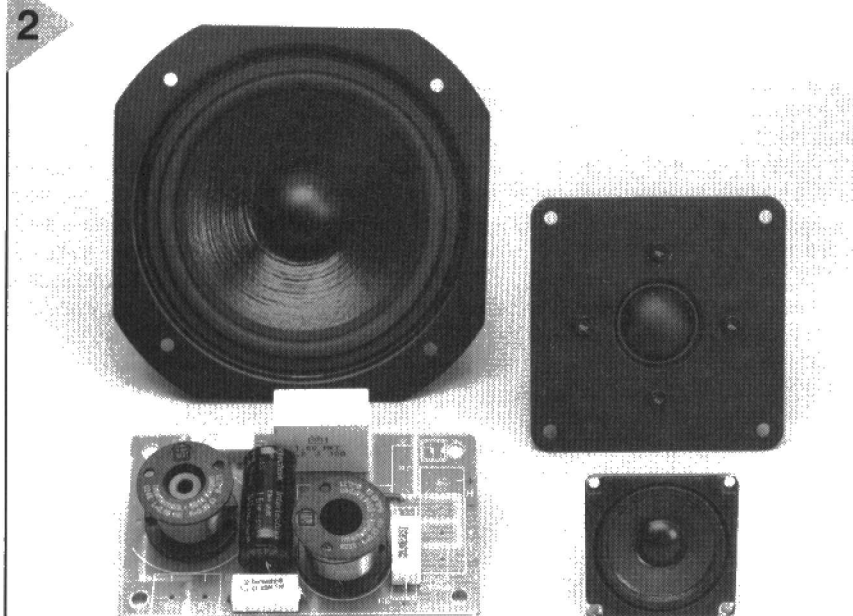
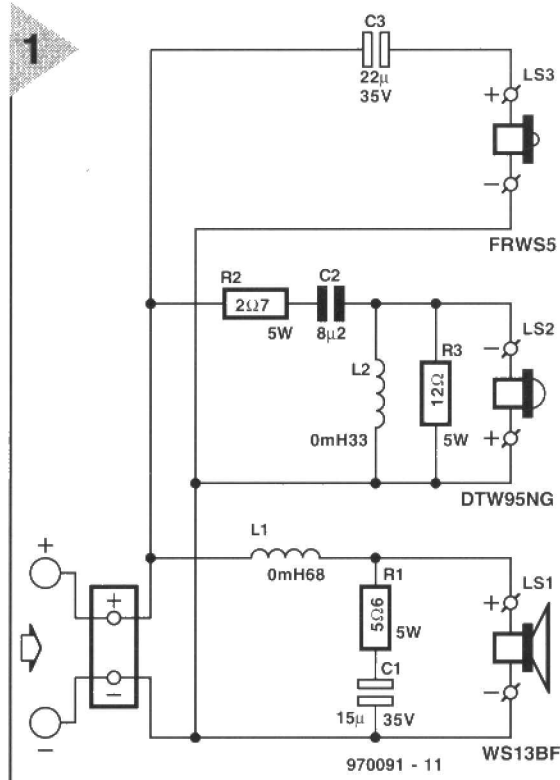


Figure 2. The drive units and crossover filter for the wall box (the electrolytic capacitor for the wideband unit is not shown).

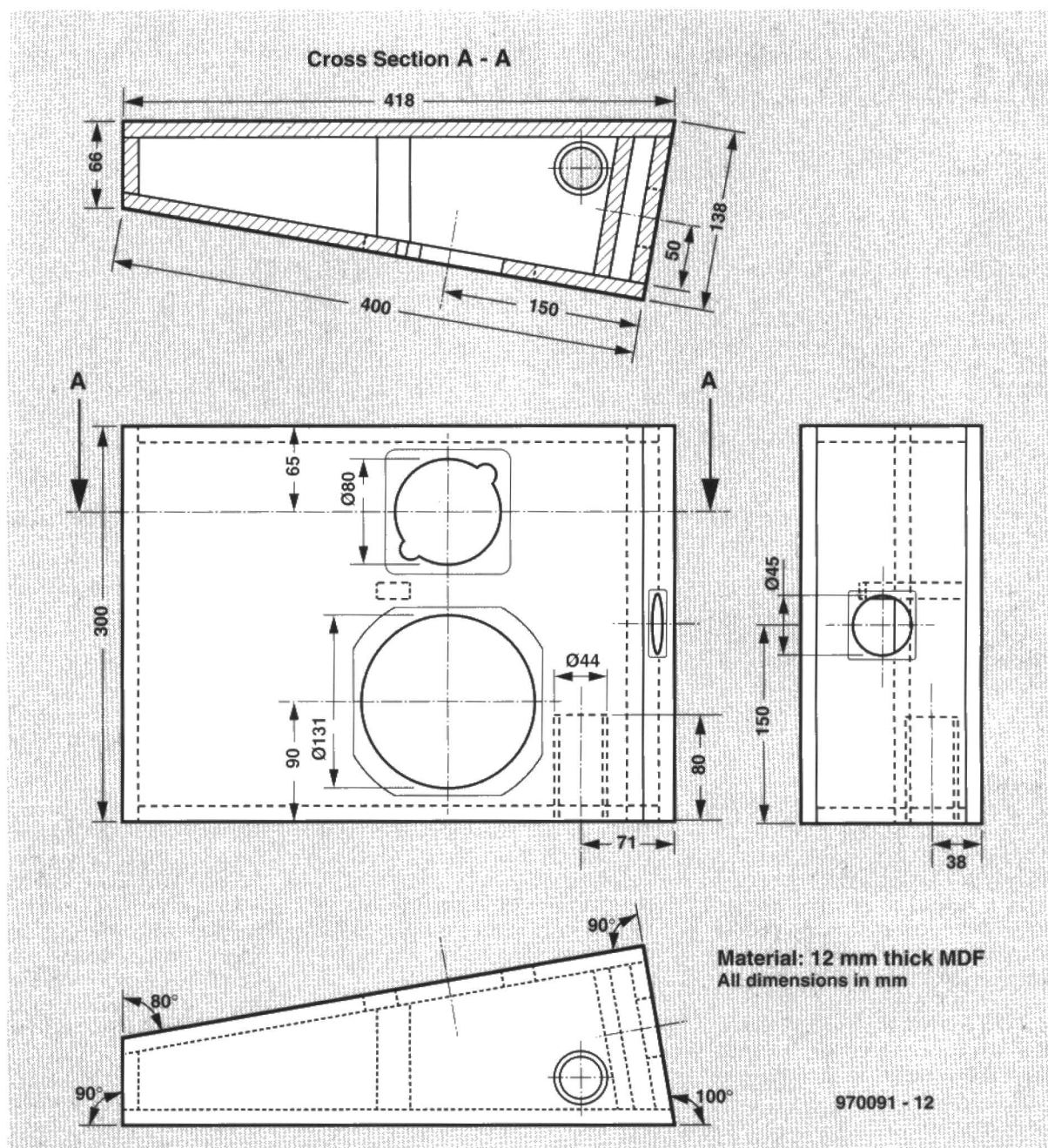


Figure 3. Construction plan for the box. Note that some of the panels are cut at 80° instead of the usual 90°.

the listener, whereas the wideband unit points slightly further forward. This makes it necessary for some of the constituent panels to be sawn at an angle of 80° instead of 90°. These angles make the enclosure look rather different from the usual rectangular box. Of course, if this angular construction is found too tedious, the box may be made rectangular with dimensions 300 × 160 × 160 mm.

Two holes are required in the front panel for the woofer and tweeter, and a single hole at the side for the wideband unit. The inside diameter of this latter hole should be enlarged with a suitable wood rasp or wood file to give

the unit 'more air' at its rear.

A horizontal brace must be glued at the centre of the box between front and rear panel.

A partition at the side gives the wideband unit its own tiny chamber.

The bottom panel needs a suitable hole for the 44 mm diameter bass reflex port, which is 80 mm long. This port results in the the enclosure being tuned to about 50 Hz.

The crossover filter is best built on a piece of prototyping or similar board. Such boards can be bought from most specialist audio retailers. It is advisable to buy the components for the filters also from such a retailer, since electronics retailers normally do not stock them.

Fit the filter board in the box and feed the requisite connecting wires to the outside (those of the wideband unit through small holes in the partition). It is, of course, also possible to fit

special (gold-plated) terminals to be underside of the box: this will look very pleasant.

Fit two small suspension plates at the top back of the box to enable it to be hung from the wall.

Fill the box with suitable wadding, wire up the drive units, and screw them into place. Mind the correct polarity, which is shown in the diagram (the tweeter should be in anti-phase with the woofer).

The box may be finished to personal taste and in accord with the decorations in the living room.

POSITIONING AND USAGE

The finished loudspeakers should be hung from a wall at ear-height (that is, at a height from the floor of about 1.6 metres). Their position should be

Parts list (per box)

Resistors:

$R_1 = 5.6 \Omega$, 5 W

$R_2 = 2.7 \Omega$, 5 W

$R_3 = 12 \Omega$, 5 W

Capacitors:

$C_1 = 15 \mu\text{F}$, 35 V, bipolar electrolytic

$C_2 = 8.2 \mu\text{F}$, metallized polyester (MKT)

$C_3 = 22 \mu\text{F}$, 35 V, bipolar electrolytic

Inductors:

$L_1 = 680 \mu\text{H}$ air-cored or suitably cored, $R_l \leq 0.5 \Omega$

$L_2 = 330 \mu\text{H}$, air-cored, $R_l \leq 0.5 \Omega$

Drive units:

$LS_1 = \text{WS13BF}$, 8 Ω (Visaton)

$LS_2 = \text{DTW95NG}$, 8 Ω (Visaton)

$LS_3 = \text{FRWS5}$, 8 Ω (Visaton)

Miscellaneous:

PVC pipe, 44 mm outer diameter, 80 mm long

Wadding, about 40×25 cm

2 off gold-plated loudspeaker terminals

Medium-density fibreboard (MDF) panels 12 mm thick:

1 off 418×300 mm

1 off 402×300 mm

1 off 420×300 mm

1 off 114×300 mm

1 off 107×300 mm

2 off 392×42×378×112 mm

4


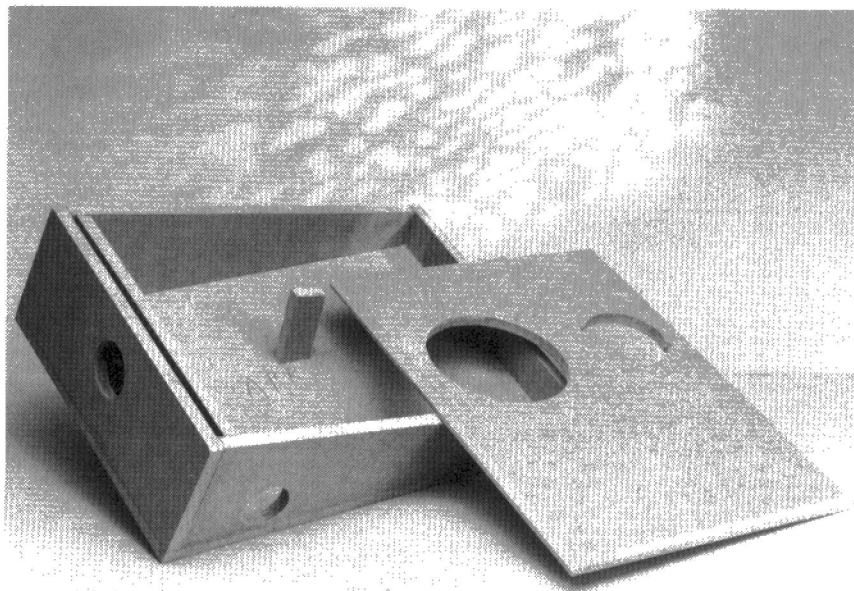
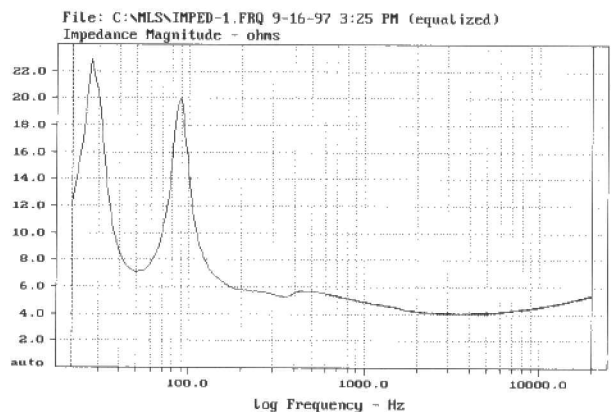


Figure 4. Inside view of the box before the top panel is put in place.

Figure 5. Frequency response curve and impedance curve of the wall box, incl. the wideband unit.

5

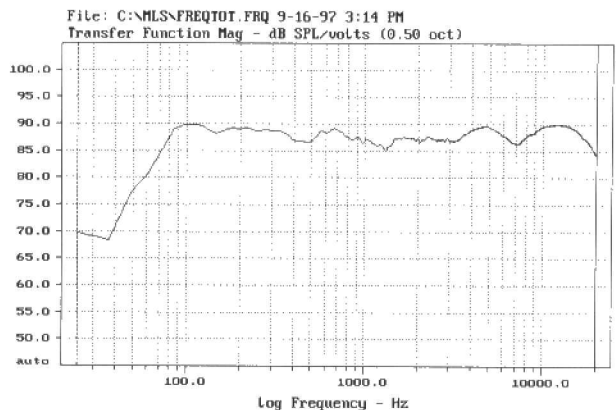

well away from corners so as not to lose the effect of the wideband unit. They should also not be placed too close (less than one metre) to a TV receiver, because the drivers are not shielded.

The frequency response and impedance characteristics are shown in **Figure 5**. Note that the minimum impedance is about 4 Ω at 10 kHz, which is a value that presents no risks to modern drive units.




A listening test on the prototype loudspeakers showed that, in spite of their modest dimensions, the sound quality and the bass reproduction are very good. Where top-class performance is required, they are best combined with a good-quality stereo system. The units are also very suitable for use as the front loudspeakers in a surround-sound installation.

[970091]

electronics on-line

DSPs on the Internet

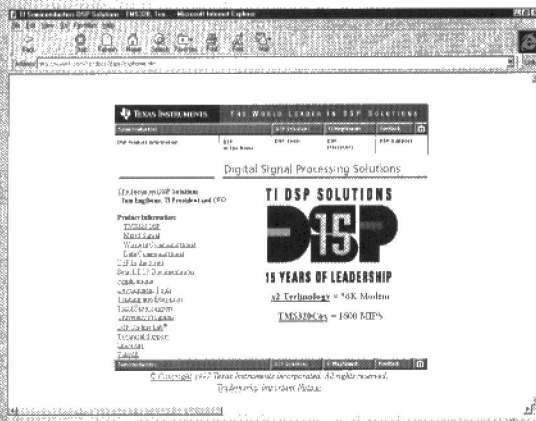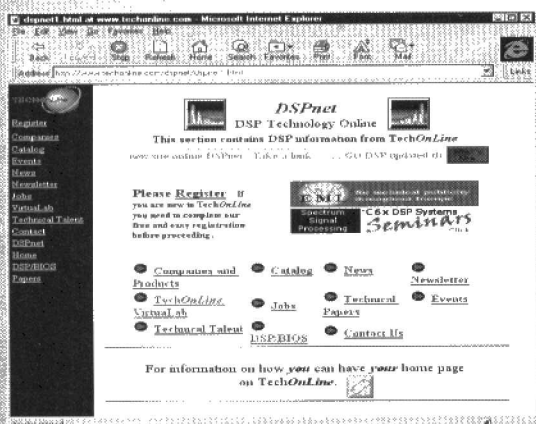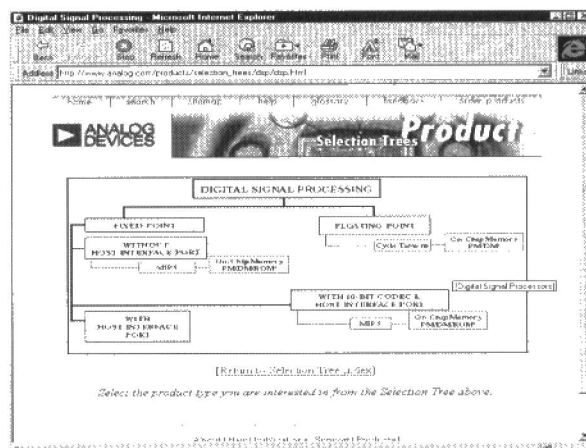If you can't wait to start working with digital signal processors (DSPs), a lot of relevant information may be found on the Internet. Datasheets and applications are published by this global network. On this page we hope to provide a number of starting points for a successful search.



DSPnet is a general forum which supplies information on practically any DSP. This site may be found at <http://www.dspnet.com> or <http://www.technoline.com/dspnet/dspnet1.html>.

Both URLs point to the same location. Once at this site, the visitor is confronted with various forums, seminar schedules, datasheet files, tips and application notes. A complete overview of all information at this site may be found at the address <http://www.technoline.com/dspnet/comp.html>.

Interestingly, this site holds the specifications of all processors found in the standard supply program of all familiar DSP manufacturers. Using general qualifiers (like fixed or floating-point processor) or a specific requirement (say, regarding computing power), the processor having the desired features is quickly located.

STRAIGHT TO THE MANUFACTURER

If you have already decided which DSP to use, you may also go straight to the

desired site. In practice, three major manufacturers control the market for DSPs. Digital signal processors from Motorola are given an extensively presentation at the web address <http://www.motorola.com> or <http://www.mot.com>.

The menus at these sites quickly guide you to the DSP main page at <http://www.mot.com/sps/dsp/products>. By virtue of the pointers you see on these pages, finding the necessary information on the DSP product line is easy.

Another large supplier of DSPs is Texas Instruments (<http://www.ti.com>) whose home page has a prominent location for everything related to DSPs. Choose <http://www.ti.com/sc/docs/dsp/dsphome.htm>

for an excellent and extensive overview of TI's DSPs.

Last but certainly not least comes Analog Devices (<http://www.analog.com>) whose homepage seems to lack a direct reference to DSPs. A good idea is to use the search option and enter 'DSP' as the argument. The result is a screen full of references to technical information like datasheets and lots of other data covering the DSPs made by Analog Devices. Alternatively, choose a direct address. Simply type http://www.analog.com/products/selection_trees/dsp/dsp.html, and the main page about Digital Signal processing will be opened.

(975094-1)

Design kits for AC motor drives

International Rectifier has introduced a family of power conversion subsystem design kits for 230 V or 460 V ac motors from 370 W to 11 kW (0.5 to 15 hp)


The PowlRTrain™ design kits combine all power conversion and power control functionality required for building state-of-the-art motor drives and controls, with or without braking, in modules or assemblies that are up to 75 percent more compact than other commercially available solutions.

The kits dramatically reduce the required design effort to translate power semiconductor into usable drive designs,

eliminating component testing and device qualification, and taking into account thermal management and noise-free layout issues. They include both an integrated power stage and a fully optimised control stage, plus a bill of materials, complete schematics, Gerber photoplots for board layouts, and a comprehensive system specification.

(977199-1)

International Rectifier, Hurst

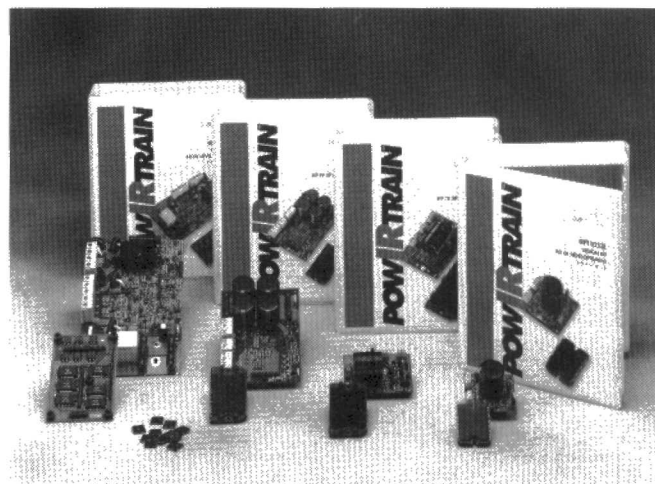


Green, Oxted, Surrey RH8 9BB. Tel. (01883) 732020, fax

(01883) 733410. Internet: www.irf.com.

Audio DAC with on-board PLL

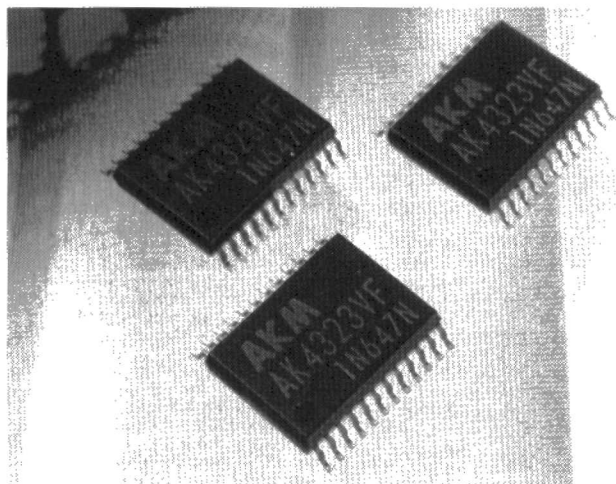New from DIP International is the AK4323 stereo D/A converter with an integral phase locked loop (PLL), designed for use in digital broadcast systems which use the 27MHz MPEG system clock.



The on-chip PLL reduces board area and saves cost as until now, separate external circuitry was required for the PLL. This part of the AK4323 provides selection of sampling clock frequencies locked to the recovered 27MHz MPEG clock, supports 2/3 division of master clock by some MPEG audio devices, and allows master clock frequencies including half rates to be chosen.

The DAC section of this CMOS device has 128x oversampling, a 20-bit 8x digital filter, combining high performance with low cost, making it ideal for high quality, cost sensitive applications. The built-in 2nd order SCF and 2nd order CTF minimises external filtering. There is digital de-emphasis for 32, 44.1 and

48 kHz sampling, which makes the AK4323 compliant with most audio applications. The dynamic range of 100 dB supports true 16-bit performance. Supplied in a small 24-pin VSOP package, power supply requirements are 4.5 to 5.5 V.

Applications include digital set top boxes, television and radio broadcast systems and post production equipment that runs from a 27MHz system clock.

(977200-1)

DIP International Ltd., Sheraton House, Castle Park, Cambridge CB3 0AX. Tel. (01223) 462244, fax (01223) 467316. Email: 100343.304@compuserve.com




PICs with 8-channel ADC and 8k×14 program memory

Microchip's new PIC16C76 and 16C77 microcontrollers offer 8k×14 words of program memory, 376 bytes of data RAM and a very low power on-chip A/D converter.

The 5 MIPS EPROM-based microcontrollers contain an on-chip, 5-channel (PIC16C76) and 8-channel (PIC16C77), 8-bit A/D converter with sample and hold, accuracy of ±1LSB and an acquisition time of just 16ms. Available in small footprint 28-pin and 40-pin pack-

ages, these one-time programmable devices feature 200-ns microcycle times, 35 single-cycle instructions, and are ideal for embedded control applications such as air bag controllers, motor control, set top boxes and network switches.

(977202-1)

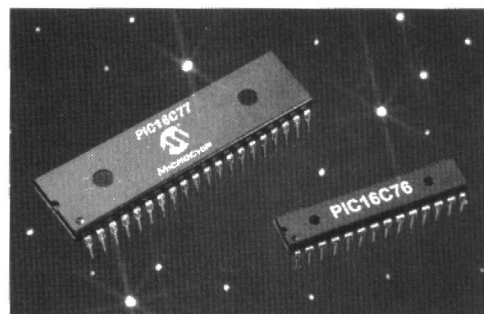


Arizona Microchip Technology Ltd., Unit 6 The Courtyard, Meadowbank, Furlong Road, Bourne End, Bucks SL8 5AJ.

Tel. (01628) 851077, fax 850259.

READERS SERVICES

ELEKTOR ELECTRONICS

NOVEMBER 1997

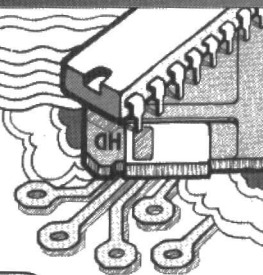

GENERAL

Printed-circuit boards (PCBs), self-adhesive front panel foils, ROMs, EPROMs, PALs, GALs, microcontrollers, and diskettes for projects which have appeared in *Elektor Electronics* may be ordered using the Order Form printed opposite. The form may also be used to order books (private customers only).

* If no product description is given, then the item is a ready-made printed circuit board (PCB).

* Items not listed here may not be available any more.

* The artwork for making a PCB which is not available ready-made through the Readers Services may be found in the relevant article.

* EPROMs, GALs, PALs, (E)PLDs, MACHs, PICs and other microcontrollers are supplied ready-programmed.

Prices and item descriptions subject to change. The publishers reserve the right to change prices without prior notification. Prices and item descriptions shown here supersede those in previous issues. E. & O.E.

PAST ISSUES

Past issues, if available, should be ordered from **Worldwide Subscription Service Ltd, Unit 4, Gibbs Reed Farm, Pashley Road, TICEHURST TN5 7HE, England, telephone (+44) 1580 200657, fax (+44) 1580 200616, email www.subscription@virgin.net**.

Prices of past issues (except July/August and December), including postage for single copies, are £3.20 (UK and Eire); £3.50 (surface mail outside UK); £3.75 (air mail Europe); £4.50 (airmail outside Europe). Prices of past July/August and December issues, including postage for single copies, are £4.25 (UK); £4.50 (surface mail outside UK); £4.75 (airmail Europe); and £5.50 (airmail outside Europe).

PAST ARTICLES

For information on past articles, please contact our Editorial and Administrative Office in Dorchester, telephone (01305) 250995, fax 250996, email elektor_uk@compuserve.com.

Article title or item	Order code	Price £	Price US\$
- PCB and diskette	970009-C	15.25	30.50
- Diskette only	976001-1	8.75	17.50
Talking Doorbell	970015-1	10.50	21.00

JANUARY 1997

Dongle Switch	960089-1	7.00	14.00
Magnetic-Field Meter	960100-1	8.50	17.00
Speed Regulator for Model Trains	960113-1	8.50	17.00
Monitor to Guard Fridge Temperature	970001-1	8.00	16.00

DECEMBER 1996

20-bit A/D converter	960110-1	22.75	45.50
Remote Control by Visible Light	960068-1	11.00	22.00
Primary-Battery Refresher	960106-1	11.25	22.50
RS232 data acquisition card:			
- PCB, PIC and disk	960098-C	35.50	71.00
- disk only	966019-1	7.25	14.50
- PIC 16C71 only	966508-1	24.00	48.00
Hands-On Electronics:			
- MicroCap V demo disks	966021-1	4.00	8.00
Electrically Isolated I2C bus	964062-1	6.75	13.50
Centronics I/O Port	964116-1	18.50	37.00
Mains Voltage Cleaner	964070-1	10.25	20.50

NOVEMBER 1996

ST62 Programmer:			
- PCB and disk	960105-C	16.75	33.50
- PCB only	960105-1	12.75	25.50
- disk only	966018-1	6.00	12.00
Hands-On Electronics:			
- MicroCap V demo disks	966021-1	4.00	8.00
Headphones Amplifier	960109-1	6.25	12.50
50W A.F. Amplifier	960079-1	8.00	16.00
Infra-red RS232 Link:			
- PCB and disk	960107-C	15.25	30.50
- disk only (Temic files)	966020-1	8.00	16.00
Steam-Engine-Noise-Generator	960087-1	7.75	15.50

OCTOBER 1996

Video Test Chart Generator:			
- PCB, EPROM, EPROM and disk	960076-C	79.50	159.00
- EPROM 27C040	966507-2	24.50	49.00
- Disk only	966011-1	7.00	14.00
Mini Flash Programmer:			
- PCB and software (disk)	960078-C	21.25	42.50
- Software only (disk)	966015-1	12.25	24.50
Mini Metal Detector	960075-1	5.50	11.00
Darkroom Timer	960086-1	11.75	23.50
Sampling Rate Converter:			
- PCB and ST62T10	960093-C	28.75	57.50
- ST62T10 (IC2)	966511-1	19.50	39.00
Thrifty Crystal Oven	960071-1	12.75	25.50
Electric-Bulb Tester	960091-1	6.00	12.00
Multi-Purpose Pascal I/O Unit (disk only)	966013-1	7.00	14.00

SEPTEMBER 1996

Digital max/min thermometer:			
- PCB and ST62T10	960010-C	27.75	55.50
- ST62T10 (IC1)	966515-1	19.50	39.00
Standby Unit for TV Economy	960063-1	12.00	24.00
Digital Compass	960085-1	7.50	15.00
RS232 Interface for A/D Converter ICL7106:			
- software on disk	966016-1	6.00	12.00

JULY/AUGUST 1996

Continuity Tester	UPBS-1	1.95	3.90
Symmetrical Power Supply	UPBS-1	1.95	3.90
Sound-to-Light Unit	950123-1	9.50	19.00
50-MHz dBm Meter	964039-1	16.50	33.00
Precision Battery Capacity Meter	964040-1	8.00	16.00
Video Fader	964076-1	12.25	24.50
Inexpensive A/D Converter:			
- PCB	964092-1	Not Available	
- software on disk	966009-1	7.00	14.00
Single-Chip AF Power Amp	964104-1	6.25	12.50
JUNE 1996			
Flash EPROM Programmer/Emulator			
- PCB + disk	960077-C	33.00	66.00
- disk only	966017-1	16.00	32.00
Keyboard Swap for PCs	950126-1	7.00	14.00
Stop that Barking!	960035-1	5.50	11.00
23cm ATX preamplifier	960072-1	7.50	15.00
Pulsimeter	960005-1	10.25	20.50
Burglar Deterrent Lighting	960022-1	7.25	14.50

MAY 1996

Intelligent Chess Clock:			
- PCB + 87C51 (946645-1)	950097-C	41.75	83.50
- 87C51	946645-1	30.75	61.50
Digital VU meter (2):			
- PCB + EPROM (946646-1)	950098-C	36.00	72.00
- EPROM 27C512	946646-1	17.75	35.50
Surround Sound Subwoofer (3):			
- PCB	960049-1	16.75	33.50
Mains Voltage Monitor:			
- PCB	960055-1	7.25	14.50
64-Channel Logic Analyser:			
- main PCB, disk & IC4, IC5	960033-C	69.75	139.50
- IC4 ISL1016	966506-1	27.50	55.00
- IC5 ISL1016	966506-2	27.50	55.00
- disk (MSDOS)	966010-1	7.00	14.00
- extension PCBs (3-in-1)	960033-2	17.00	34.00
- IC20/30/40 ISL1016	966506-2	27.50	55.00

APRIL 1996

Article title or item	Order code	Price £	Price US\$
U24028 Battery Charger	950120-1	12.00	24.00
Centronics Interface:			
- PCB + disk (966008-1)	960052-C	16.25	32.50
- Disk (Windows)	966008-1	6.00	12.00
PC-Controlled AF Analyser (2):			
- Software on disk	966001-1	26.00	52.00

MARCH 1996

Houseplant Buzzer	950118-1	10.00	20.00
PIC-Controlled RDS Decoder:			
- PCB + PIC (966505-1)	960050-C	27.50	55.00
- PIC 16C84	966505-1	22.75	45.50

FEBRUARY 1996

SIMM tester:			
- PCB + EPROM (966503-1)	960039-C	28.25	56.50
- EPROM	966503-1	10.25	20.50
I2C Interface for Centronics port:			
- PCB + disk (946202-1)	950063-C	20.25	40.50
- control software on disk	946202-1	12.25	24.50
Passive VU meter	950124-1	8.00	16.00
Icy Roads Warning	960029-1	6.00	12.00

JANUARY 1996

SECAM-to-PAL Converter	950078-2	29.00	58.00
Passive Component Tester - PCB	960032-1	13.75	27.50
- Front panel foil		Not available	

DECEMBER 1995

3.3-15V Power Supply	950106-1	9.25	18.50
Practice Amplifier for Guitars			
PCB + front panel foil	950016-C	30.50	61.00
PCB only	950016-1	17.25	34.50
Front panel foil only	950016-F	13.75	27.50
Smart Transistor Tester:			
- PCB + PIC (956502-1)	950114-C	44.25	88.50
- PIC 16C71	956502-1	35.50	71.00
Micro PLC System:			
- PCB + 87C750/51 + disk	950093-C	44.50	89.00
- 87C750/51	956514-1	24.50	49.00
- control software on disk	956016-1	10.00	20.00
Active potentiometer	954099-1	9.50	19.00
Descaler	954080-1	5.75	11.50
Active probe	954093-1	8.00	16.00
Two-way PC-Fax Interface	954033	11.75	23.50

NOVEMBER 1995

PIP Processor:			
- PCB + 87C51 (956505-1)	950078-C	54.75	109.50
- 87C51	956505-1	30.75	61.50
FM noise squelch	950089-1	10.75	21.50
PA 300 power amplifier	950092-1	19.75	39.50
Jogging LED	950112-1	7.00	14.00
Oscilloscope prescaler	950115-1	27.75	55.50

OCTOBER 1995

MatchBox BASIC computer:			
- PCB, 87C51, disk and Quick Reference Card	950011-C	59.25	118.50
- 87C51	956508-1	43.50	87.00
- Course diskette (DOS)	956009-1	11.50	23.00
- Quick Reference Card	950011-P	3.25	6.50

SEPTEMBER 1995

Hi-Fi headphone amplifier	950064-1	5.00	10.00
Dongle safe:			
- PCB	950069-1	12.75	25.50
- GAL IC2 (20V8)	956511-1	10.00	20.00
- GAL IC6 (22V10)	956512-1	11.75	23.50
HexFET power amp upgrade:			
- amplifier PCB	930102	12.75	25.50
Copyleft eliminator update:			
- PCB + MACH (956504-1)	950084-C	40.50	81.00
- MACH IC	956504-1	36.50	73.00
RF tone-dip oscillator	950095-1	5.25	10.50

JULY/AUGUST 1995

Simple RF function generator	950023-1	7.50	15.00
Alkali/Manganese battery charger	950065-1	6.75	13.50
Fast charger for NiCd batteries:			
- PCB + ST62T20 (956509-1)	950076-C	22.75	45.50
- ST62T20	956509-1	14.75	29.50
Simple I/O card	954074-1	11.50	23.00

For availability of older items, please contact our Dorchester office.

Elektor Electronics slipcase




Price £2.95 + P&P (£1.50 UK, £2.00 outside UK)

CircuitMaker[®]

The Virtual Electronics Lab[™]

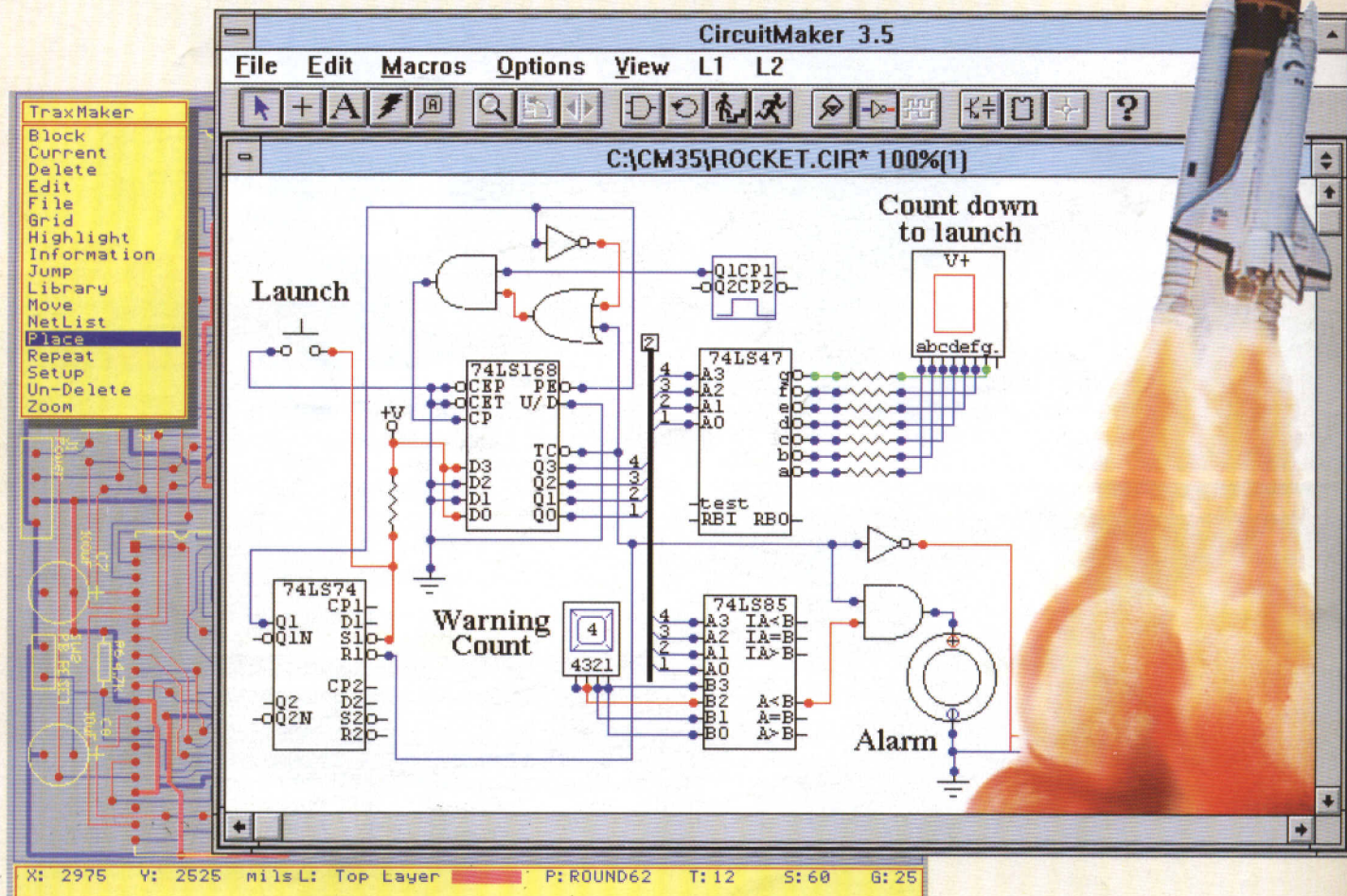where you can launch today's electronics project
into tomorrow and beyond...



TraxMaker[™]

- DOS version only £199
- 30 day satisfaction guarantee
- user definable "Design Rules"
- imports CircuitMaker PCB netlist
- automatic or manual routing of tracks
- 8 layer, 32" x 32" maximum board size
- automatic or manual component placement

*New
Product*

CircuitMaker[®]

- still only £199
- PCB netlist export
- includes 1500+ devices
- SPICE netlist import/export
- professional schematic features
- digital, analog and mixed-mode simulation

*New Windows
95/NT/3.1x
Versions*

**Call now to order your complete circuit design system
or request additional information:**

01480-300-695

Fax: 01480 461 654

Lab-Volt (UK) Ltd

28 Stephenson Road
Industrial Estate
St. Ives
Cambridgeshire PE17 4WJ
England

FREE ON-LINE DEMO:

AOL: file search, CircuitMaker
CompuServe: GO MICROCODE
Internet: <http://www.microcode.com>
All trademarks are the property of their owners.